



## 4. ELECTRICAL PRINCIPLES

### Chapter 4.2 Electrical and magnetic fields

### ARRL Amateur Extra Class






## Section 4.1

# Electric field

Caused by a difference in charge

Field lines from + to -

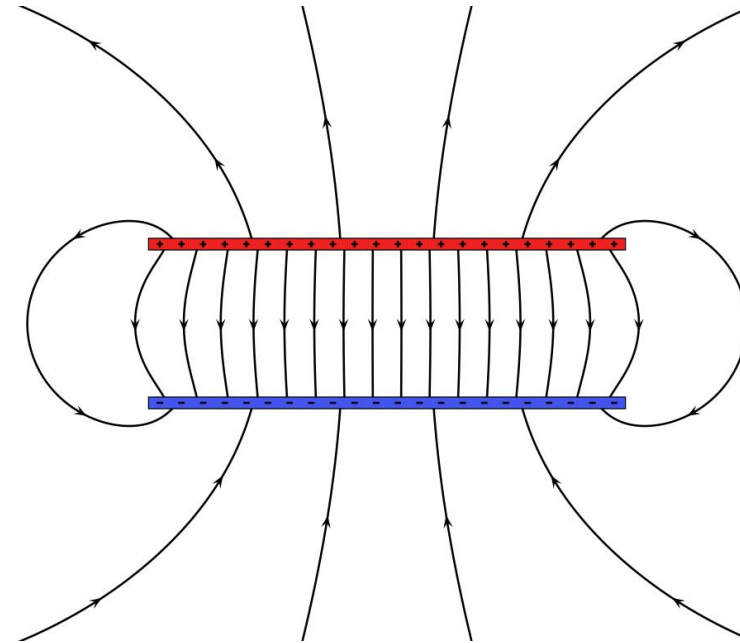



# Magnetic field


Magnetic field around a wire

Proportional to the current

Direction depends on direction of the current flow

**Current flow :**  
positive -> negative  
Use **RIGHT** hand rule


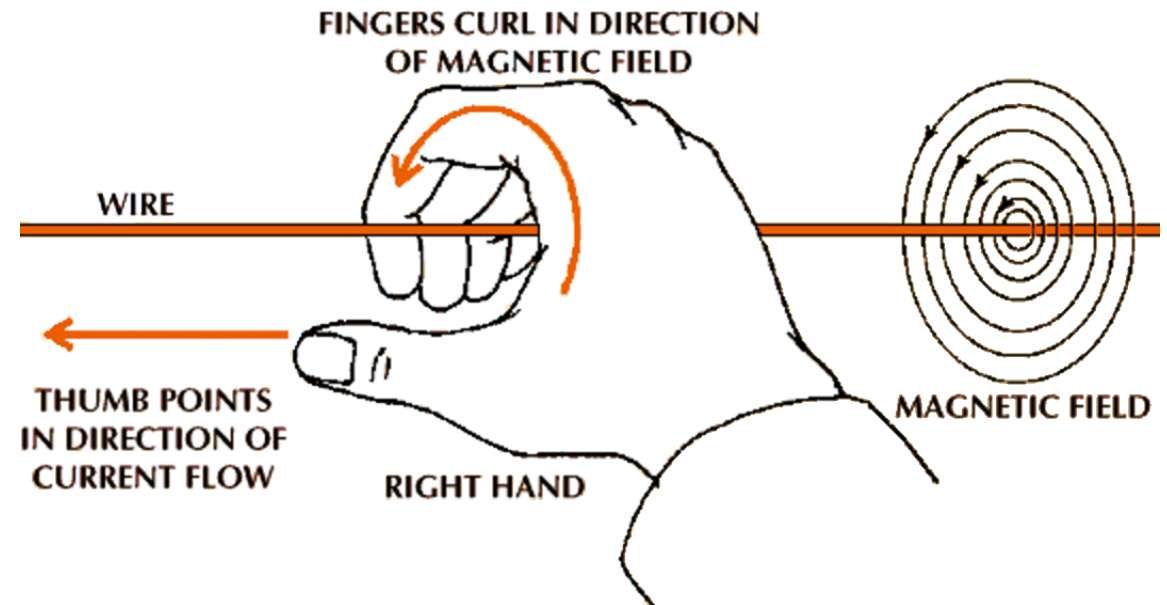
**Electron flow :**  
negative -> positive  
Use **LEFT** hand rule





## Section 4.3

# Time constant - capacitor

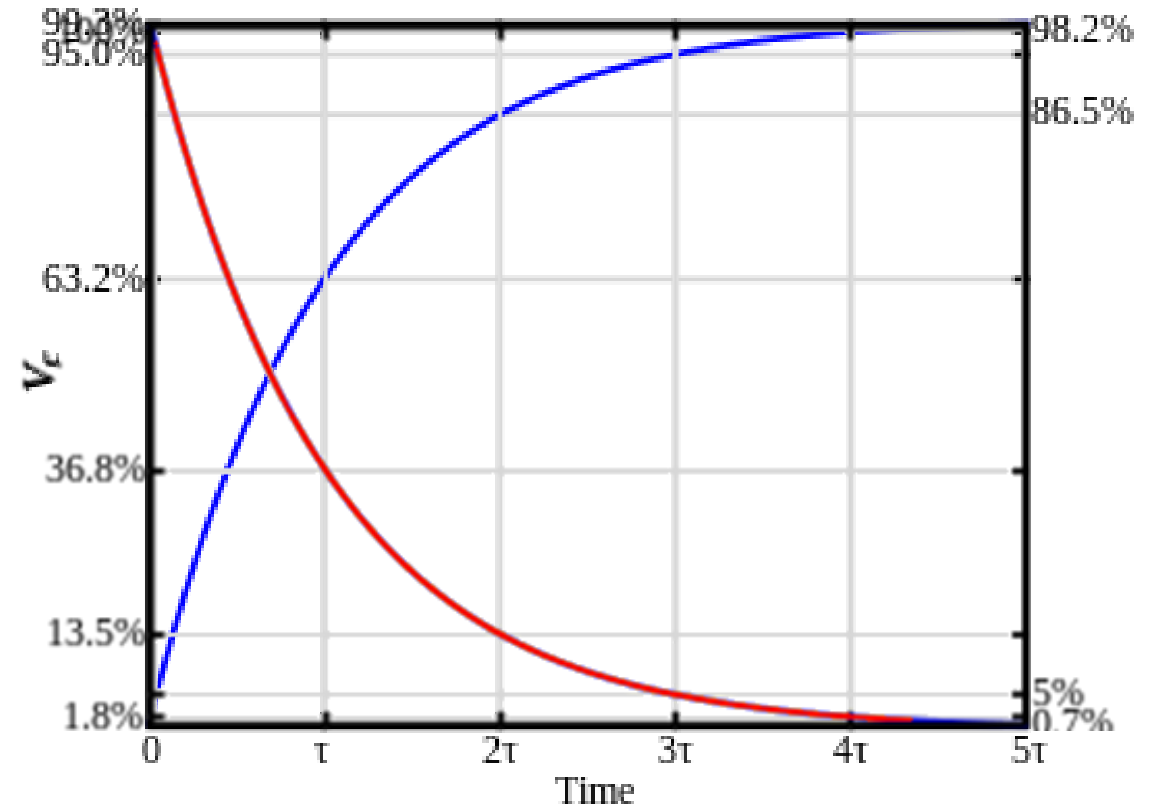
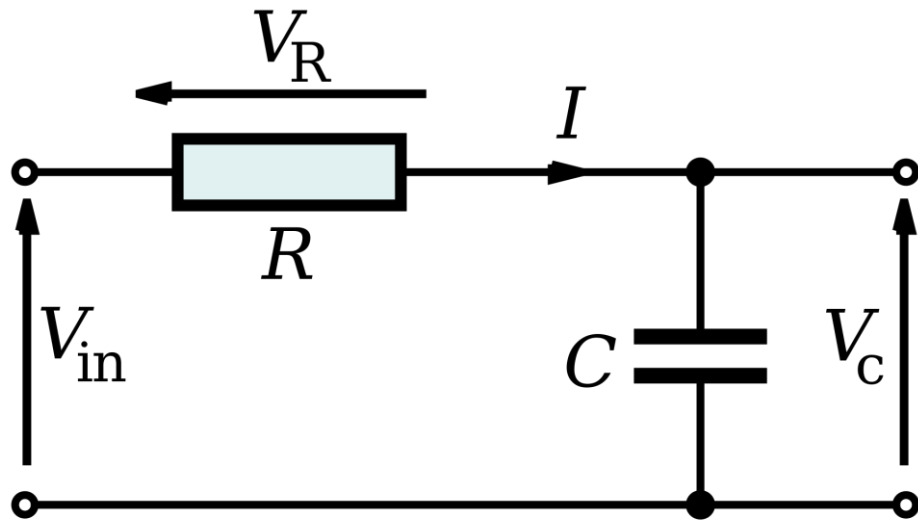




# Time constant – capacitor : math

Charging  $V(t) = V_0(1 - e^{-t/\tau})$

Discharging  $V(t) = V_0(e^{-t/\tau})$

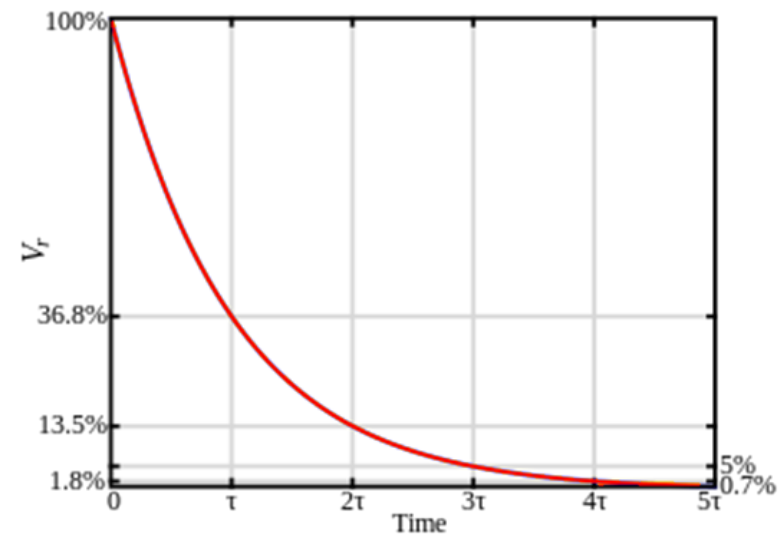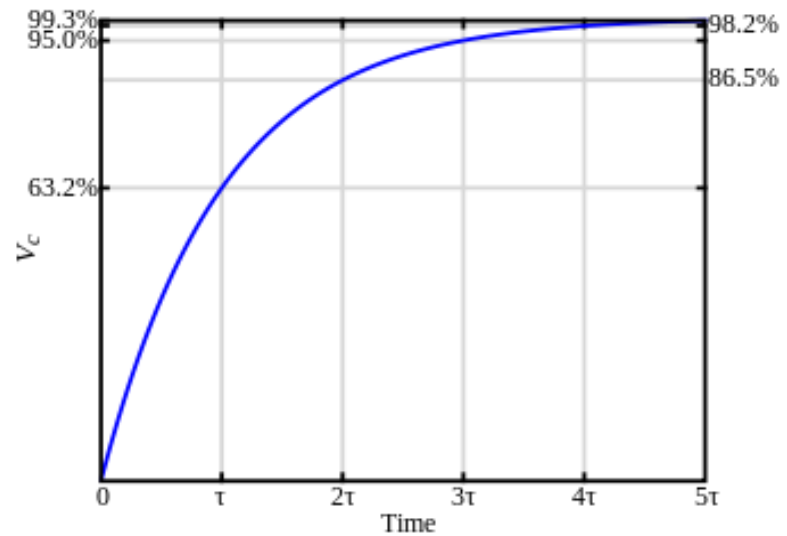

$$\tau = RC \text{ [seconds]}$$



# Time constant – capacitor : math example


Q: What is the time constant ?

$$\tau = RC \text{ [seconds]}$$

$$\tau = 220\mu F \cdot 1M\Omega$$

$$\tau = 220 \cdot 10^{-6} \cdot 1 \cdot 10^6$$



$$\tau = 220 \cdot 1 = 220s$$

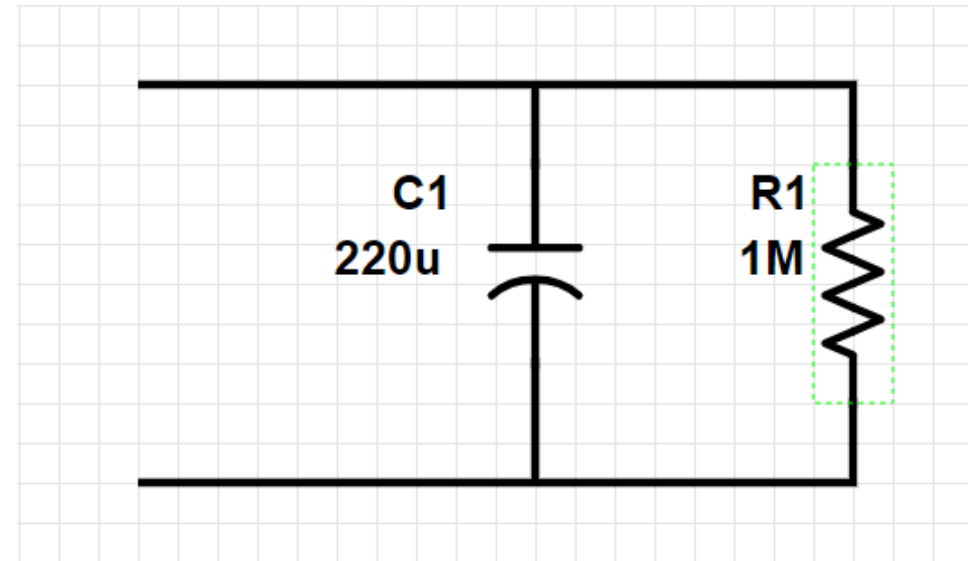



# Section 4.1

## Time constant - inductor

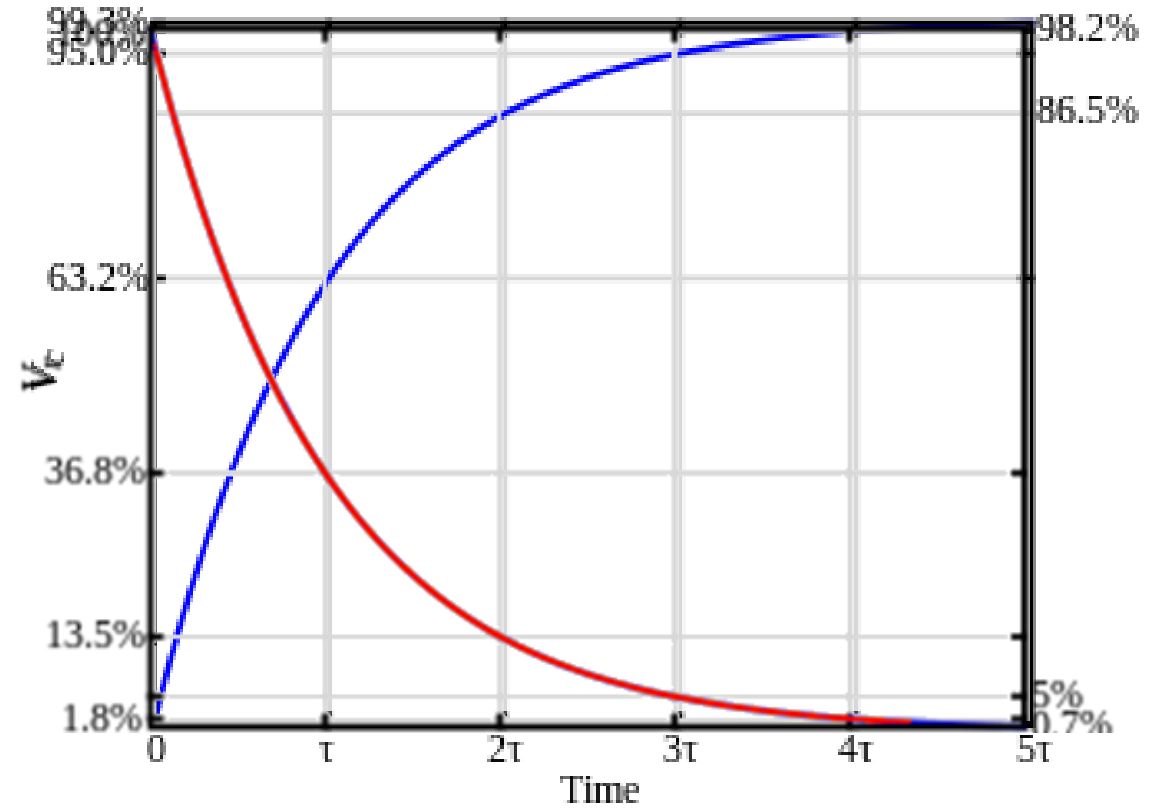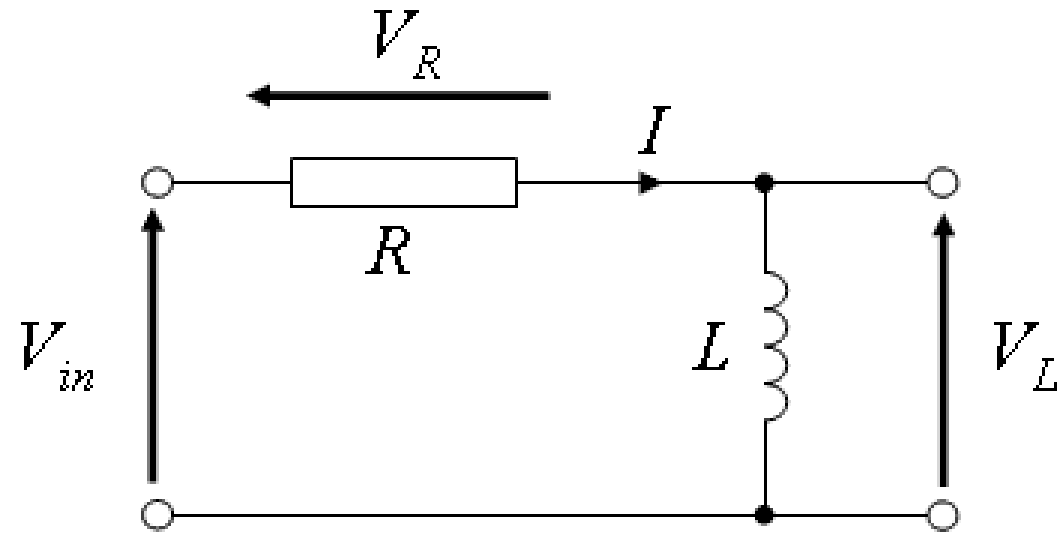





# Time constant – inductor : math

Charging

$$V(t) = V_0(e^{-t/\tau})$$

Discharging

$$V(t) = V_0(1 - e^{-t/\tau})$$

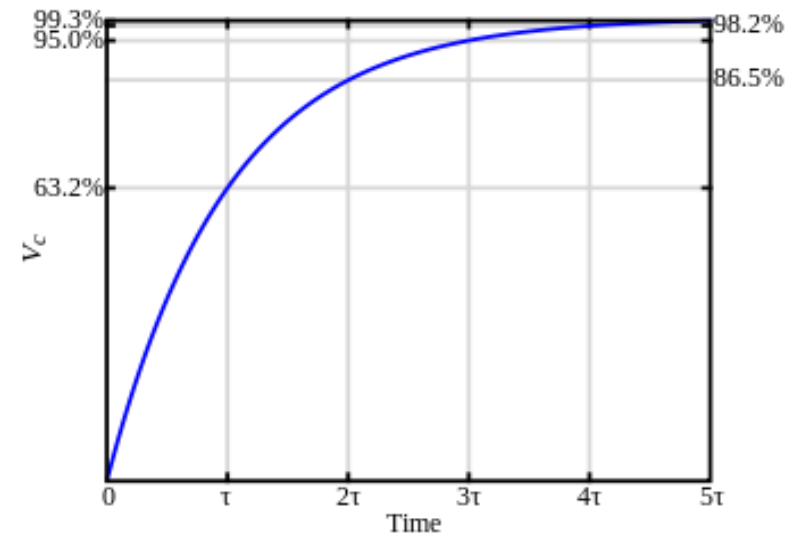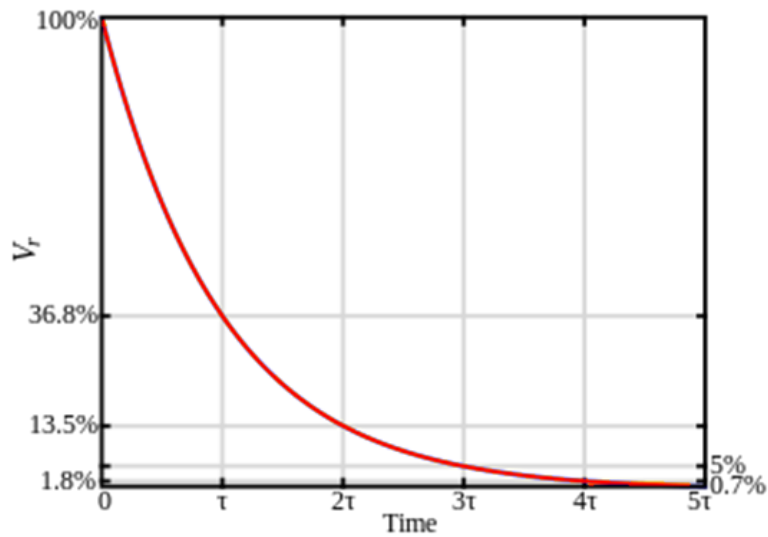

$$\tau = \frac{L}{R} \text{ [seconds]}$$





# Time constant – demo


Time constant:

$$\tau = RC \text{ [seconds]}$$

$$C = \frac{\tau}{R}$$

Prefix cheat-sheet:

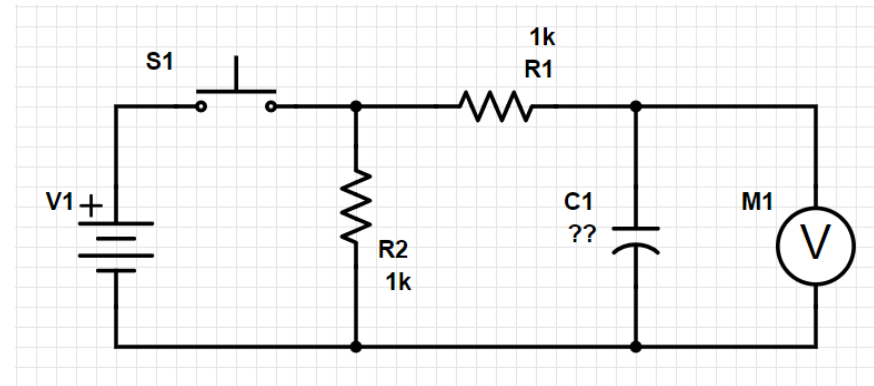- M =  $10^6$
- k =  $10^3$
- m =  $10^{-3}$
- $\mu$  =  $10^{-6}$
- p =  $10^{-9}$






# Section 4.3

## Phase angle



Current flows when capacitor charging

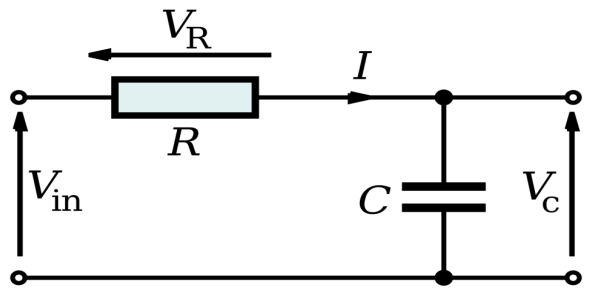

When capacitor fully charged, no current flows

If we feed it with sinus wave (AC);

Current Leads Voltage: 'I' leads 'E'

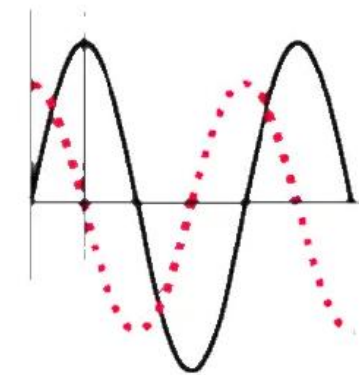
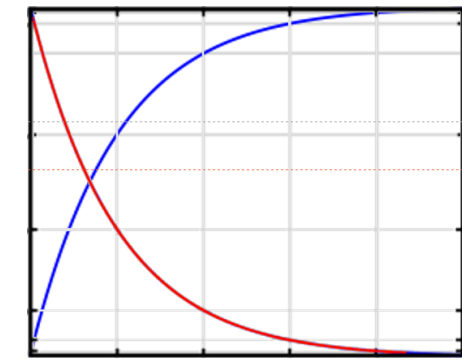


---- voltage  
---- current




# Phase angle

Current flows magnet field is static

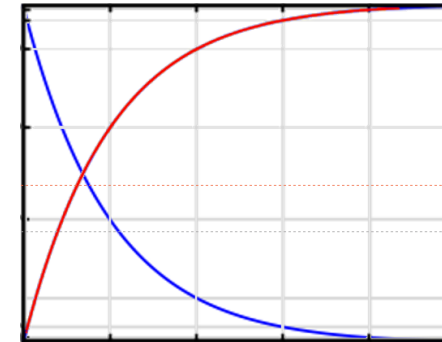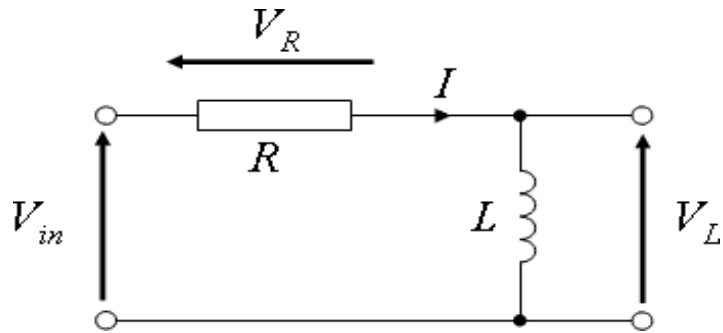

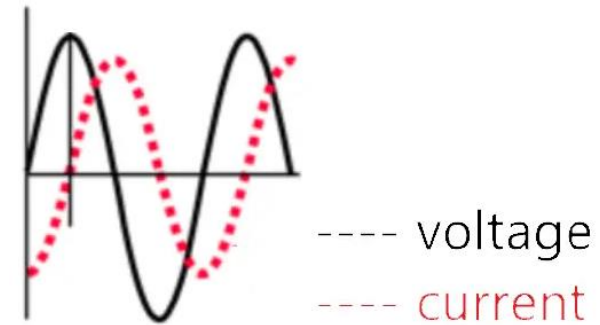If we feed it with sinus wave (AC);  
 Voltage leads Current: 'E' leads 'I'






# Phase angle


Inductive (L)

'E' leads 'I'

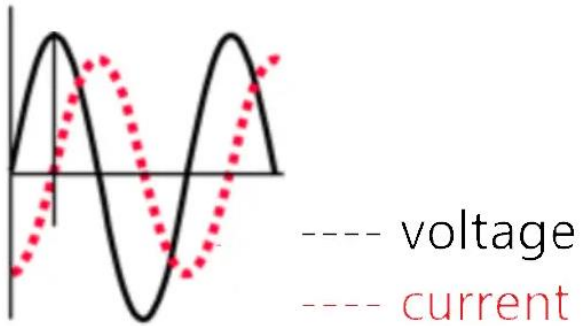

Capacitive (C)

'I' leads 'E'

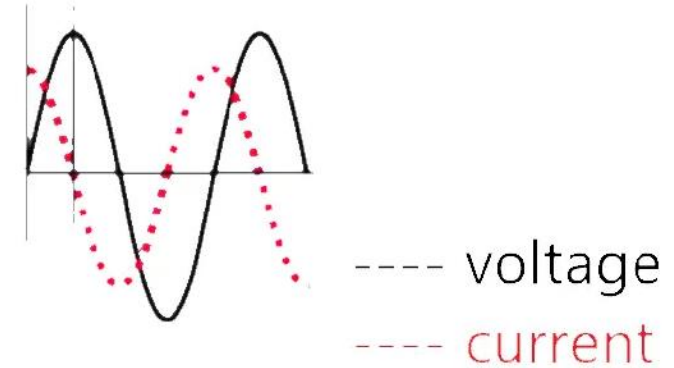

E-L-I the I-C-E man



# Complex impedance

Combining Resistance (R) and Reactance (X)


= Impedance (Z)

$Z = (\text{resistive part}) + j \cdot (\text{reactive part})$

$Z = R + jX$

Positive  $jX$  = inductive

Negative  $jX$  = capacitive

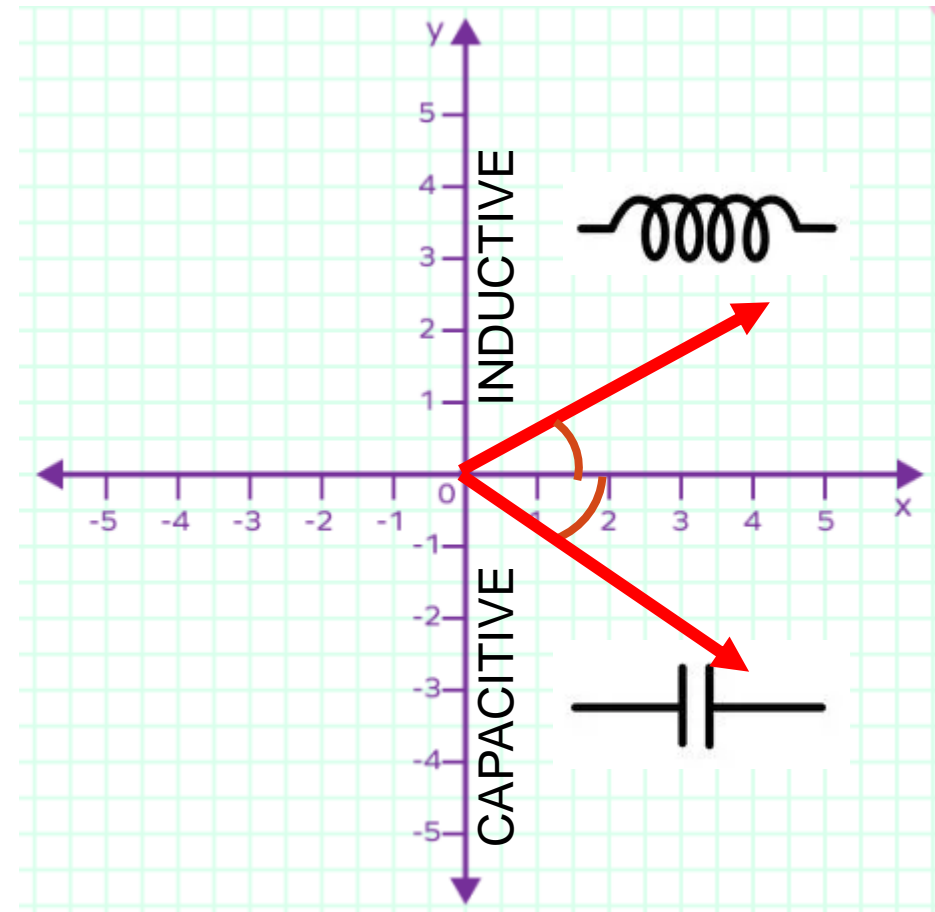




# Complex impedance


Calculate phase angle of two reactances in series:

$$Z = (250 + j100) + (200 - j400)$$

$$Z = 450 - j300$$

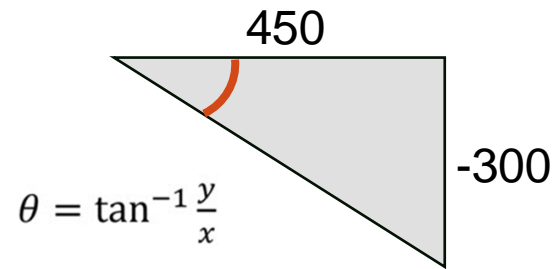
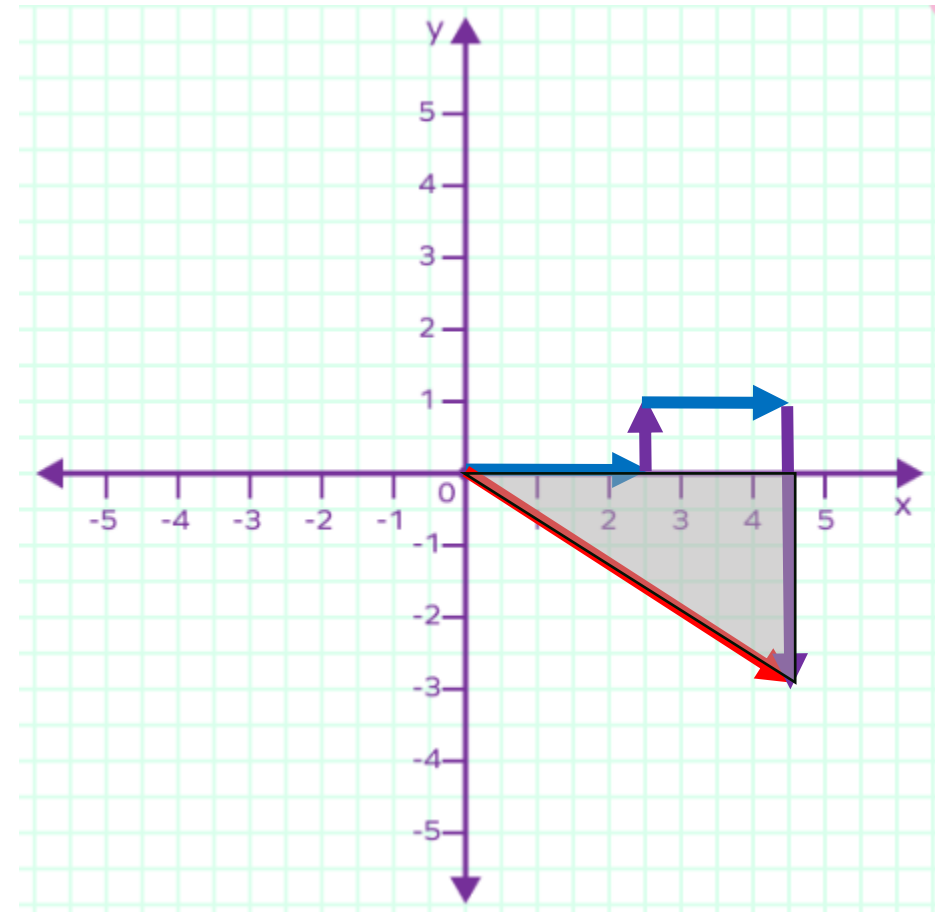
$$\theta = \tan^{-1} \left( \frac{-300}{450} \right) = -33.7$$





# QUESTIONS?

ONLINE EXAM REVIEW AND PRACTICE QUESTIONS:

**<http://www.arrl.org/examreview>**