



## **Technician License Course**

### **Chapter 3**

#### **Section 3.1 - Electricity**



# Fundamentals of Electricity



## Fundamentals of Electricity

- Radios are powered by electricity and radio signals are a form of electrical energy.
- A basic understanding of how we control electricity allows you to better install and operate your radio.




## Fundamentals of Electricity

- Electrons are negatively-charged atomic particles, usually surrounding an atom's positively-charged nucleus.
- Depending on the material, the electrons can move in response to an *electromotive force*.
- The electrons can move from atom to atom, or even completely free of the atoms.

Atom structure

- ⊕ Proton
- Neutron
- ⊖ Electron

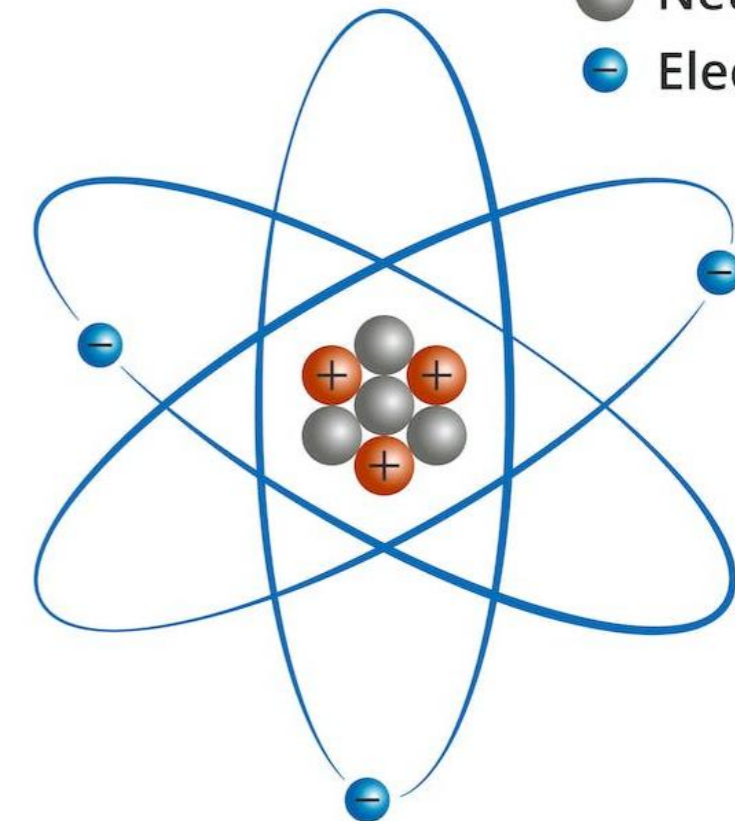




## Fundamentals of Electricity

- Electrical charge can be positive or negative.
- Opposite charges attract each other
- Electrical current is the flow of *electrons*.
- Electrons want to match up with an atom

Electricity Electron

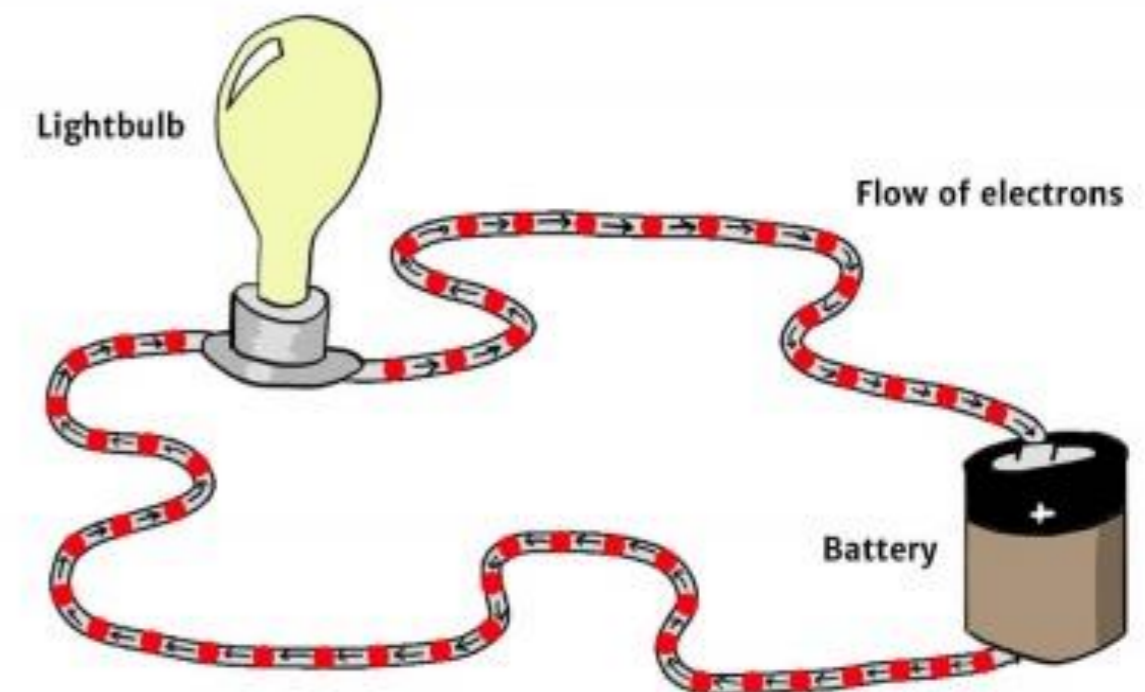



# Basic Electrical Concepts



## Basic Electrical Concepts

- **Current:** the movement of electrons, measured in *amperes (A)* by an ammeter, and represented by *I* in formulas
- **Voltage:** the amount of electromotive force (emf), also called electrical potential, measured in *volts (V)* by a *voltmeter*, represented by *E* or *V* in formulas



## Basic Electrical Concepts



- **Resistance:** the opposition to the movement of electrons, measured in *ohms* ( $\Omega$ ) by an *ohmmeter* and represented by R in formulas.
- Resistance is like friction and turns electrical energy into heat when current flows.
- **Conductors** permit current flow (low resistance) and **insulators** block current flow (high resistance).




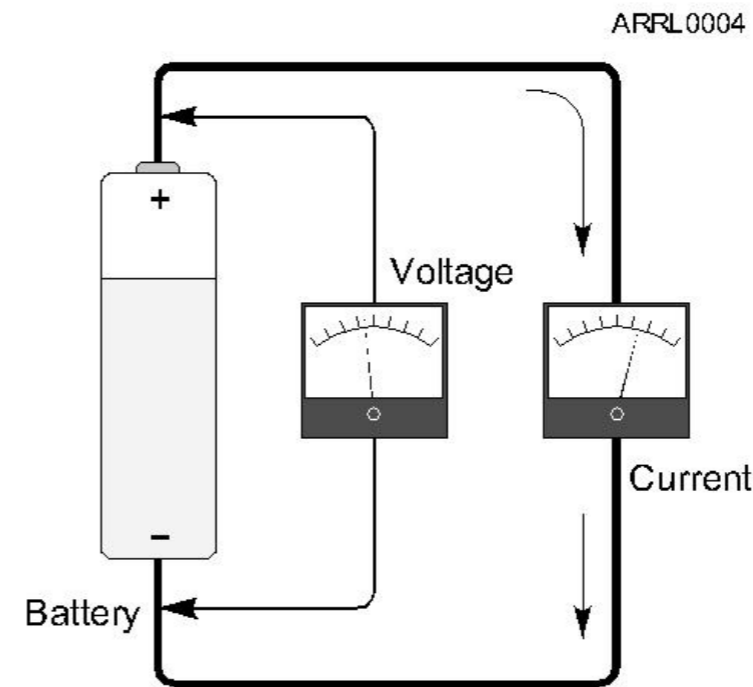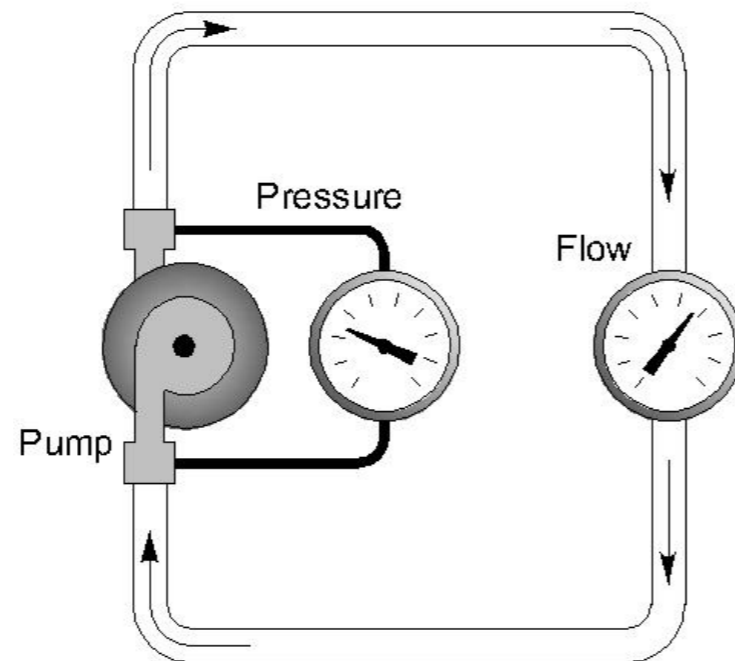
## Basic Electrical Concepts

- The flow of water through a pipe is a good analogy to understand the three characteristics of electricity and how they are related.








# Electricity: The Water Analogy

High Voltage, Low Current

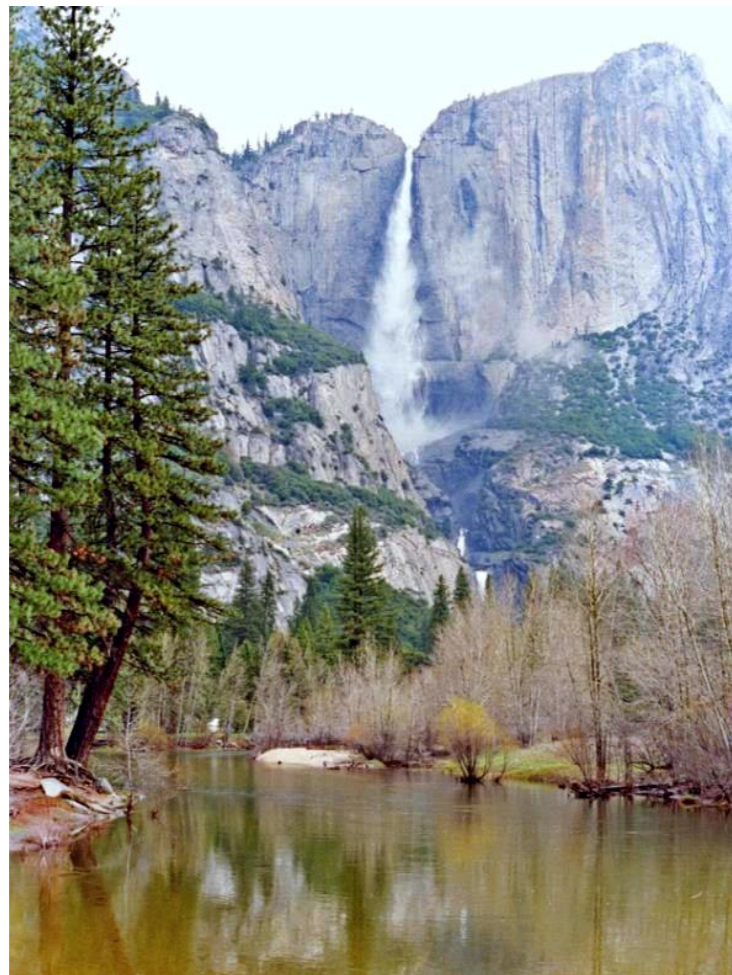

Low Voltage, High Current








## Basic Electrical Concepts

High Voltage, Low Current

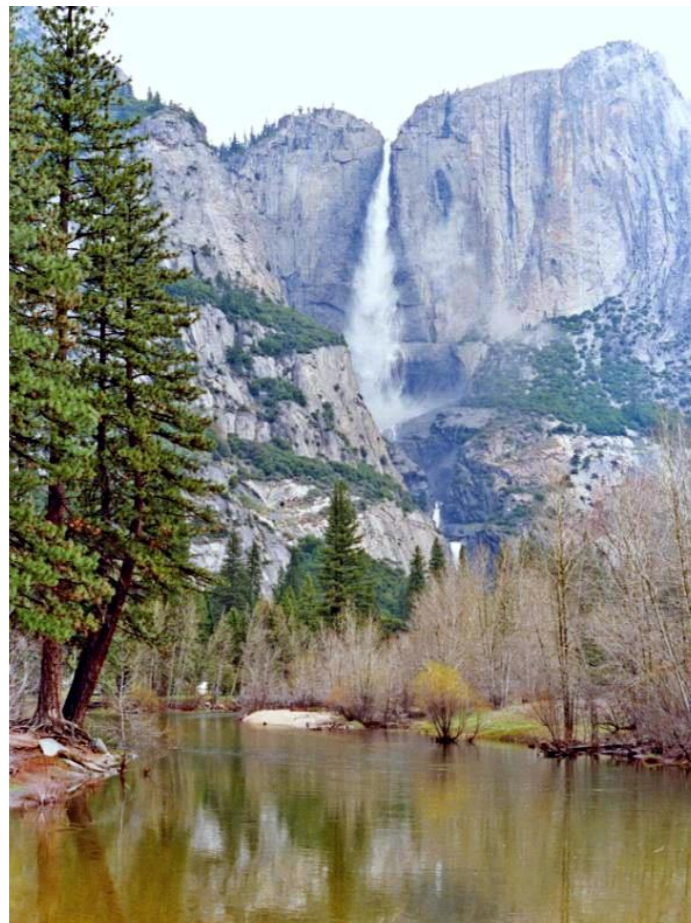

Low Voltage, High Current






## Basic Electrical Concepts

- Voltage from a *source* of electrical energy causes current to flow.
- Resistance is a material's opposition to the flow of current.
- Voltage, current and resistance affect each other. For example, higher voltage (bigger push) causes more current (more flow).


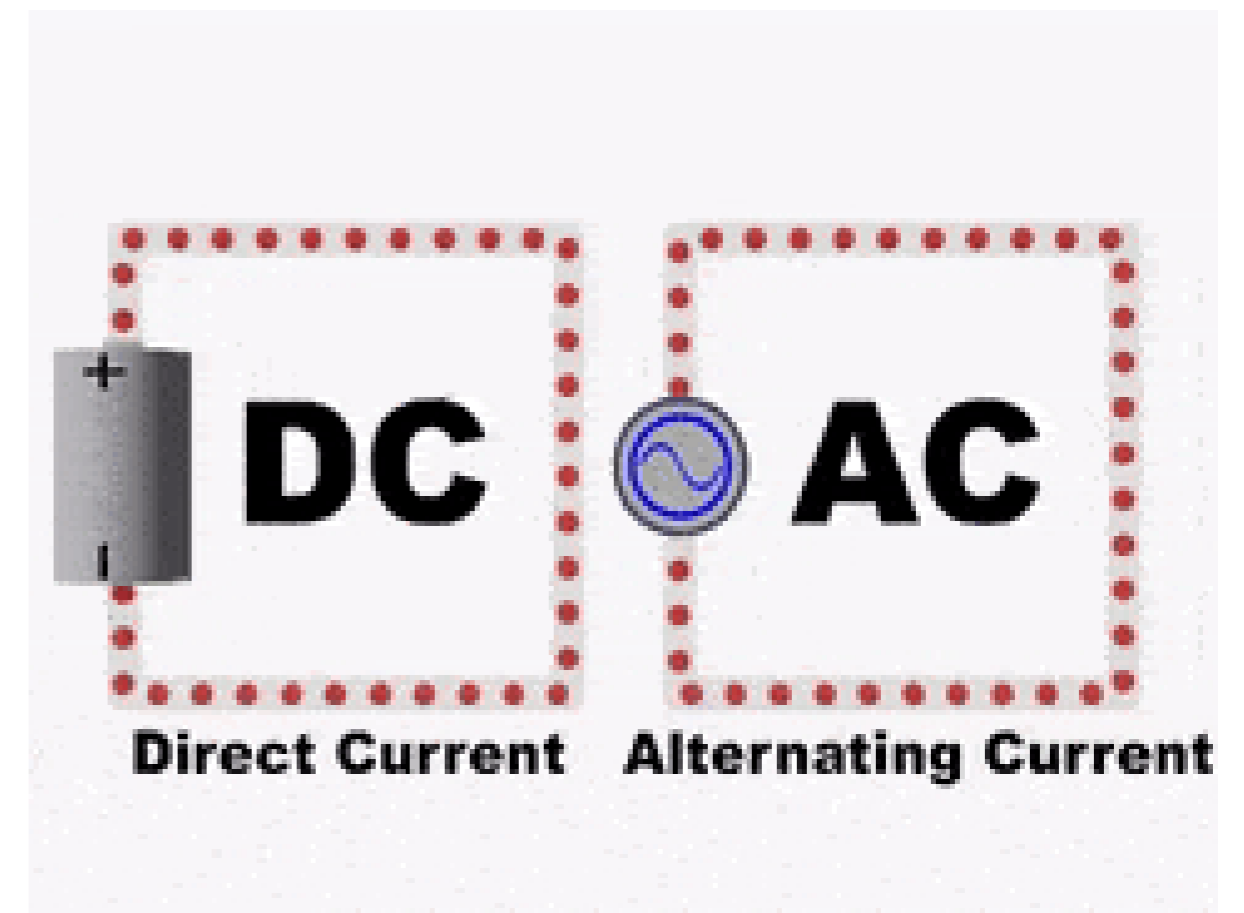
## The Two Kinds of Current

- Current that flows in only one direction, is called direct current (dc).
- Batteries are a common source of dc.







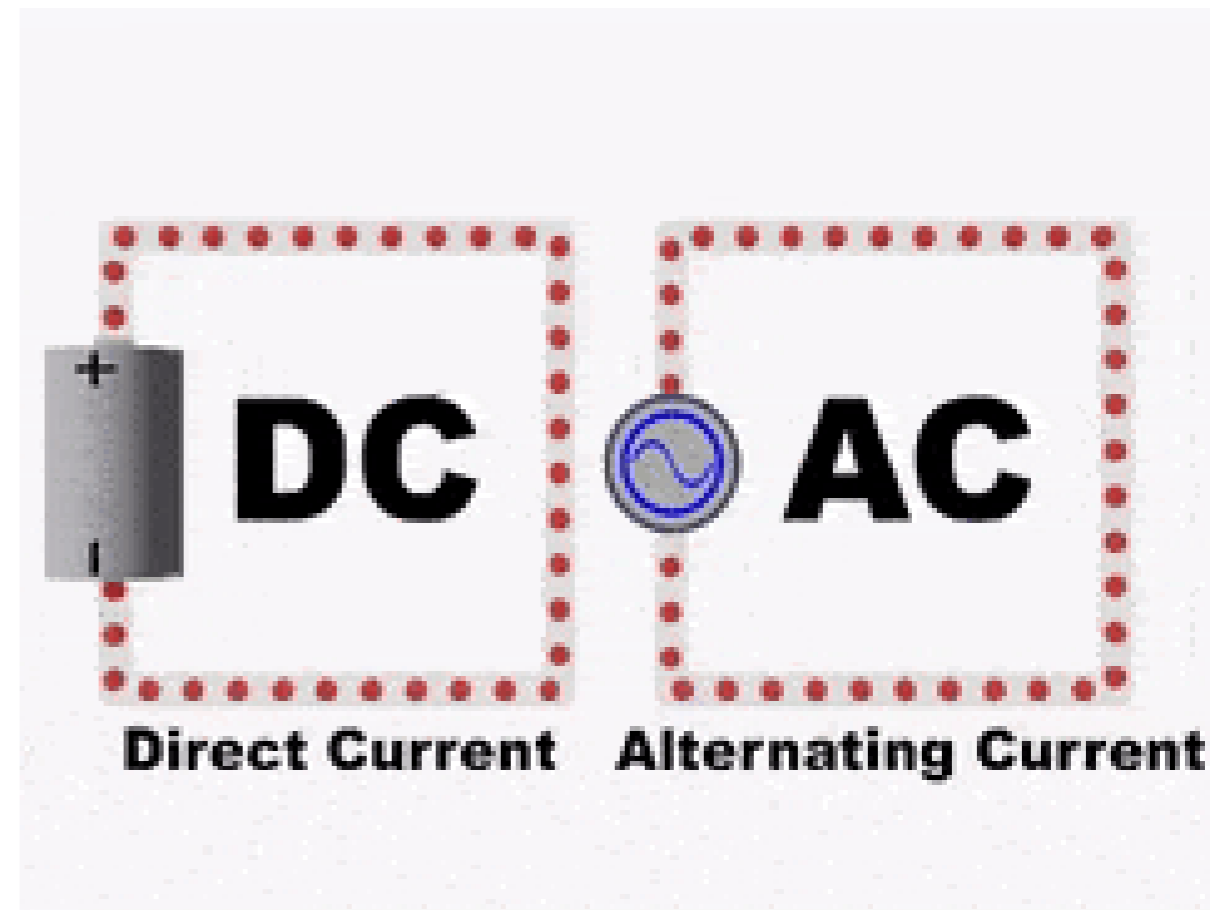
## The Two Kinds of Current


- Current that flows in one direction then in the opposite direction is called alternating current (ac).




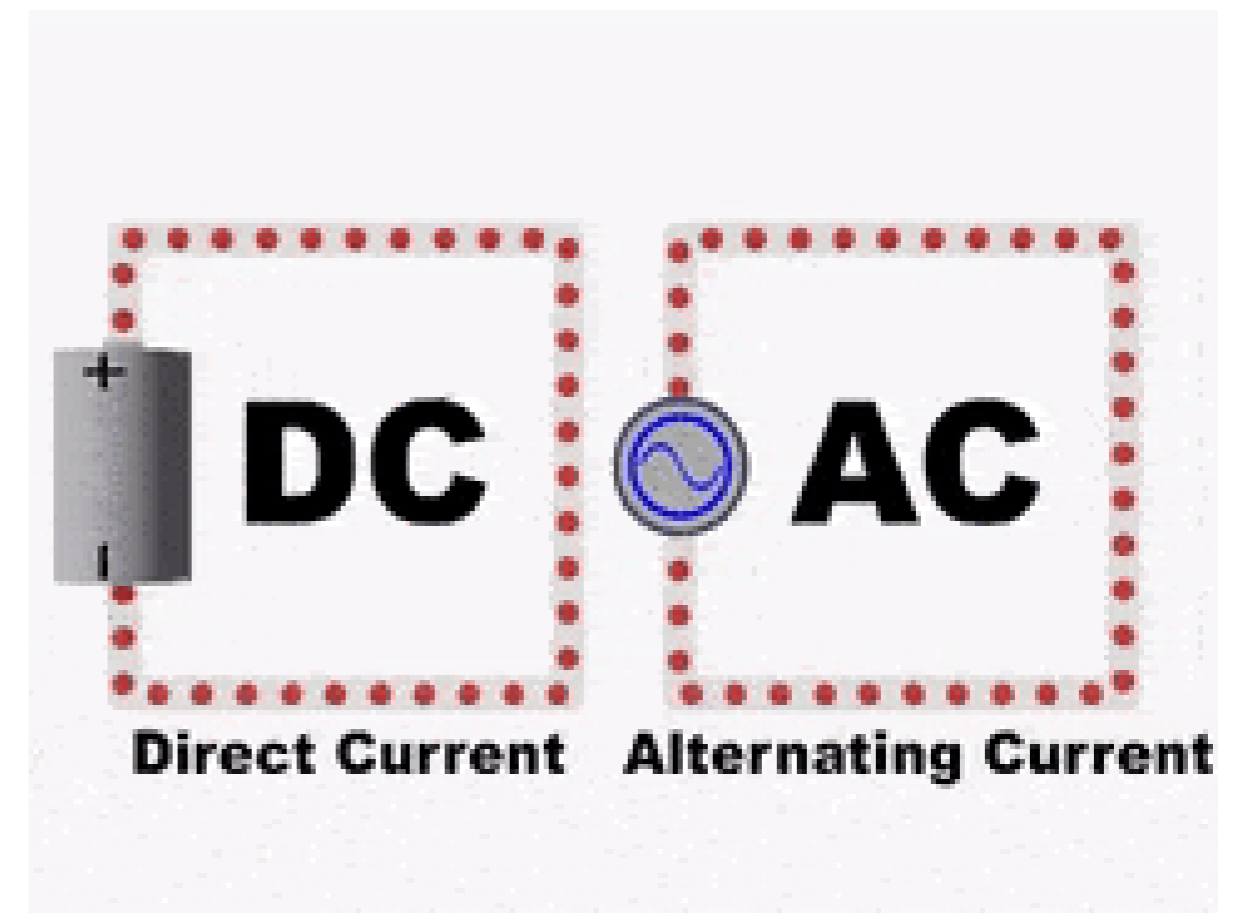
## The Two Kinds of Current


- Current that flows in one direction then in the opposite direction is called alternating current (ac).
- Household current is ac




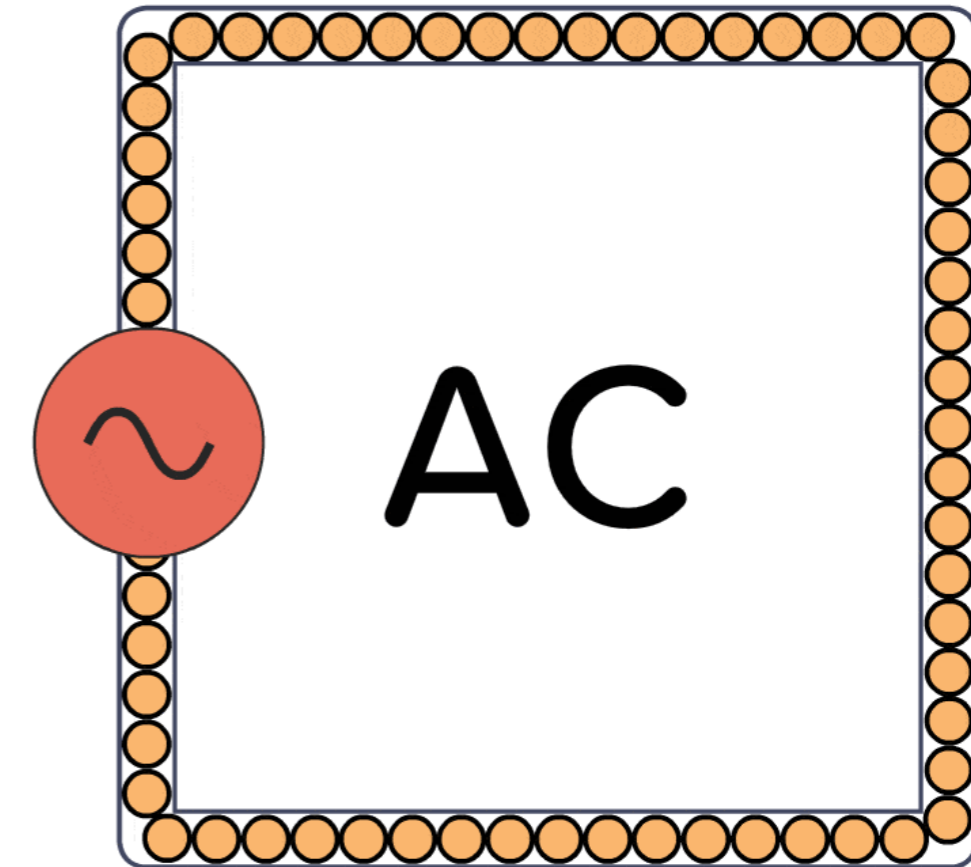
## The Two Kinds of Current

- AC current reverses direction on a regular basis
- Each process of reversing is a *cycle*.
- The number of cycles per second is *frequency*, measured in hertz (Hz).
- 1 Hz = 1 cycle per second








## The Electric Circuit: An Electronic Roadmap

- For current to flow, there must be a path from one side of the energy source to the other side of the source
- This path is called a *circuit*.


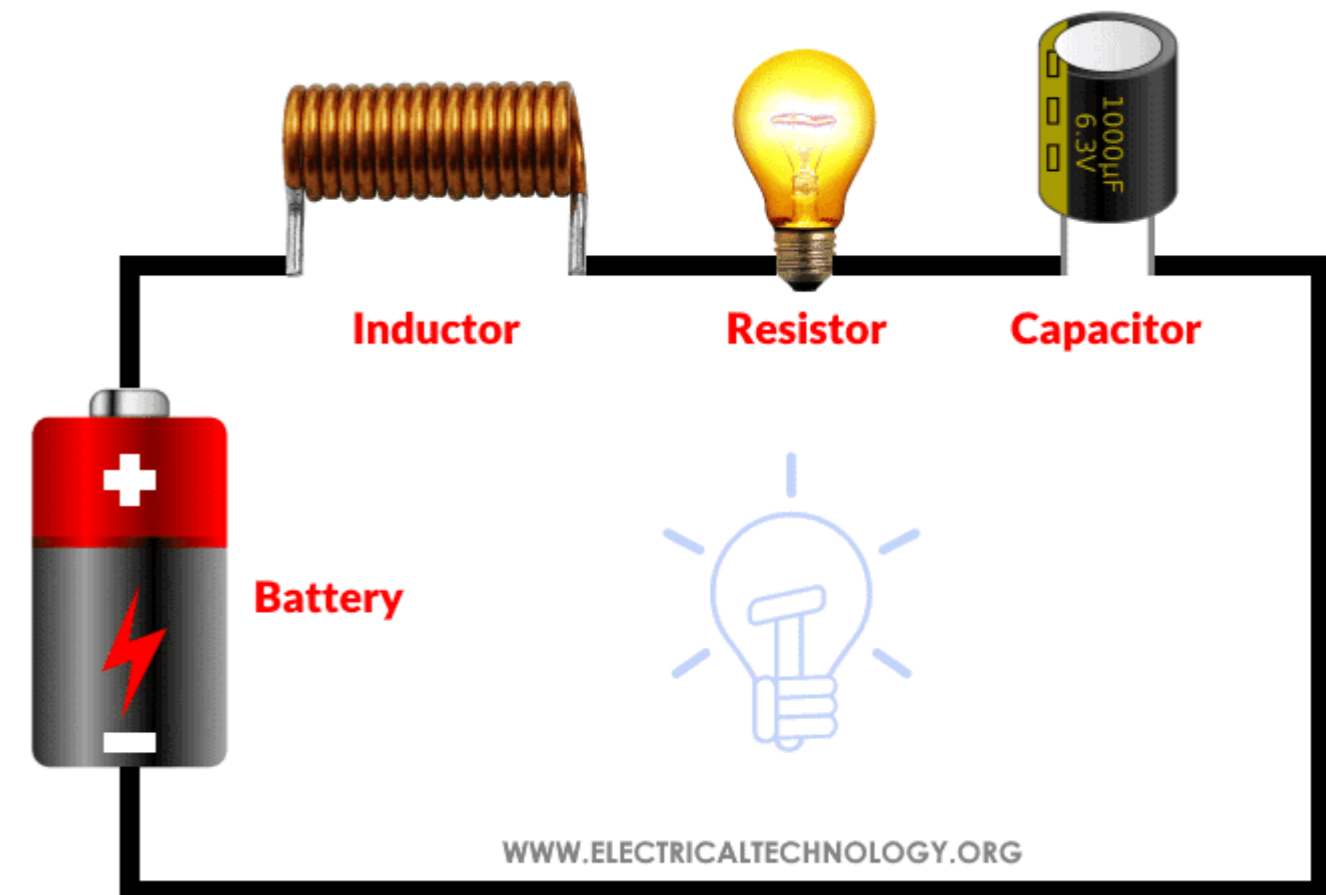
## The Electric Circuit: An Electronic Roadmap

- For current to flow, there must be a path from one side of the energy source to the other side of the source – this path is called a *circuit*.






## Series vs Parallel Circuits

- There are two types of electric circuits:
  - Serial and,
  - Parallel


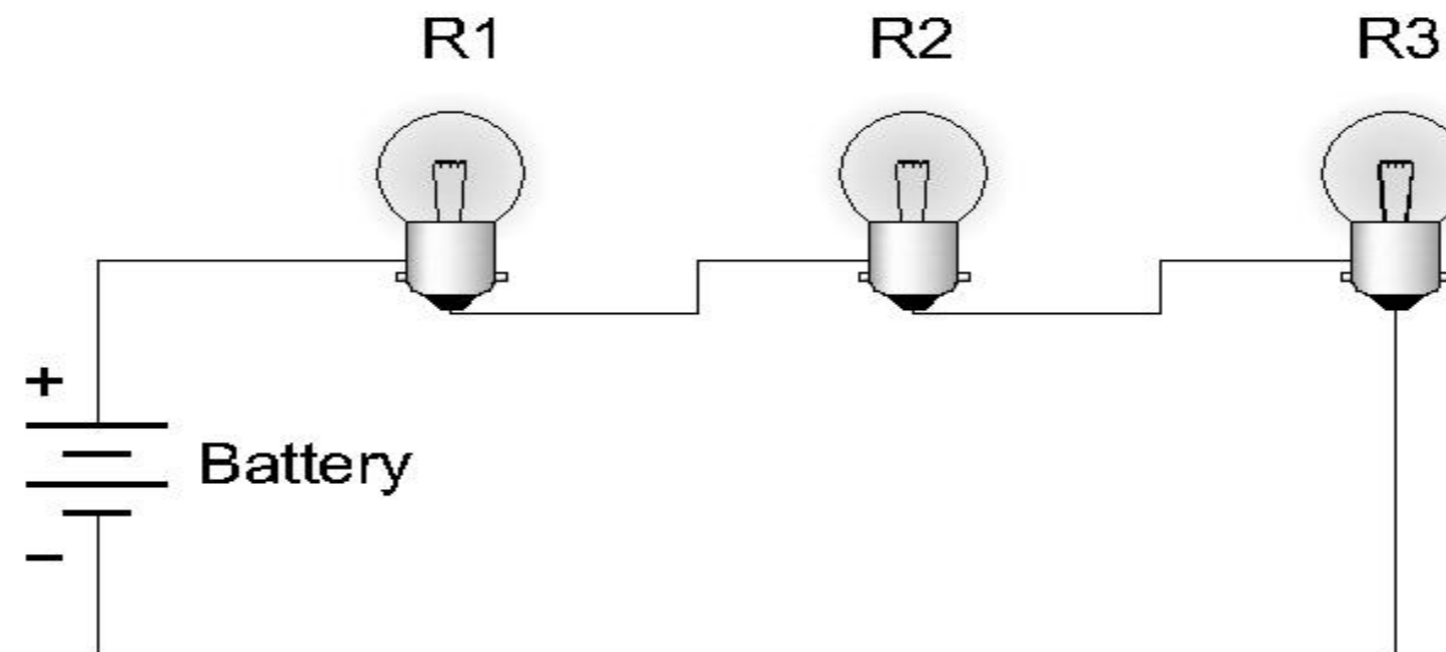
## Series Circuits


- Series circuits provide one and only one path for current flow
- Current the same through each component





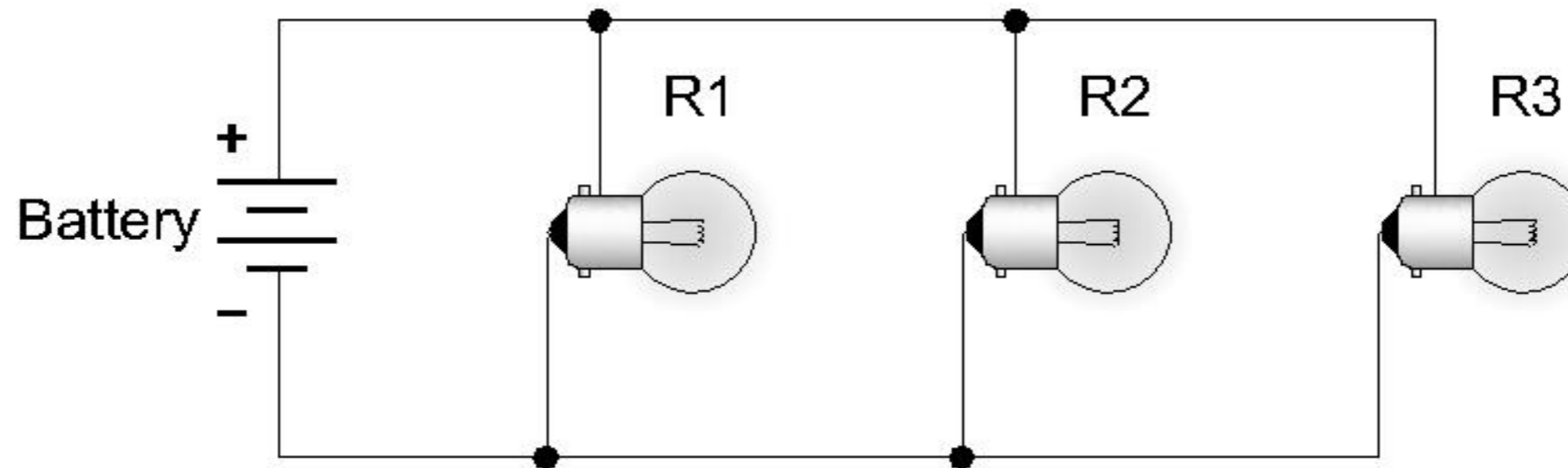
## Parallel Circuits

- Parallel circuits provide multiple paths for current flow.
- Voltage is the same across all components






## How do you connect a Volt/Amp Meter?

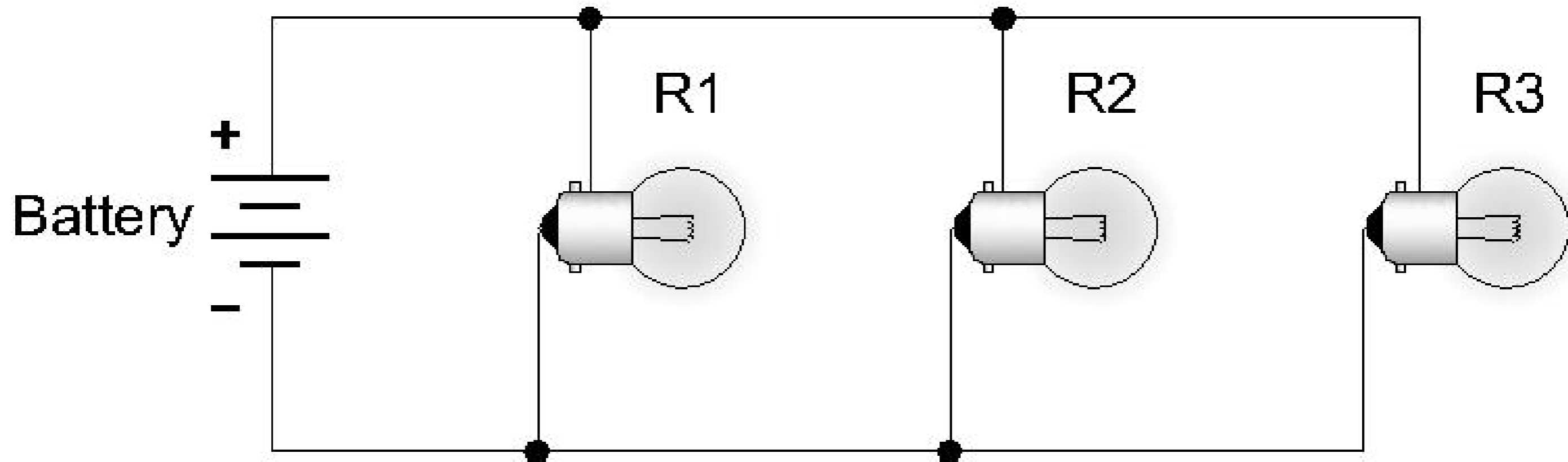



## Ohm's Law

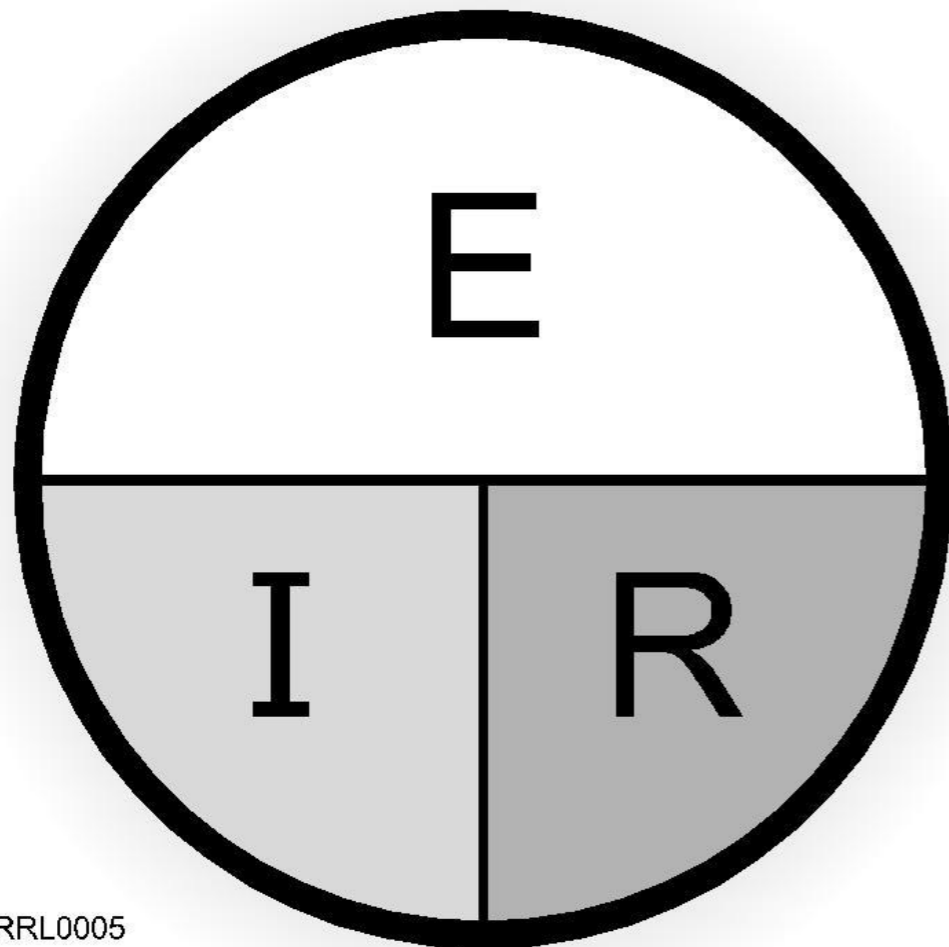


$$E = I \times R$$



## Ohm's Law

- E represents voltage  
- Units – volts (V)

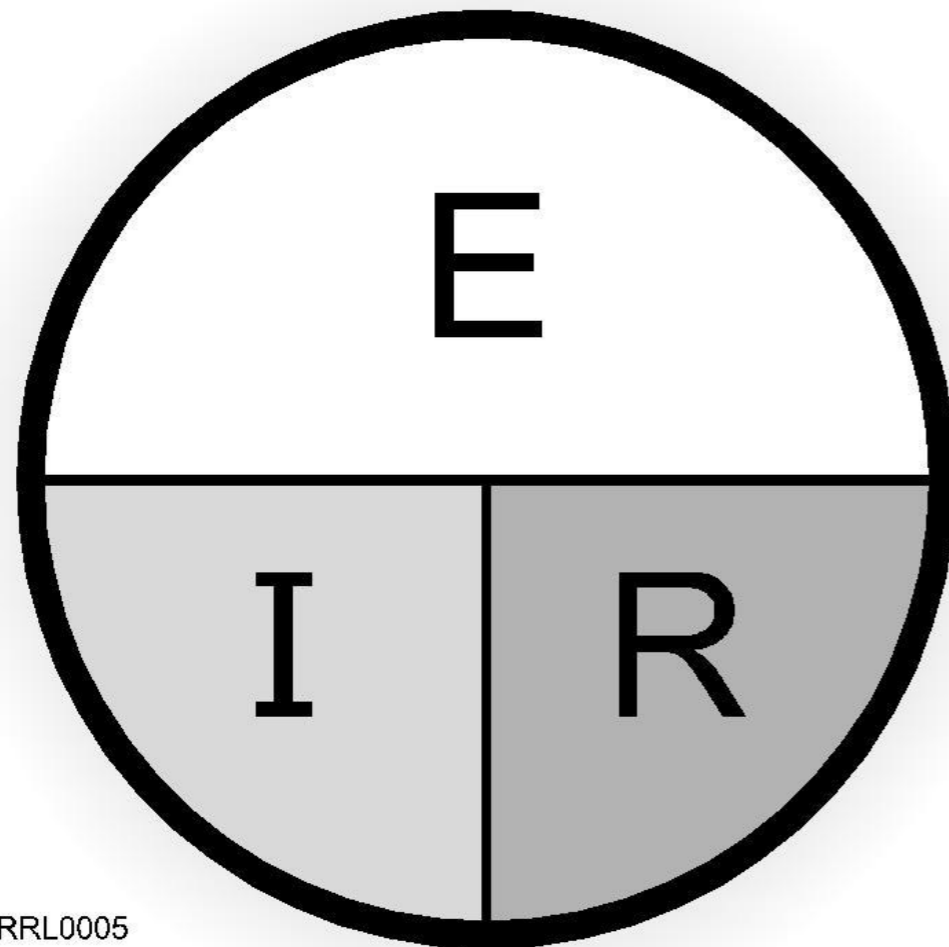


ARRL0005





## Ohm's Law

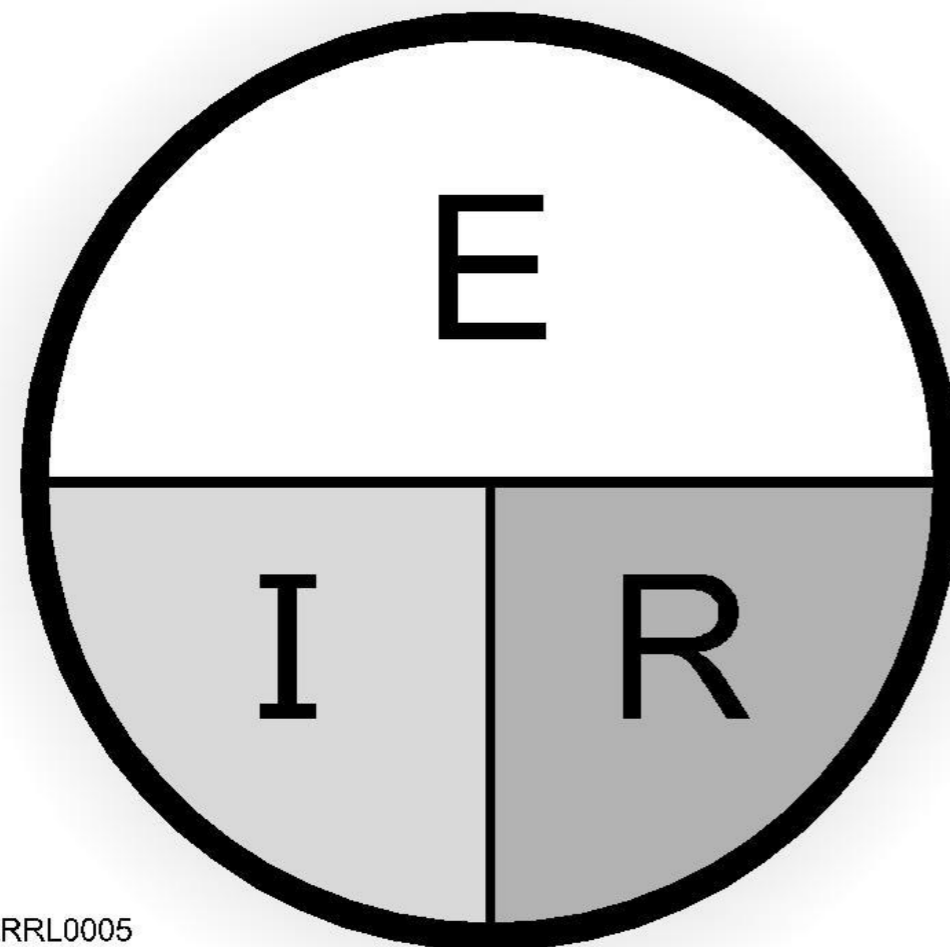


ARRL0005

- E represents voltage  
- Units – volts (V)
- I represents current  
- Units – amperes (A)




## Ohm's Law

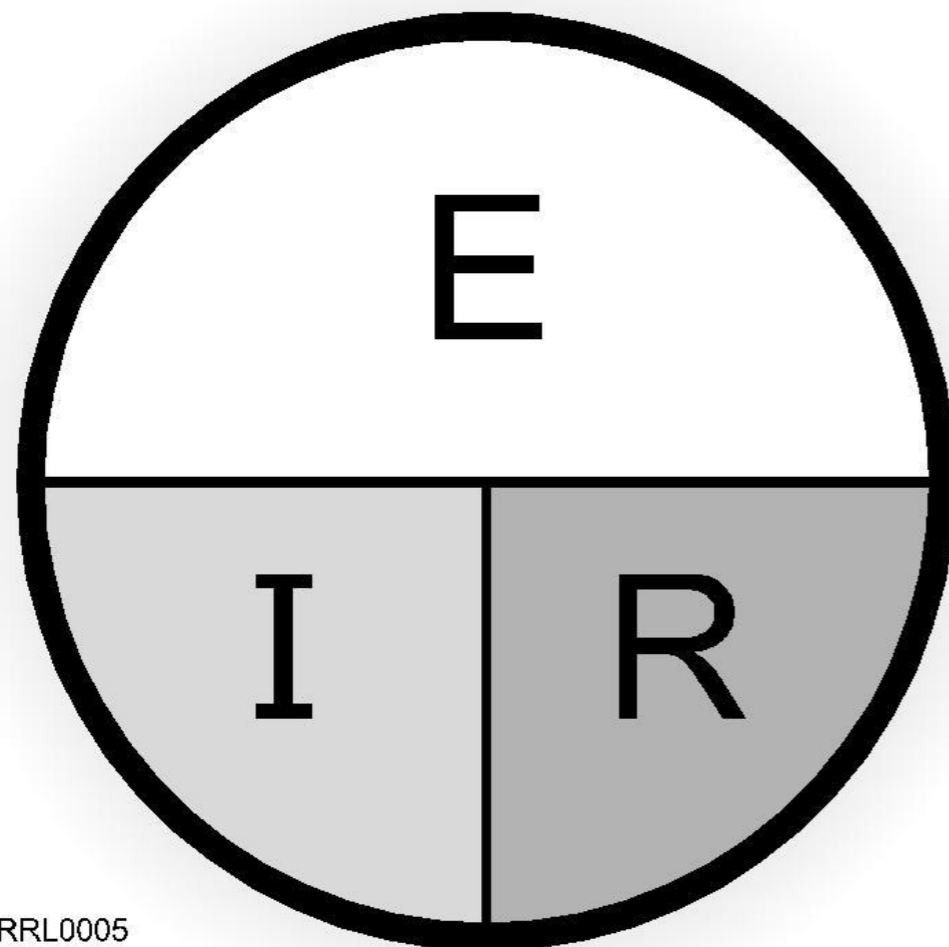

- E represents voltage  
- Units – volts (V)
- I represents current  
- Units – amperes (A)
- R represents resistance  
- Units – ohms ( $\Omega$ )



## Ohm's Law

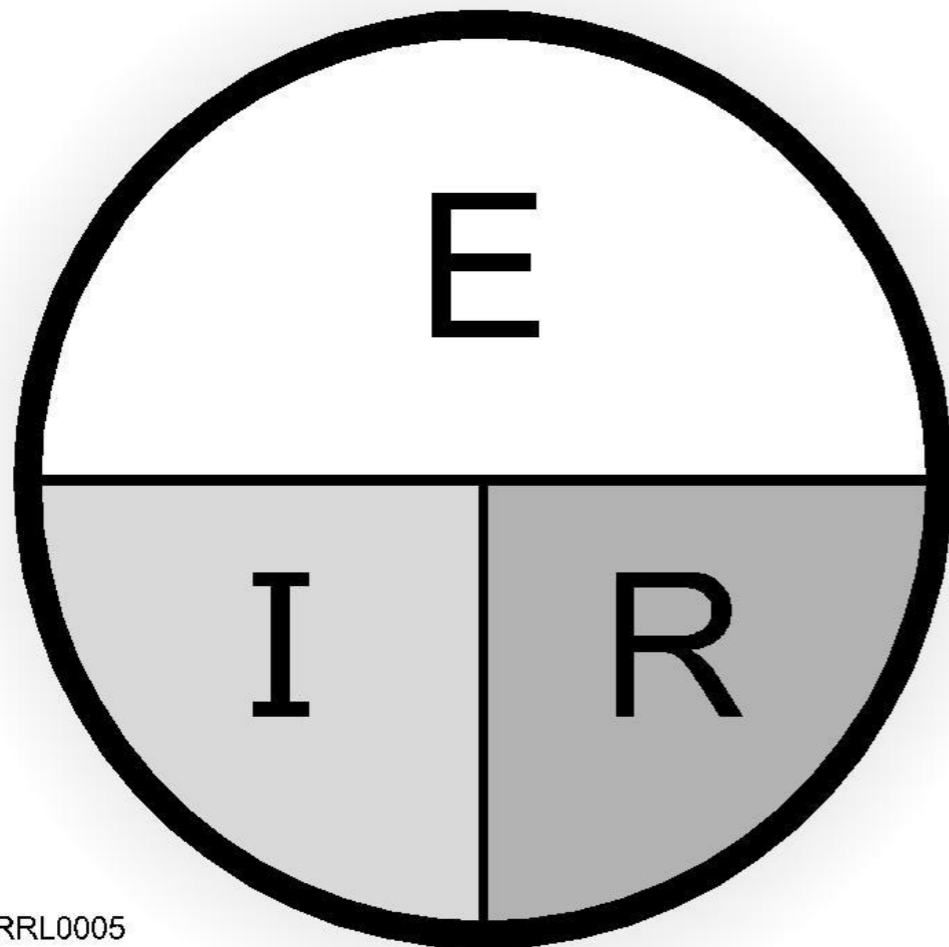


ARRL0005

•  $R = E / I$



## Ohm's Law

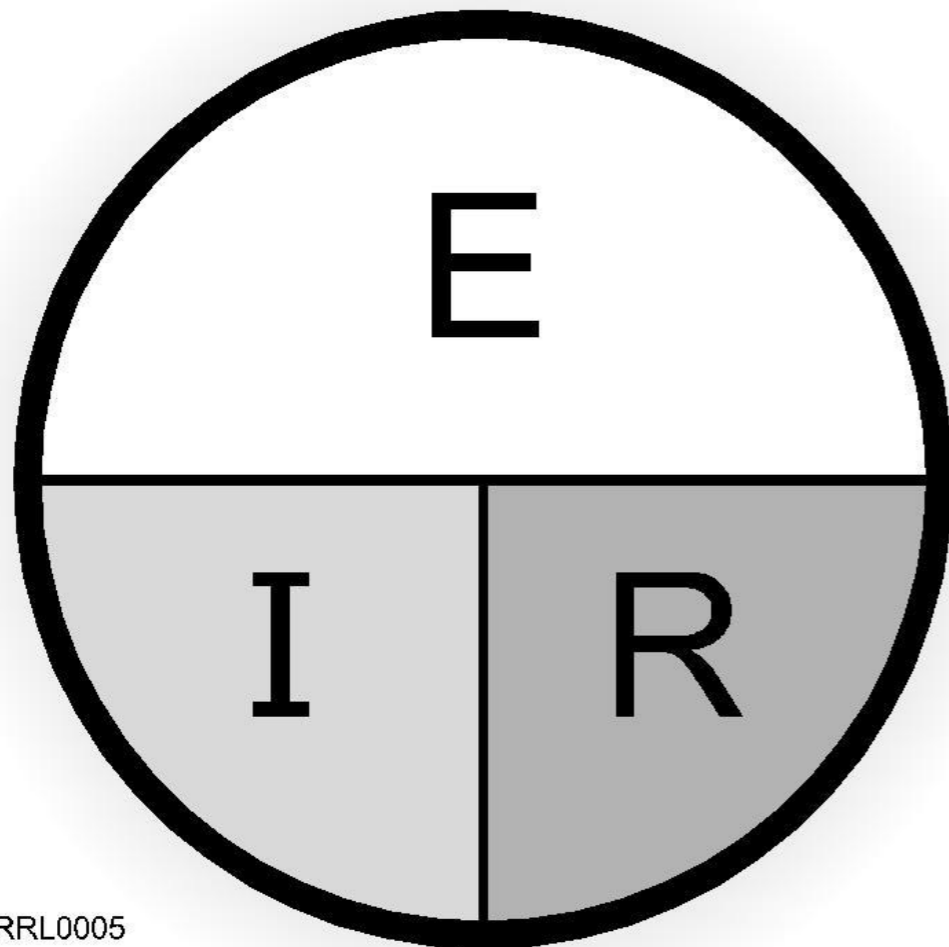


ARRL0005

- $R = E / I$
- $I = E / R$



## Ohm's Law

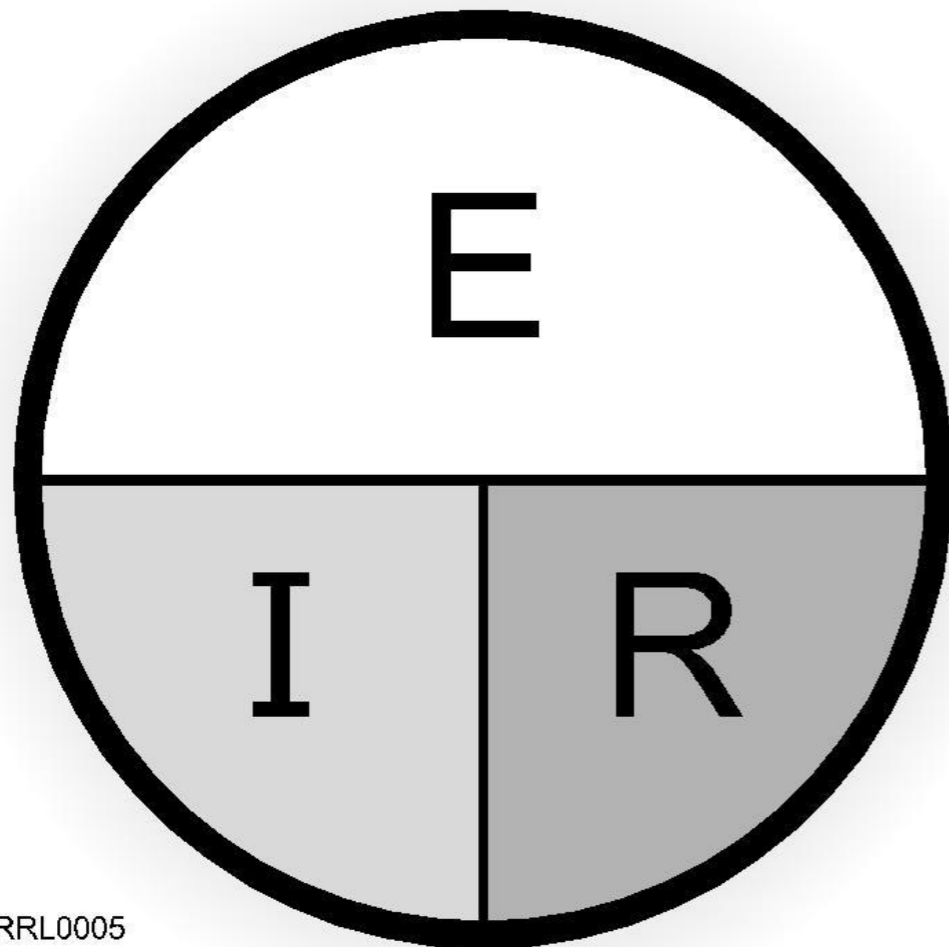

ARRL0005

•

$$R = E / I$$

$$I = E / R$$

$$E = I \times R$$



## Power - Electrons Doing Work and Expending Energy



## Power - Electrons Doing Work and Expending Energy

- Any time energy is expended, power is consumed.



## Power - Electrons Doing Work and Expending Energy

- Any time energy is expended, power is consumed.
- Electrons moving through resistance expend electrical energy and consume power.





## Power - Electrons Doing Work and Expending Energy

- Any time energy is expended, power is consumed.
- Electrons moving through resistance expend electrical energy and consume power.
- Power is the rate at which energy is consumed.



## Power - Electrons Doing Work and Expending Energy

- Any time energy is expended, power is consumed.
- Electrons moving through resistance expend electrical energy and consume power.
- Power is the rate at which energy is consumed.
- Power is measured in units of watts (W).



## Power Equation




## Power Equation

- Power is calculated as the product of voltage and current


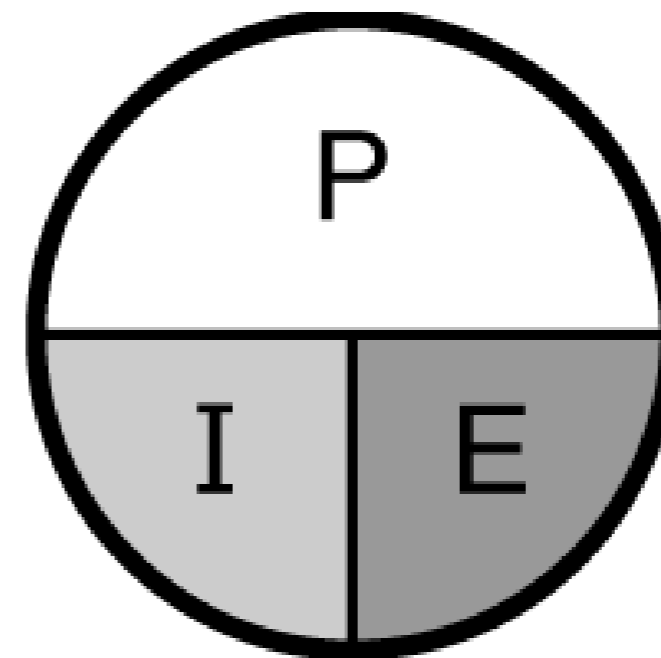
## Power Equation

- Power is calculated as the product of voltage and current






## Power Equation

- Power is calculated as the product of voltage and current

$$P = E \times I$$

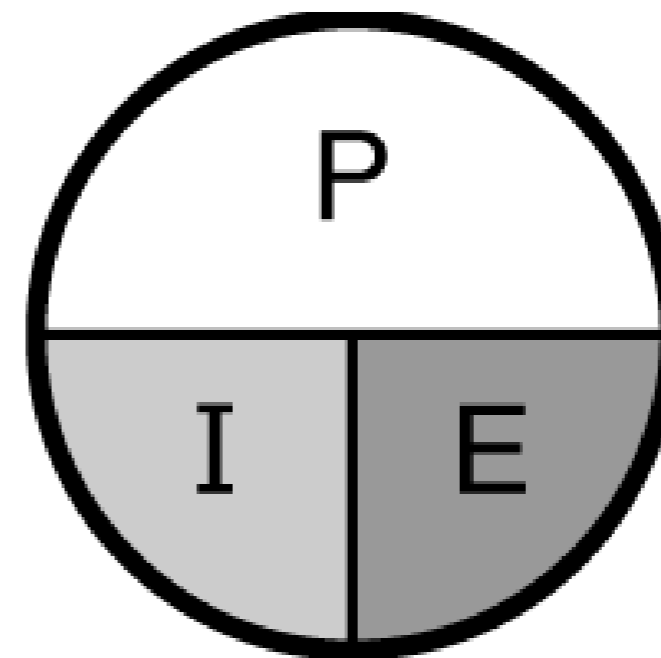




## Power Equation

- Power is calculated as the product of voltage and current

$$P = E \times I$$

$$E = P / I$$

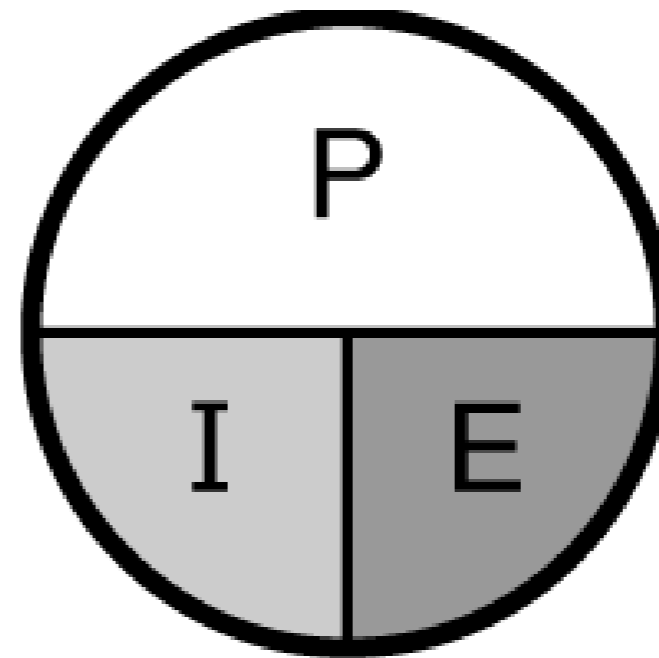




## Power Equation

- Power is calculated as the product of voltage and current

$$P = E \times I$$

$$E = P / I$$

$$I = P / E$$

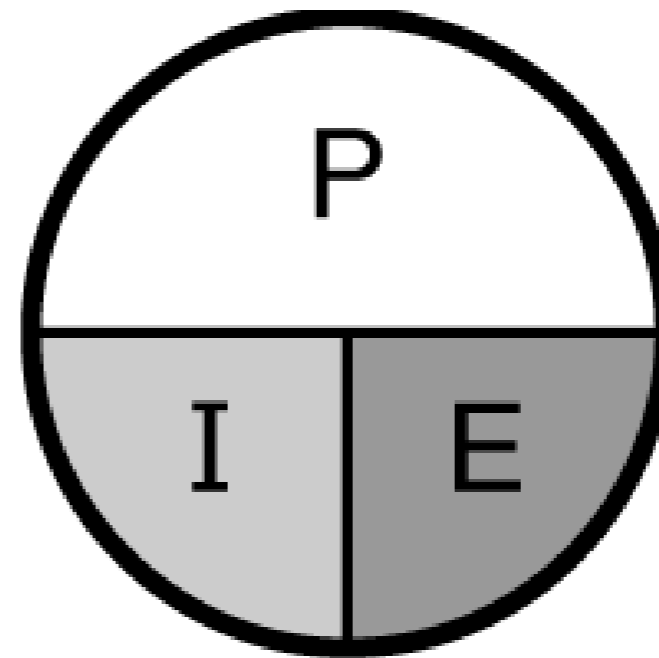






## Power Equation

- Power is calculated as the product of voltage and current

$$P = E \times I$$

$$E = P / I$$

$$I = P / E$$

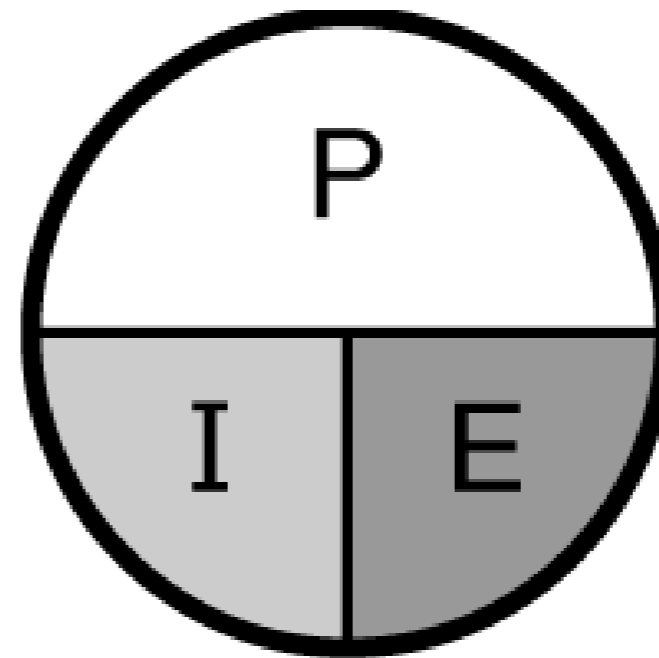

- Like Ohm's Law, if you know two of the values, you can calculate the third.

# Ham Radio License Course

Discovering the Excitement of Ham Radio



**ARRL** The national association for  
AMATEUR RADIO®

# Are there any questions?