



## 3. ELECTRICITY, COMPONENTS and CIRCUITS

### Chapter 3 Part 2 of 3

### Components and Units





# Controlling flow of current

We use various **components** to control the flow of current

Resistors


Capacitors

Inductors

Diodes

Transistors

Integrated circuits

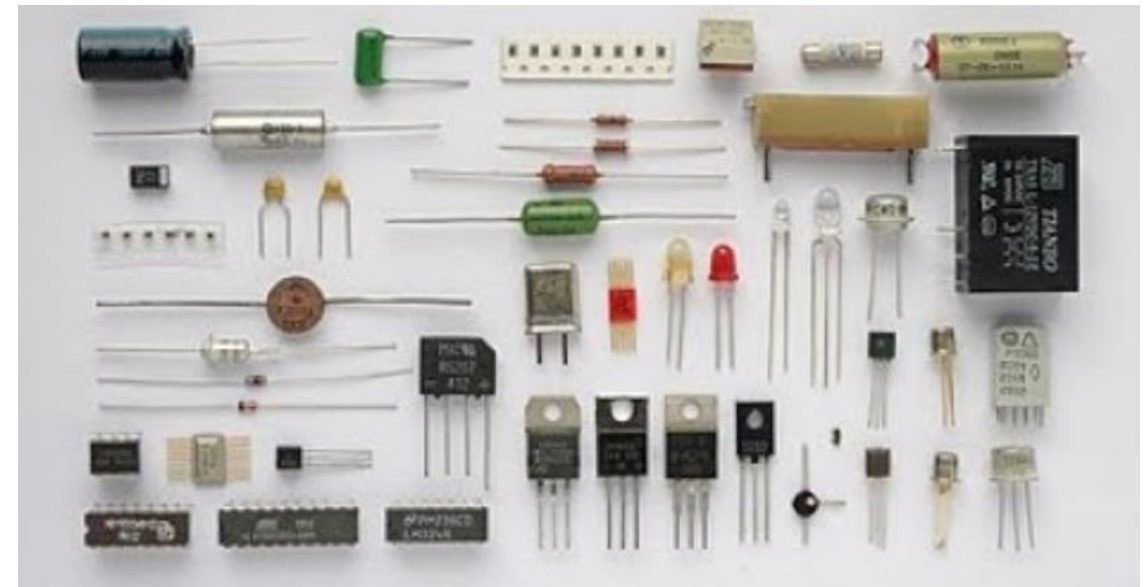



Switches, Relays, Transformers, LED's, Displays, Lightbulbs,  
Speakers, Fuses, Sensors, Connectors, Cables.....


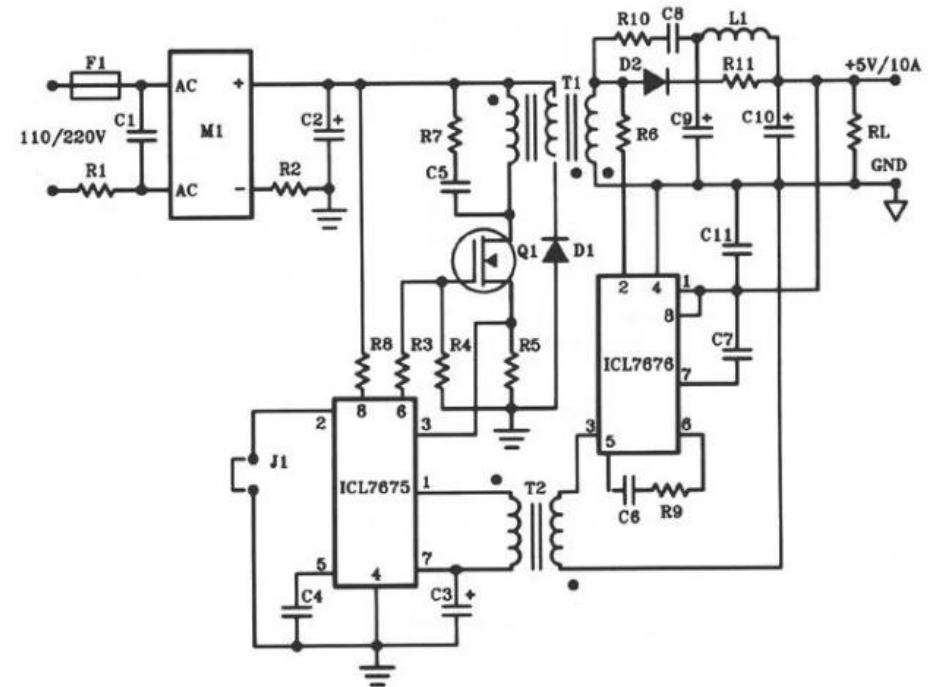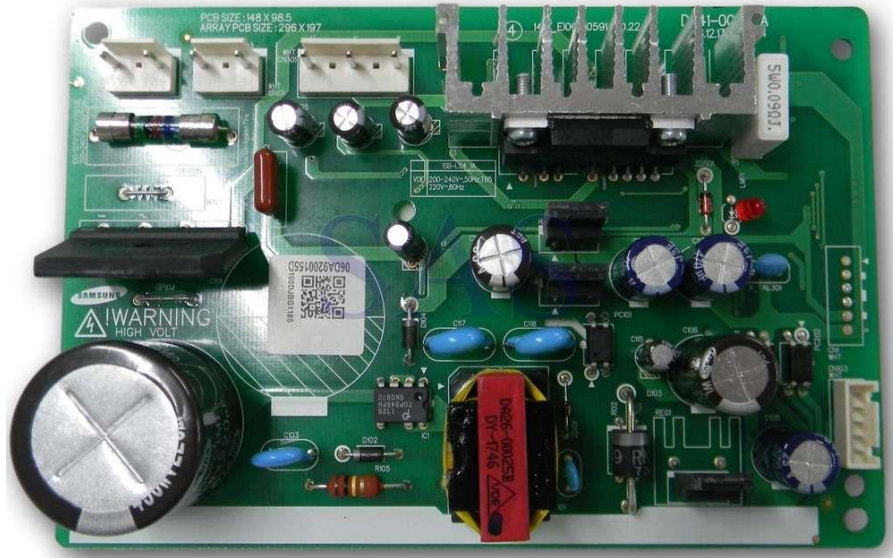
# Schematic diagram

A schematic diagram shows how the parts are connected, but not necessarily the location of the parts

This makes it easier to understand the function of the circuit






# Schematic symbols

The lines and dots on the schematic represent connections between the components

The schematic uses standardized symbols for the various components

The parts are given designators, like 'R3' to denote what the component is, commonly:

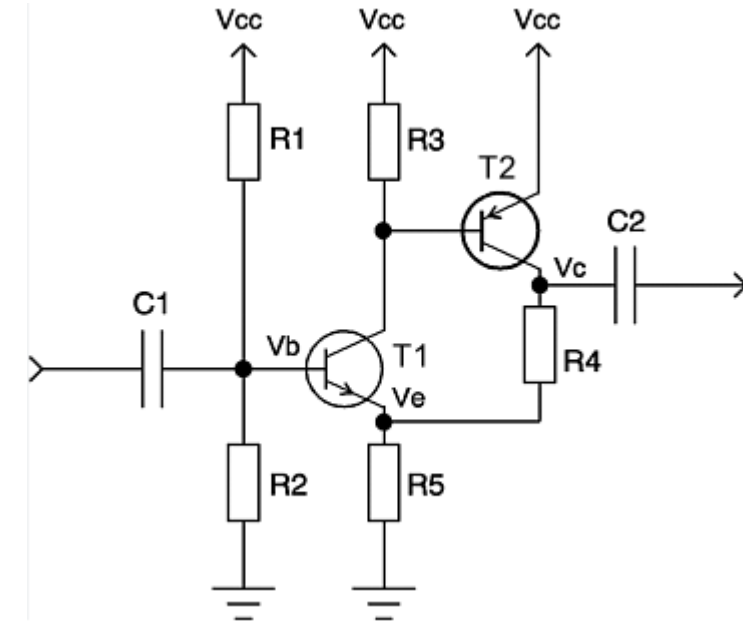- R : resistors
- C : capacitors
- L : inductors
- T : transistors
- D : diodes
- IC : integrated circuits
- J : jumpers / connectors





# Resistor

Resistors restrict the flow of current

It has a value measured in **Ohm ( $\Omega$ )**, called **resistance**

Schematic symbol:






# Variable Resistor, Potentiometer

Used to adjust the resistance

For example, a volume control

Schematic symbol:

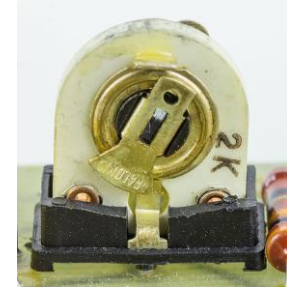



# Capacitor



Capacitors store electric energy in an **electric** field

It has a value measured in **Farad (F)**, called **capacitance**

Schematic symbol:



Also variable:

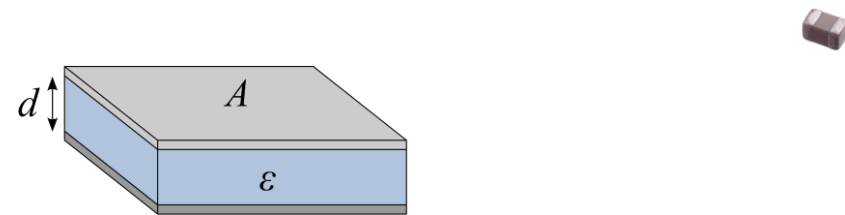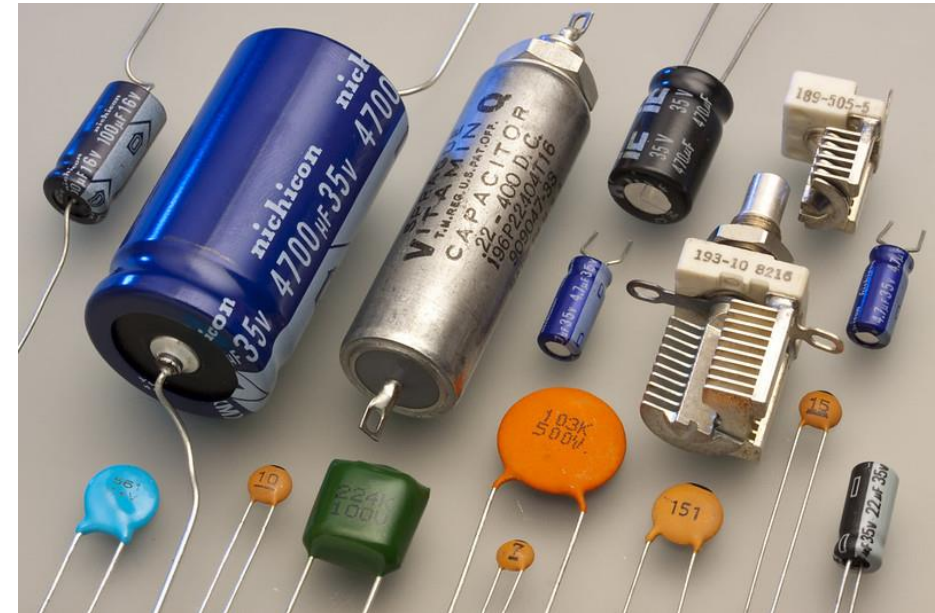



# Inductor

Inductors store electric energy in a **magnetic** field

It has a value measured in **Henry (H)**, called **inductance**

Schematic symbol: 

Also variable/core: 







# Unit recap

Passive component's values covers wide ranges

Resistors: $\Omega$ (Ohm, resistance)	0 $\Omega$ – 10,000,000 $\Omega$
Capacitors: F (Farad, capacitance)	0.000,000,000,001 F – 0.01 F
Inductors: H (Henry, inductance)	0.000,000,000,1 H – 0.1 H

**Prefixes** makes handling wide ranges of numbers much easier



# Prefixes

Prefix	Symbol	Multiplier		Common name
Tera	T	$\times 10^{12}$	$\times 1\,000\,000\,000\,000$	trillion
Giga	G	$\times 10^9$	$\times 1\,000\,000\,000$	billion
Mega	M	$\times 10^6$	$\times 1\,000\,000$	million
Kilo	k	$\times 10^3$	$\times 1\,000$	thousand
Deci	d	$\times 10^{-1}$	$\times 0.1$	tenth
Centi	c	$\times 10^{-2}$	$\times 0.01$	hundredth
Milli	m	$\times 10^{-3}$	$\times 0.001$	thousandth
Micro	$\mu$	$\times 10^{-6}$	$\times 0.000\,001$	millionth
Nano	n	$\times 10^{-9}$	$\times 0.000\,000\,001$	billionth
Pico	p	$\times 10^{-12}$	$\times 0.000\,000\,000\,001$	trillionth



# Reactance

Resistors oppose the flow of electrons (current)

- Independent of direction and frequency

Capacitors and Inductors store energy and also oppose the current, but behaves different depending on frequency

Capacitors create **capacitive reactance ( $X_C$ )**

- Decreases with increasing frequency

Inductors create **inductive reactance ( $X_L$ )**

- Increases with increasing frequency

Reactance is measured in Ohm ( $\Omega$ )




# Impedance

Any real component has ALL of:

- Resistance
- Capacitance
- Inductance

The combination of these is called **Impedance** (Z).

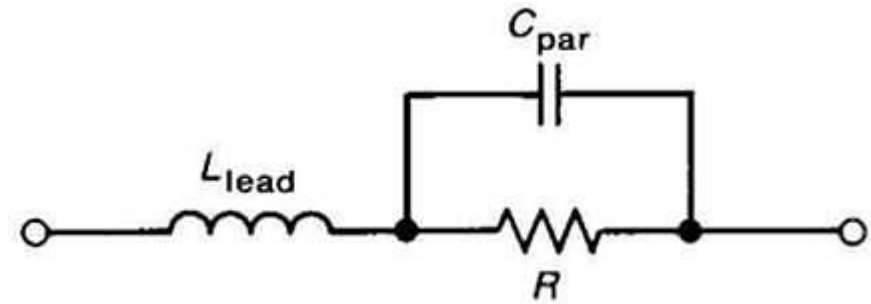..and is also measured in Ohm ( $\Omega$ )






# Resonance

This circuit has both capacitive and inductive reactance


This is called a **tuned circuit**

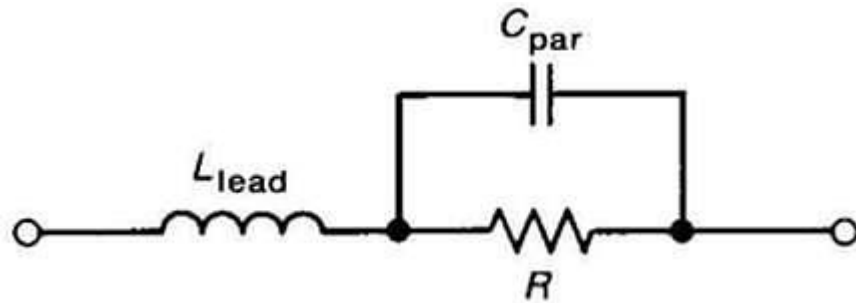

$X_C$  decrease as the frequency increase

$X_L$  increase as the frequency increase

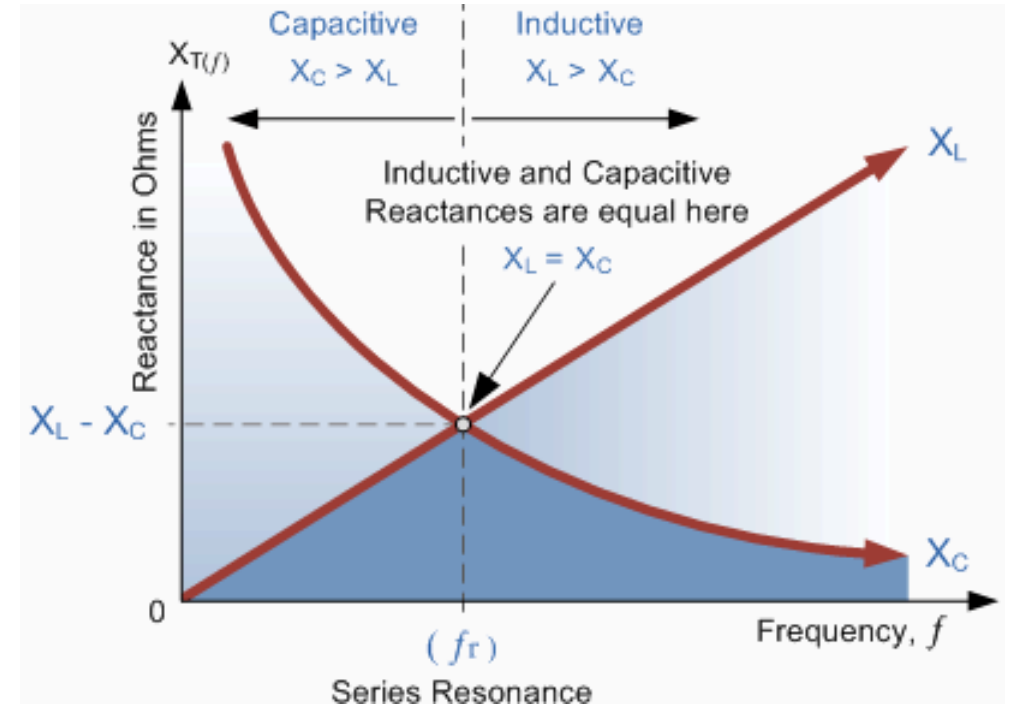The point where  **$X_C = X_L$**  is called **resonance**






# More components : Semiconductors

Most commonly made of **silicon** or **germanium**

By adding “impurities”, current flow can be controlled

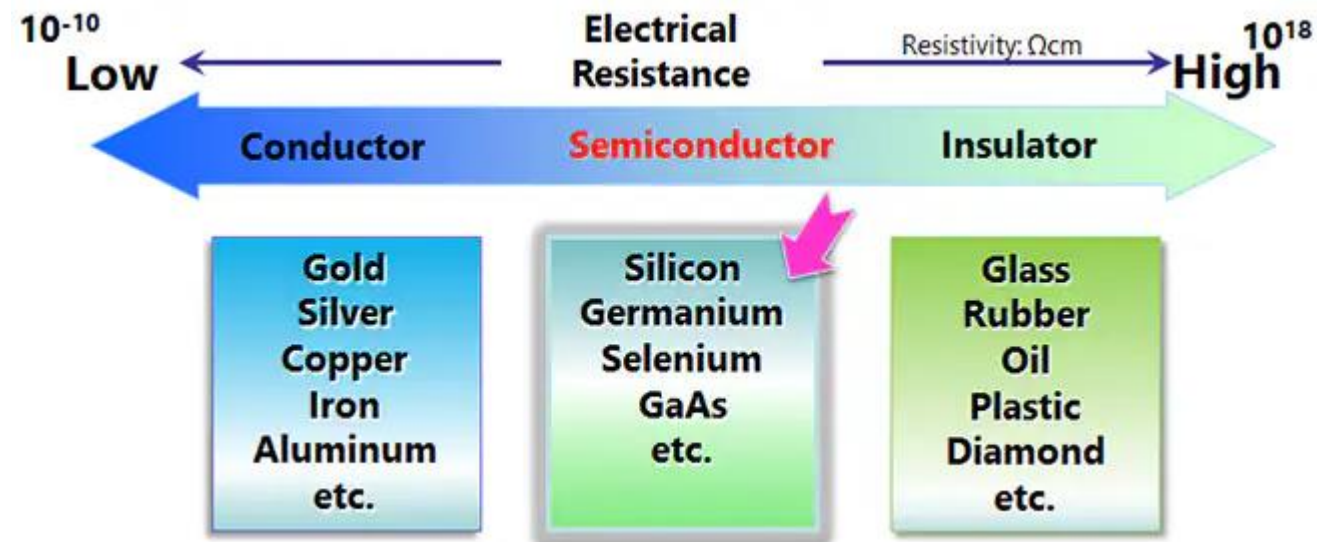‘P’ and ‘N’ material has more or less electrons than usual





# Diode



Only conducts in one direction\*

Current flows from the Anode to the Cathode, but not in the other direction

Used to **rectify** AC into DC

When current flows, there's a small voltage over the diode, called **forward voltage drop**.

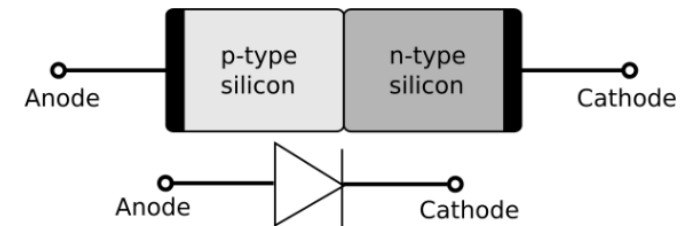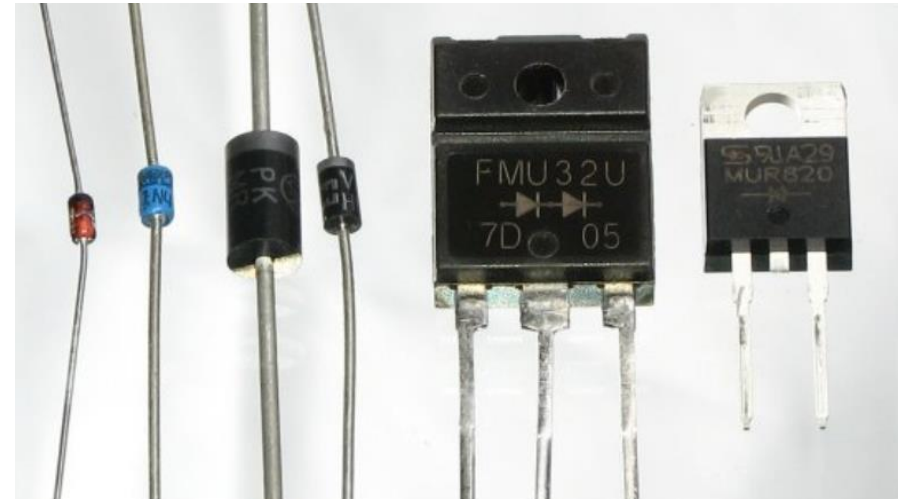Usually 1V or less depending on the diode and current.



\*) **Zener diodes** conduct in reverse direction, with a very specified voltage drop



# Light Emitting Diodes



Forward current cause electrons to jump between layers

The jump emits photons

Color depends on material

Used for indication and illumination

Small, efficient, fast, cheap

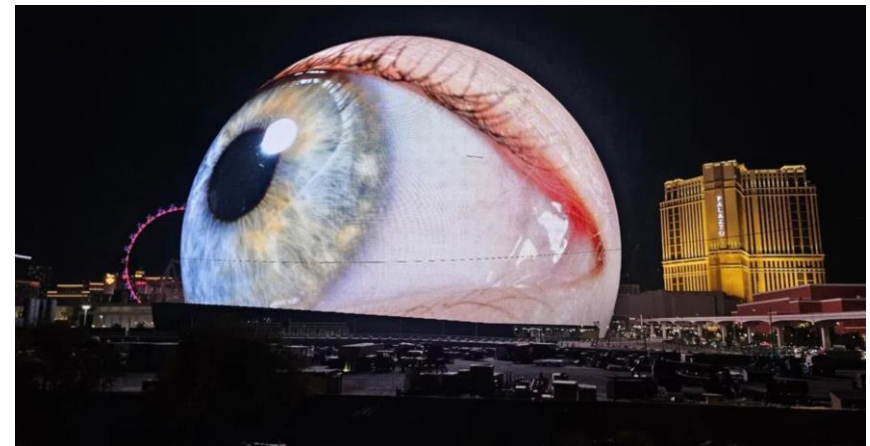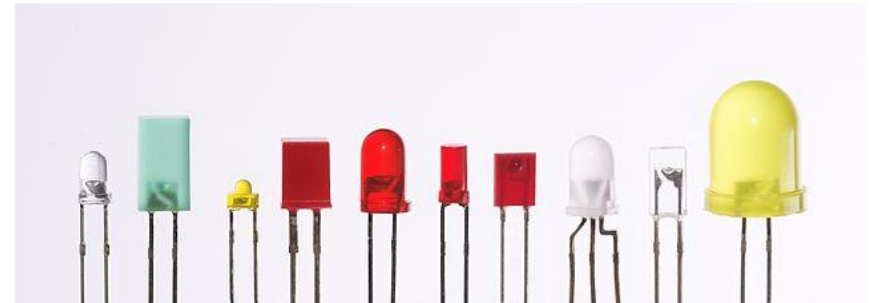





# Transistors

Controls a larger signal with a smaller signal.

Can be used as an **amplifier** or as a **switch**



The amount of amplification is called **gain**

## BJT's

- **Three** layers: N-P-N or P-N-P
- **Collector, Base, Emitter**
- Controlled by current
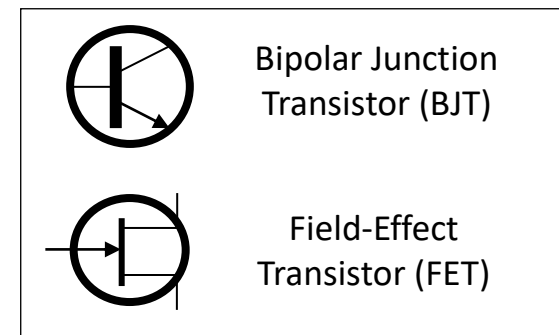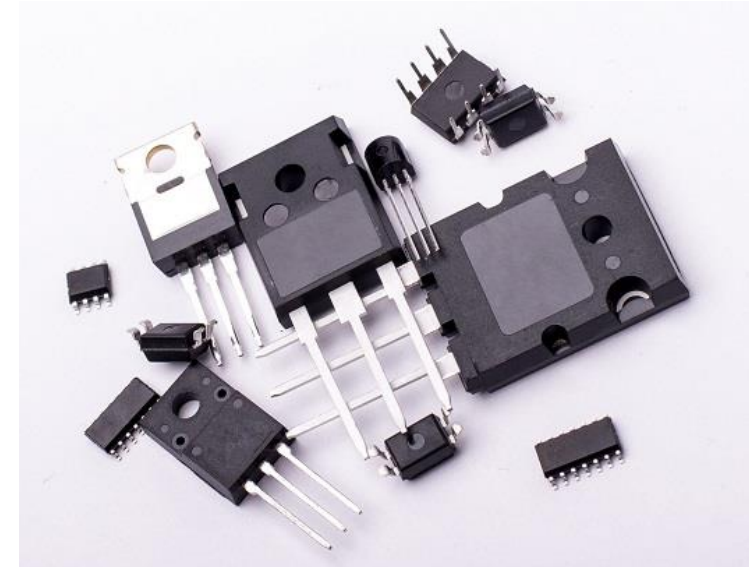
## FET's

- Path of N or P material
- **Source, Gate, Drain**
- Controlled by voltage






# Integrated circuits

Multiple components on a very small silicon plate

Wires bonded out to pins or pads

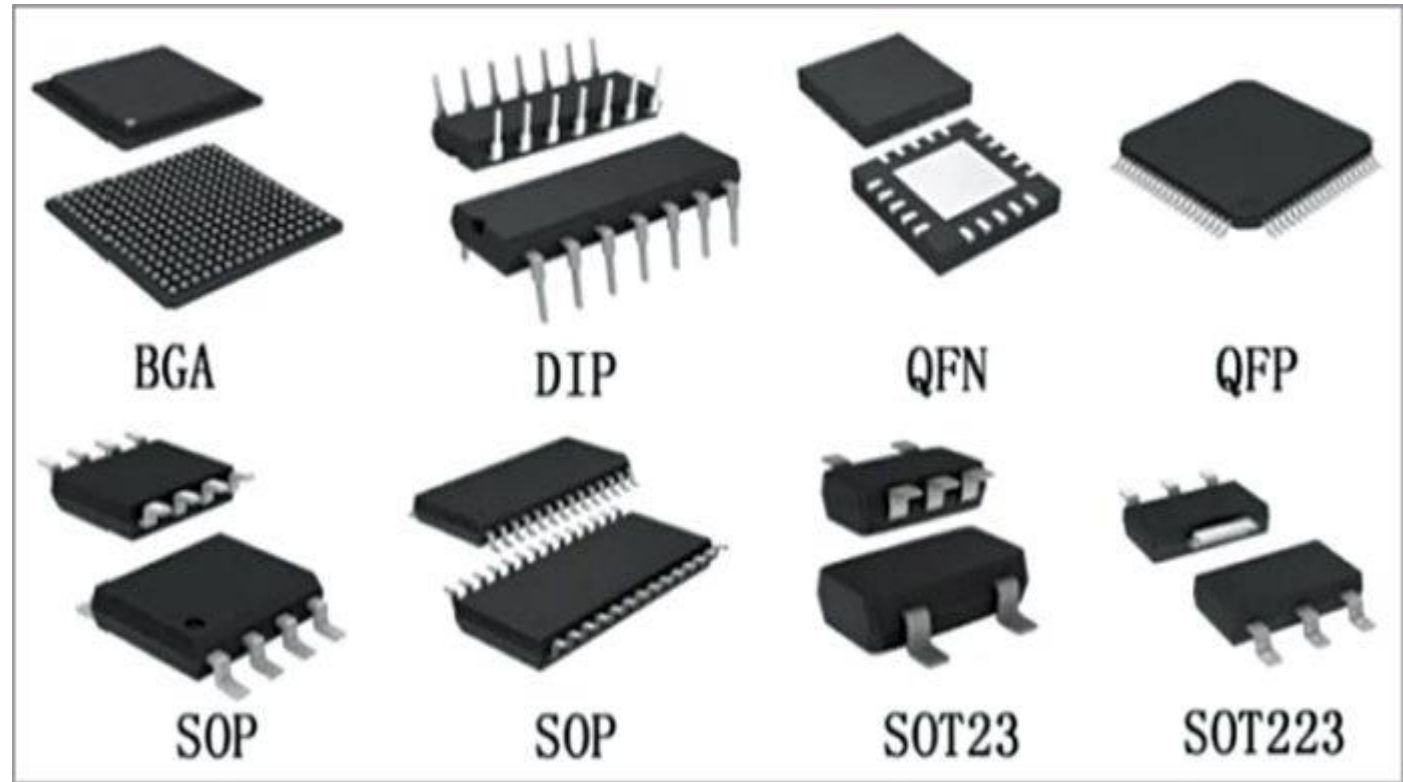Can have both analog and digital functions





# Transformers

Two (or more) inductors

Sharing a core – so sharing the magnetic field



Allows transfer of energy (constant power)

Schematic symbol:





Isolates and translate voltage and current

For example 120VAC to 12VAC

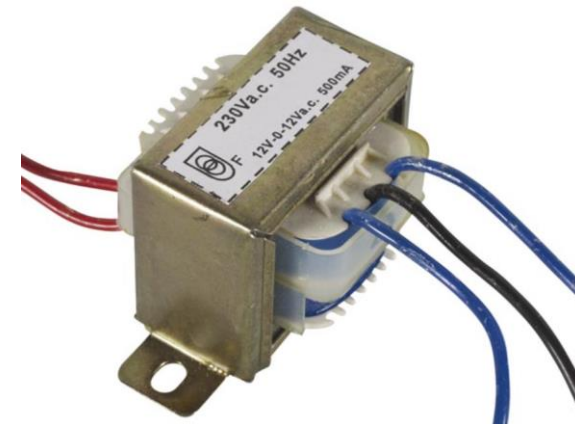
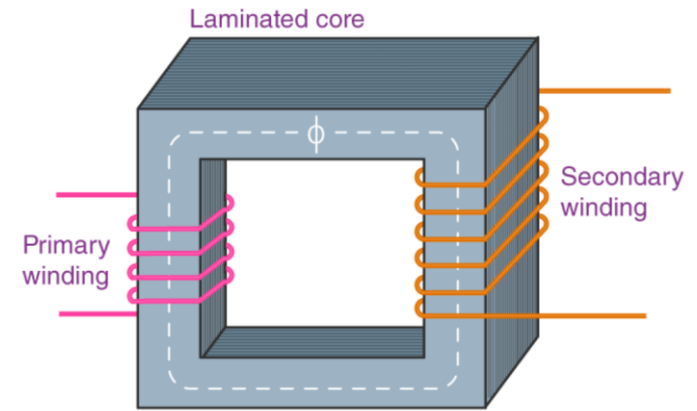


# Electromechanics

## Switches

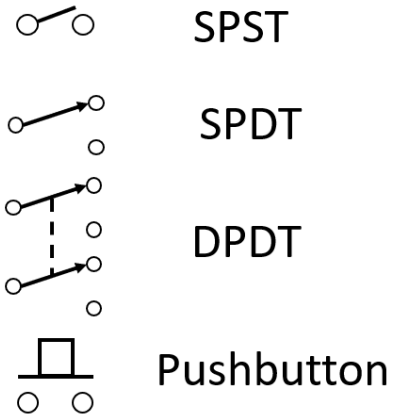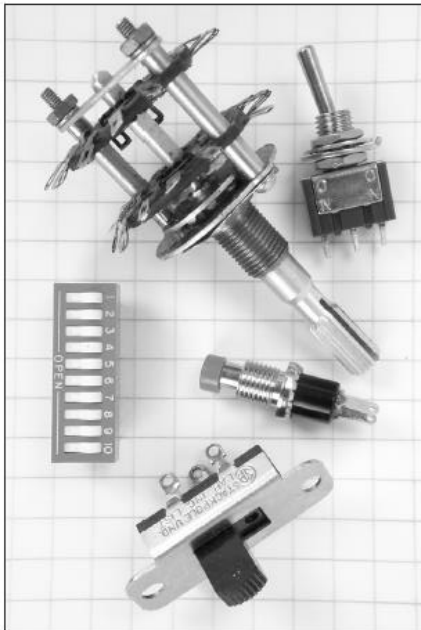

## Relays

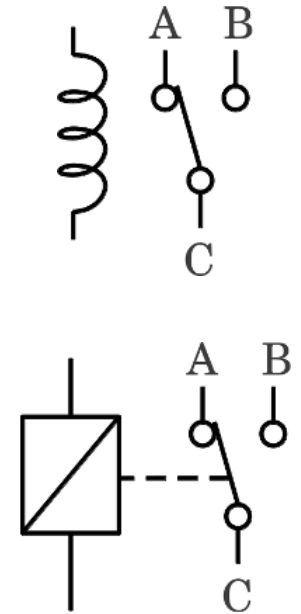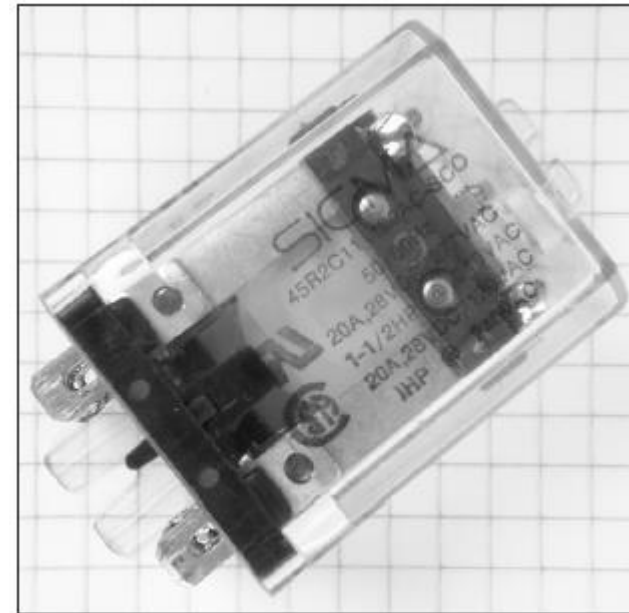




# Protective components


## Fuses

- Blow : one time protection

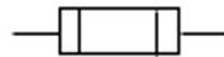

Fuses

Circuit  
Breaker

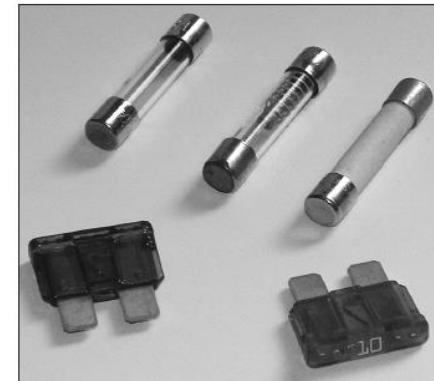

## Circuit breakers

- Trip : can be reset and reused

Protects a circuit from overload (too much current)

Replacing a fuse/breaker with one with a higher current rating may allow a fault to permanently damage the circuit or cause a hazard/fire.





Questions!