



Technician License Course

Chapter 3

Section 3.2 – Components and Units



Electronics – Controlling the Flow of Current

- To make an electronic device (like a radio) do something useful (like a receiver), we need to control and manipulate the flow of current.



Electronics – Controlling the Flow of Current

- To make an electronic device (like a radio) and do something useful (like a receiver), we need to control and manipulate the flow of current.
- There are several different electronic components that are used to do this



Schematic Diagrams

- We can draw pictures of electronic components forming circuits, such as for the parallel and series circuit examples. This is too cumbersome for most circuits.




Schematic Diagrams

- We can draw pictures of electronic components forming circuits, such as for the parallel and series circuit examples. This is too cumbersome for most circuits.
- Schematic diagrams use symbols with different components, each having a different symbol.



Schematic Diagrams

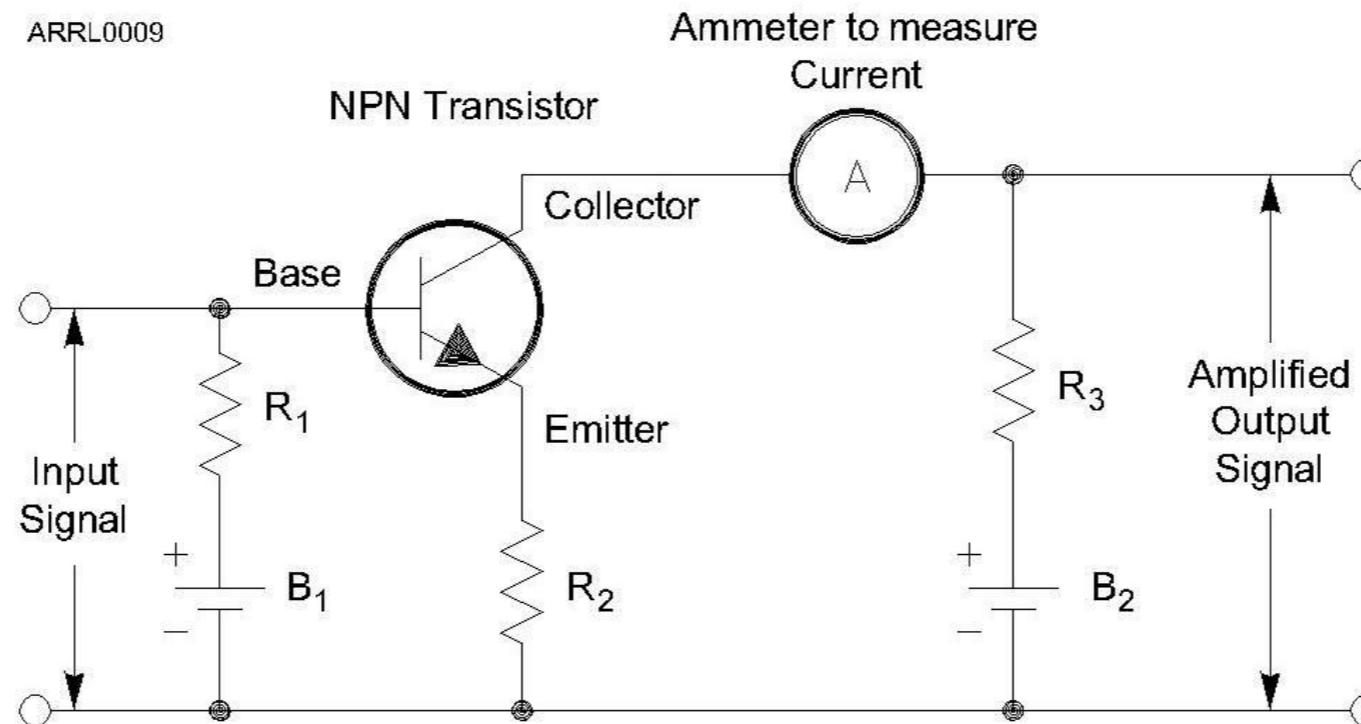


The lines and dots on schematics represent electrical connections between the components.



Component Designators

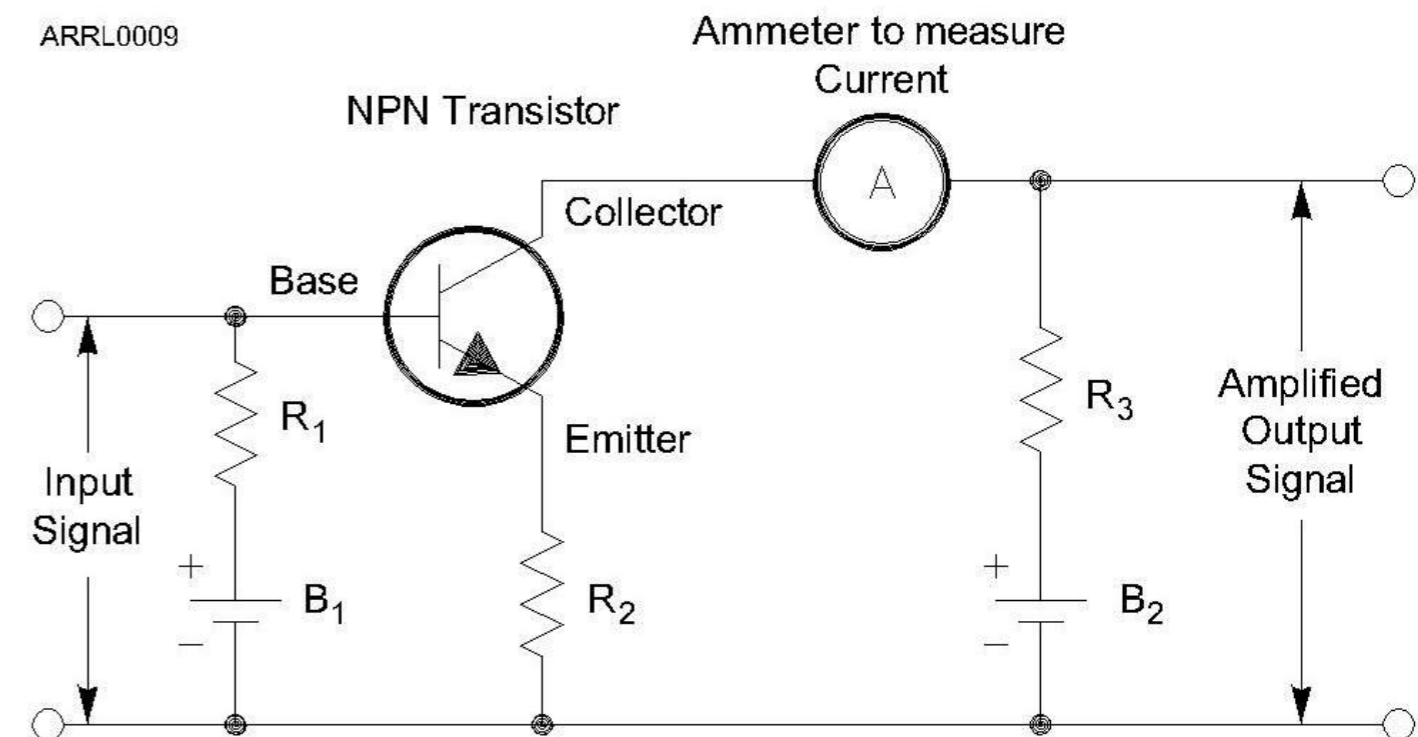- Each schematic symbol has a *designator* to denote which component it refers to. For example, the 10th resistor in a circuit is R10.
- Resistors (R), capacitors (C), inductors (L).





The Resistor




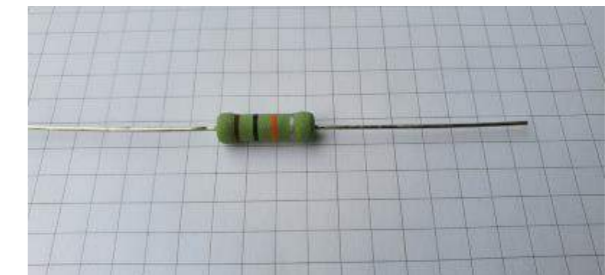
The Resistor

- The function of a resistor is to restrict the flow of current.
- Schematic symbol
- Remember Ohm's Law:
$$I = E / R$$
$$E = I \times R$$



The Resistor

- The function of a resistor is to restrict the flow of current.
- Schematic symbol 
- Remember Ohm's Law:
$$I = E / R$$
$$E = I \times R$$



© YoktoBit (via Wikimedia Commons)



© YoktoBit (via Wikimedia Commons)



© oomlout (via Wikimedia Commons)




The Variable Resistor

- A resistor that you can change the value of.




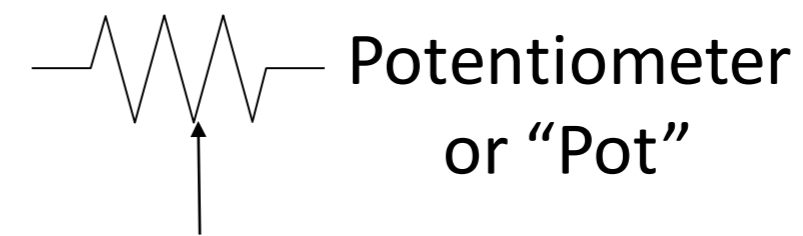
© Raimond Spekking / [CC BY-SA 4.0](https://creativecommons.org/licenses/by-sa/4.0/) (via Wikimedia Commons)



Arrow indicates adjustable value, such as for a volume control.




The Capacitor

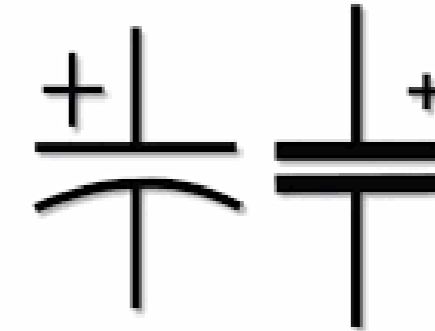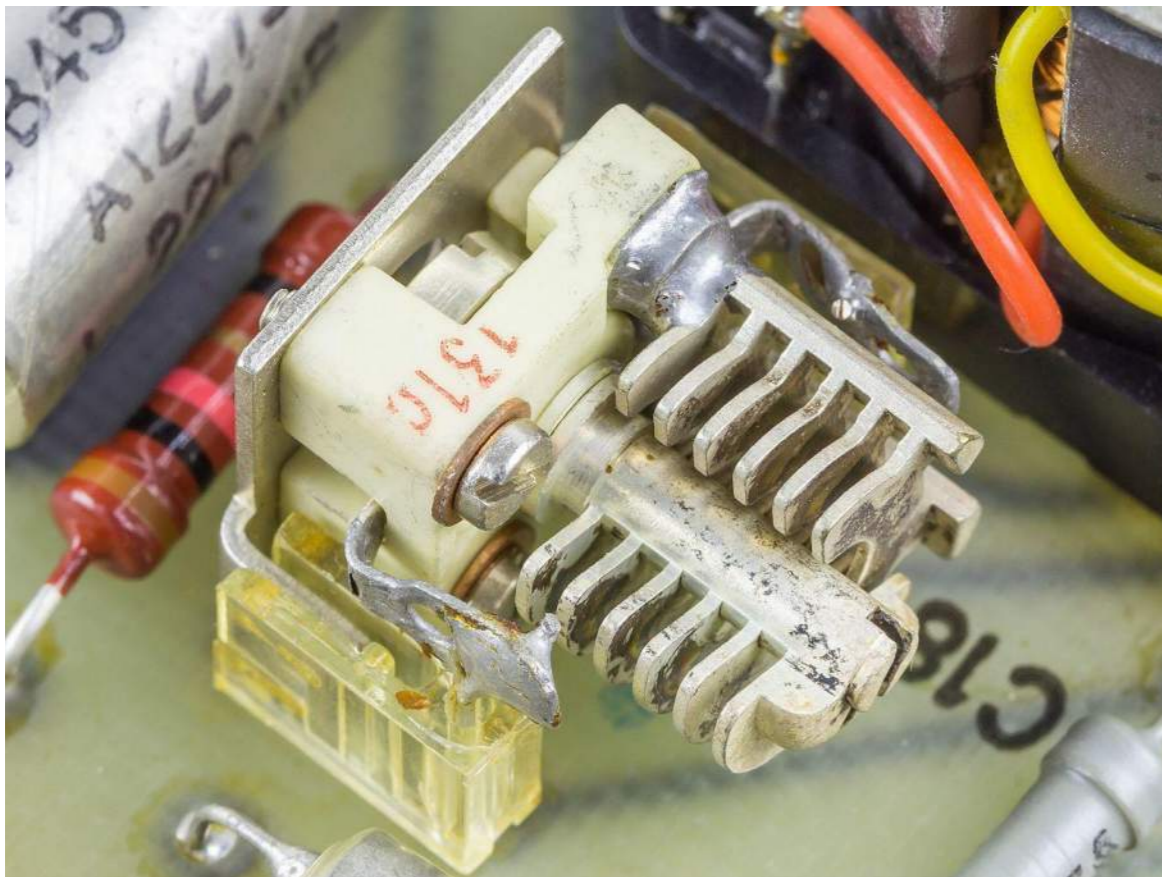



The Capacitor

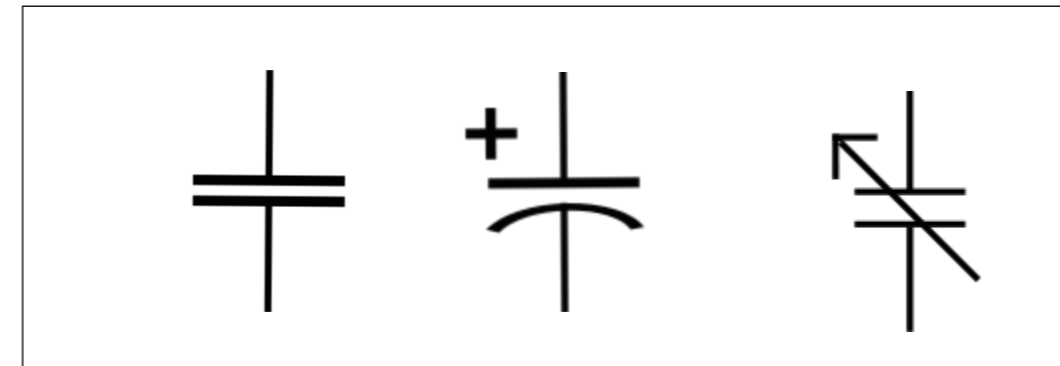
- The function of a capacitor is to store electrical energy – called *capacitance*.
- Schematic symbols





The Capacitor

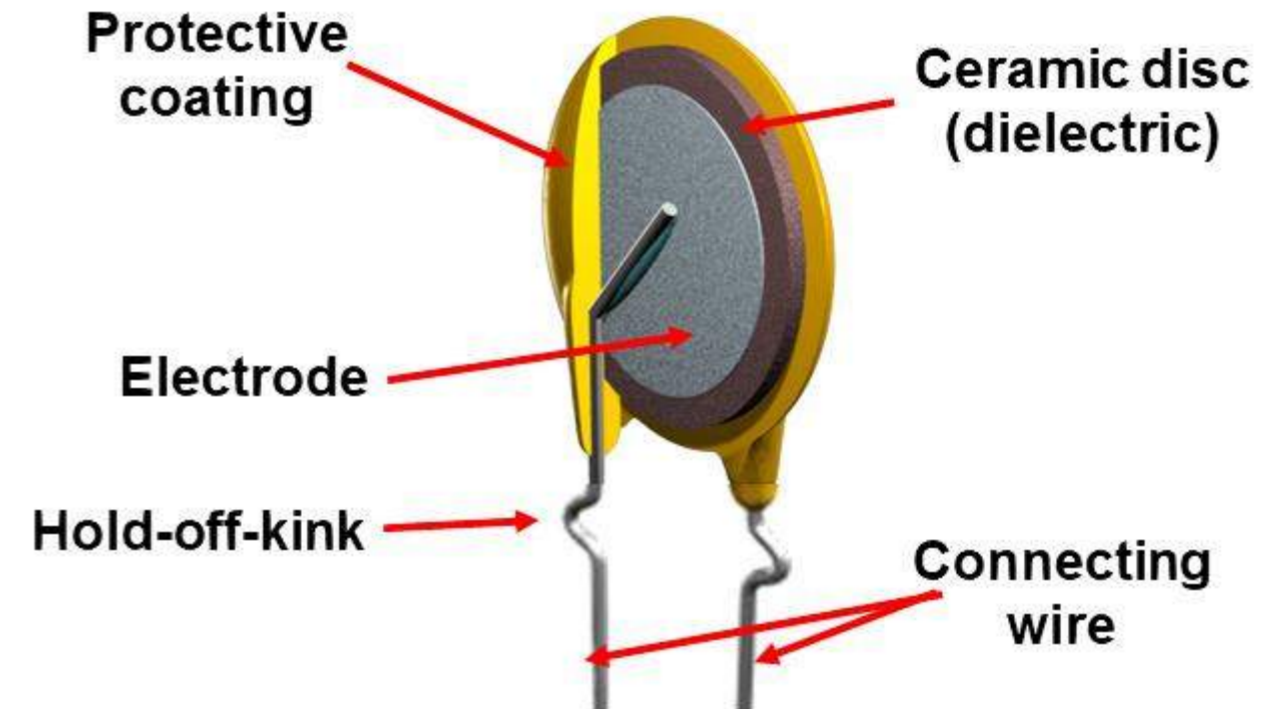
- The function of a capacitor is to store electrical energy – called *capacitance*.
- Schematic symbol
Acts like a battery





The Capacitor

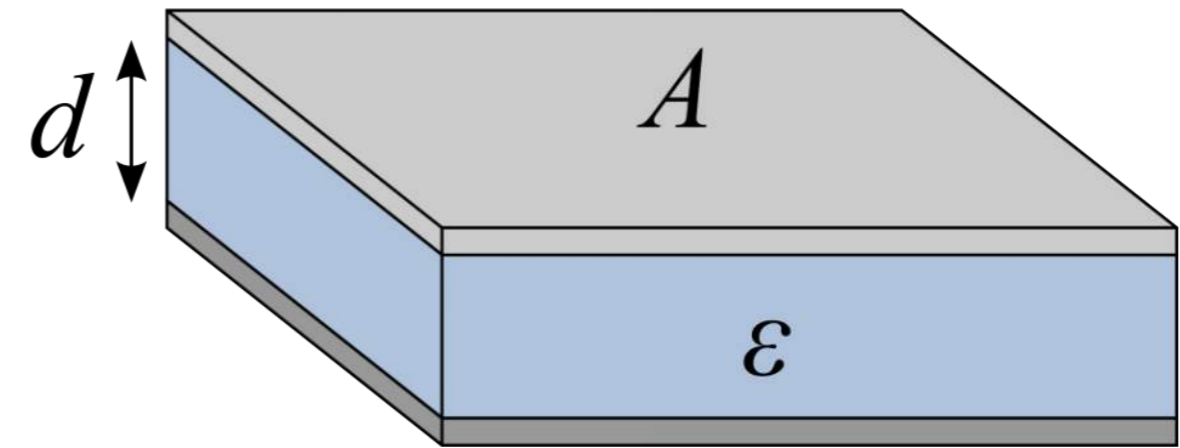- The function of a capacitor is to store electrical energy – called *capacitance*.
- Schematic symbol
 - Acts like a battery
 - Stores energy in an electric field created by voltage between the electrodes
- material between them



with insulating



The Inductor


- Schematic symbol



© Adriusa (via Wikimedia Commons)



© Jx (via Wikimedia Commons)

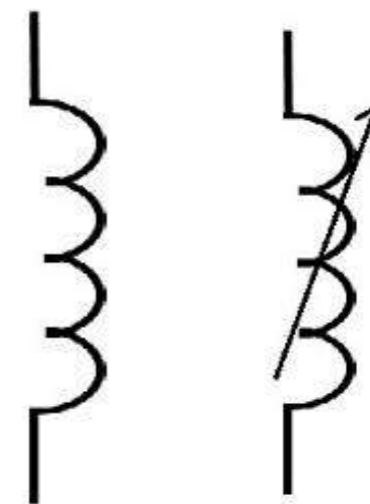



The Inductor

- The function of an inductor is to store magnetic energy – called *inductance*.



The Inductor

- The function of an inductor is to store magnetic energy – called *inductance*.
- A coil of wire around a *core* of air or magnetic material like iron or ferrite




The Inductor

- The function of an inductor is to store magnetic energy – called *inductance*.
- A coil of wire around a *core* of air or magnetic material like iron or ferrite
- Stores energy in a magnetic field created by current in the wire




The Transformer

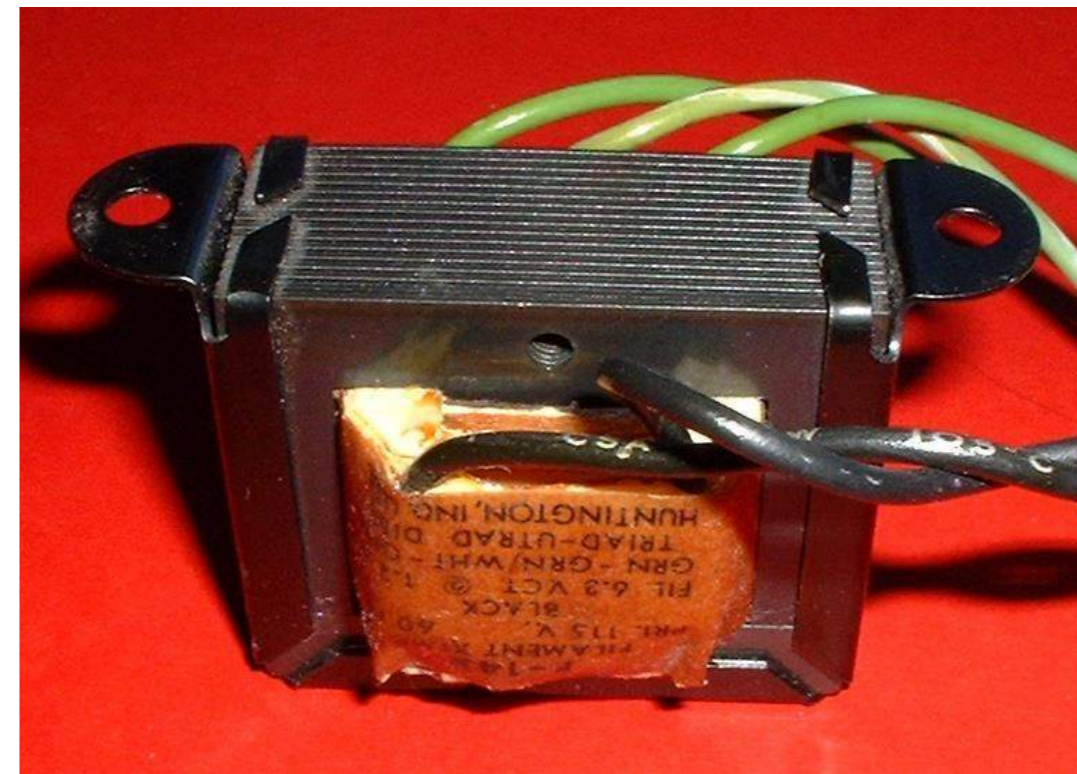




The Transformer

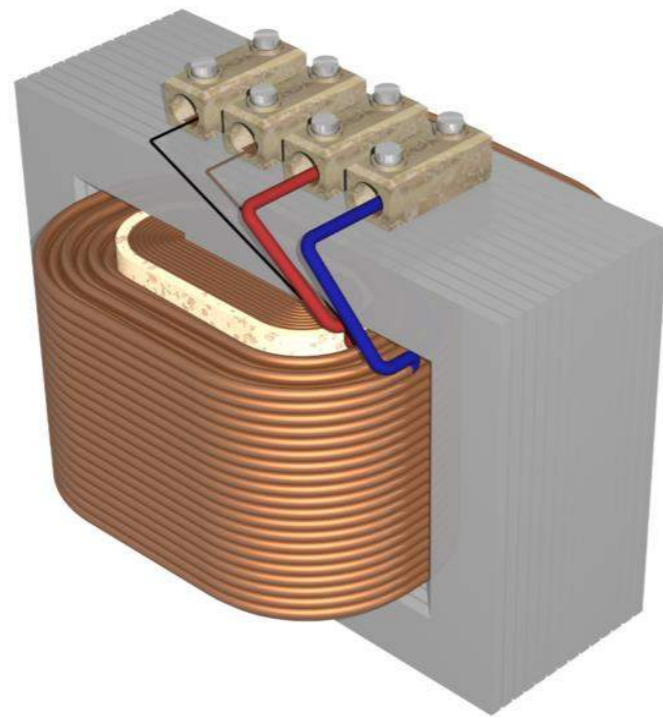- A pair of inductors sharing a common core



© Mtdorov (via Wikimedia Commons)

- Schematic symbol

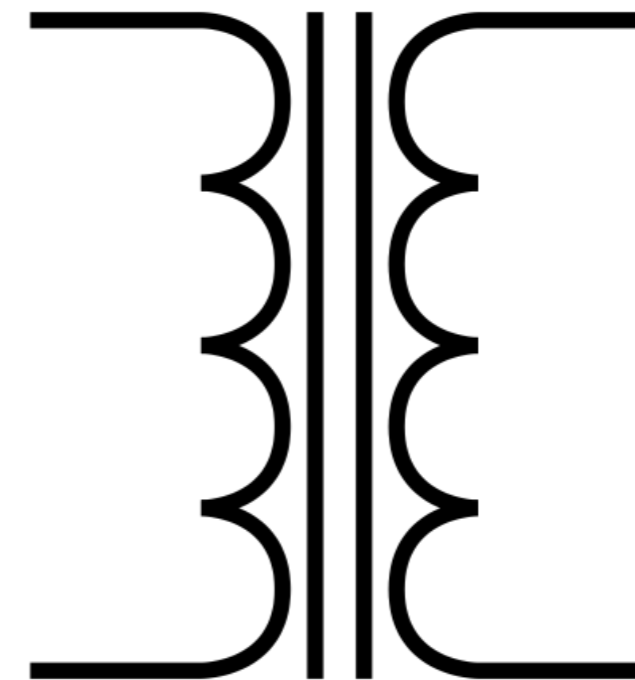




The Transformer

- A pair of inductors sharing a common core
- Also share their magnetic field

- Schematic symbol

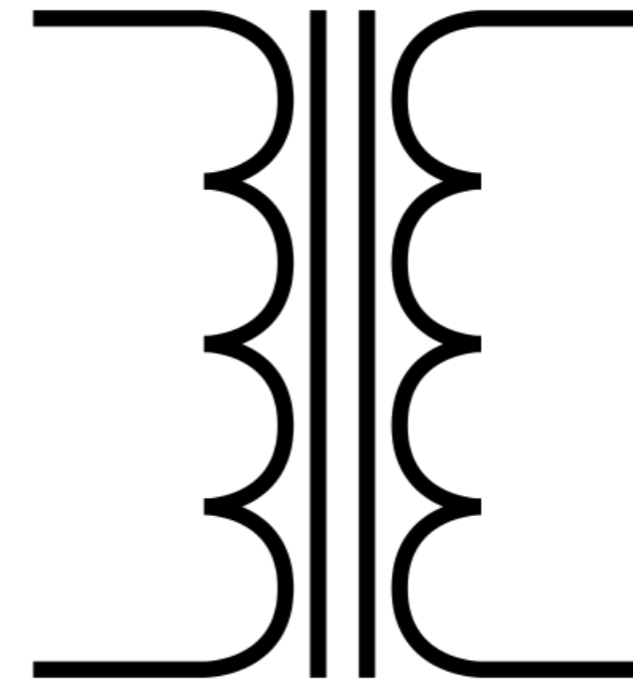




The Transformer

- A pair of inductors sharing a common core
- Also share their magnetic field
- Used to transfer energy from one circuit to another without a direct connection (isolation)
- Changes the ratio of voltage and current (step-up, step-down)

- Schematic symbol

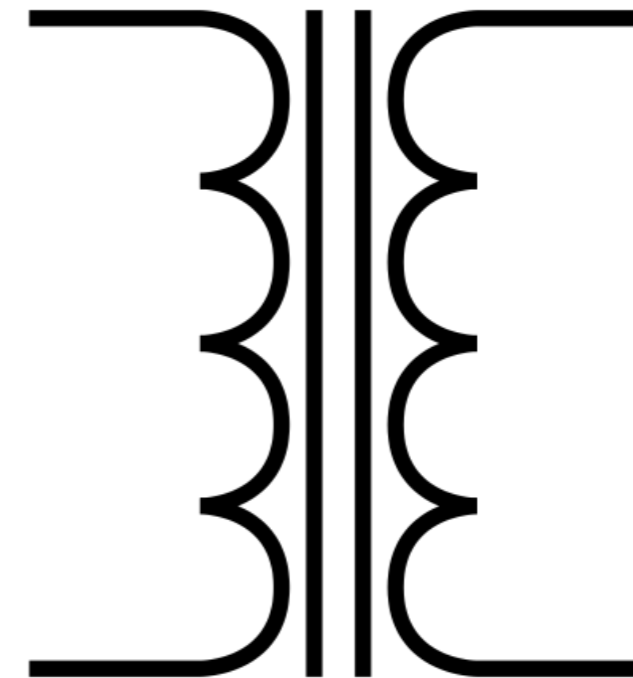



Electrical Units

- Each type of component has a value measured in specific units:
 - Resistors > resistance > ohms (Ω)
 - Capacitors > capacitance > farads (F)
 - Inductors > inductance > henrys (H)



Indicators and Displays



© Mister RF (via Wikimedia Commons)



© Mister RF (via Wikimedia Commons)



Indicators and Displays

- Indicators communicate status
 - ON/OFF, ready/stand-by, left/right
 - LEDs, light bulbs, symbols, audio tones
- Displays communicate values or text
 - Numeric values, warnings, messages
 - Digital and analog meters, LCD screens



Reactance



Reactance

- Capacitors and inductors store energy, rather than dissipating it like resistors.



Reactance

- Capacitors and inductors store energy, rather than dissipating it like resistors.
- Energy storage creates an effect called *reactance* (symbol X) that acts like a resistance in opposing the flow of ac current.



Reactance

- Capacitors and inductors store energy, rather than dissipating it like resistors.
- Energy storage creates an effect called *reactance* (symbol X) that acts like a resistance in opposing the flow of ac current.
 - Capacitors create *capacitive reactance* (X_C)



Reactance

- Capacitors and inductors store energy, rather than dissipating it like resistors.
- Energy storage creates an effect called *reactance* (symbol X) that acts like a resistance in opposing the flow of ac current.
 - Capacitors create *capacitive reactance* (X_C)
 - Inductors create *inductive reactance* (X_L)



Reactance

- Capacitors and inductors store energy, rather than dissipating it like resistors.
- Energy storage creates an effect called *reactance* (symbol X) that acts like a resistance in opposing the flow of ac current.
 - Capacitors create *capacitive reactance* (X_C)
 - Inductors create inductive reactance (X_L)
 - The effects of each are complementary



Impedance



Impedance

- The combination of resistance (R) and reactance (X) is called impedance, represented by the symbol Z .



Impedance

- The combination of resistance (R) and reactance (X) is called impedance, represented by the symbol Z .
- Impedance represents a circuit's opposition to both ac and dc currents.



Resonance



Resonance

- A component's reactance depends on frequency: X_L increases with frequency while X_C decreases.



Resonance

- A component's reactance depends on frequency: X_L increases with frequency while X_C decreases.
- At the frequency for which a circuit's X_L and X_C are equal, their effects cancel. This is the circuit's *resonant frequency*.




Resonance

- A component's reactance depends on frequency: X_L increases with frequency while X_C decreases.
- At the frequency for which a circuit's X_L and X_C are equal, their effects cancel. This is the circuit's *resonant frequency*.
- At *resonance*, a circuit has only resistance, which affects ac and dc current equally.



Resonant or Tuned Circuit

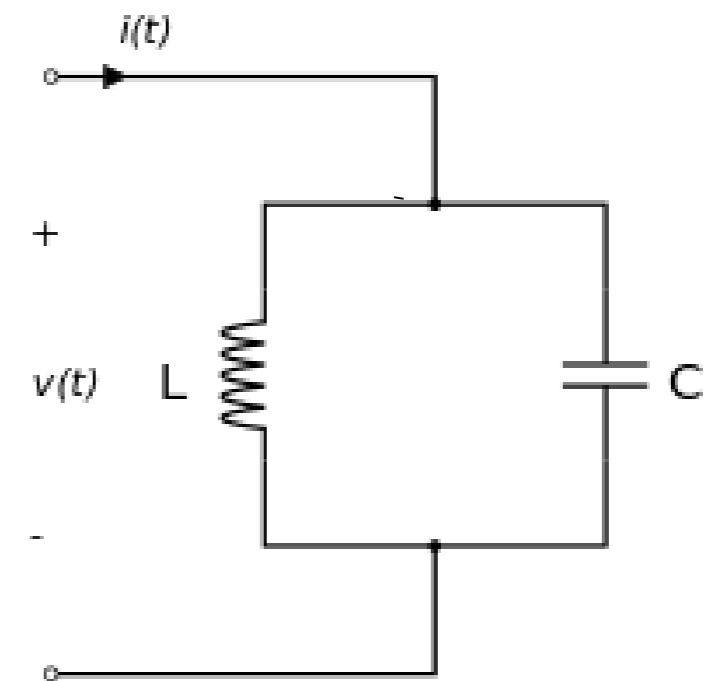- Capacitors and inductors connected together create a *tuned circuit*.
- When X_L and X_C are equal, the circuit is *resonant*.
- If C or L are adjustable the resonant frequency can be varied or tuned.





Semiconductor Components



Semiconductor Components

- Made of material like silicon that are “OK” conductors but not as good as metals.



Semiconductor Components


- Made of material like silicon that are “OK” conductors but not as good as metals.
- Impurities added to semiconductors create material with more than usual electrons (*N-type*) and fewer than usual (*P-type*) electrons.



Semiconductor Components

- Made of material like silicon that are “OK” conductors but not as good as metals.
- Impurities added to semiconductors create material with more than usual electrons (*N-type*) and fewer than usual (*P-type*) electrons.
- Structures of N and P material can control current flow through the semiconductor.

The Diode

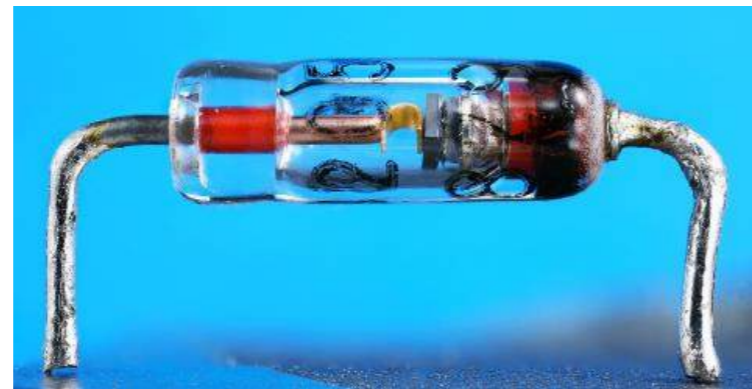


© Mister RF (via Wikimedia Commons)



© Raimond Spekking / [CC BY-SA 4.0](https://creativecommons.org/licenses/by-sa/4.0/) (via Wikimedia Commons)

- Schematic symbols

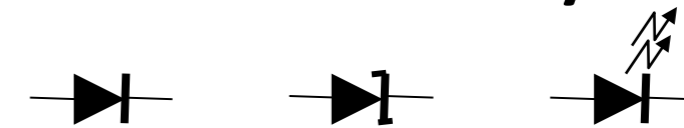


- Designator
- (D or CR)



The Diode

- Allows current to flow in only one direction.

- Schematic symbols

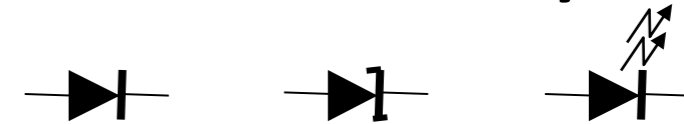


- Designator
- (D or CR)




The Diode

- Allows current to flow in only one direction.
 - Two electrodes: *anode* and *cathode*

- Schematic symbols

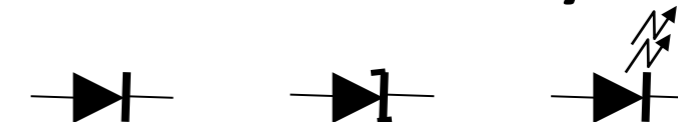

- Designator
- (D or CR)

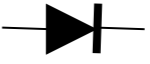
Anode  Cathode



The Diode


- Allows current to flow in only one direction.
 - Two electrodes: *anode* and *cathode*
 - AC current is changed to varying pulses of DC – called *rectification*

- Schematic symbols

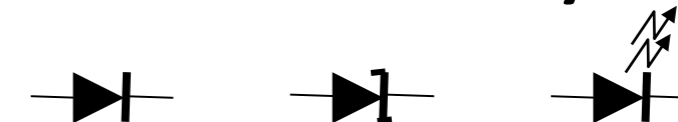

- Designator

- (D or CR)


Anode  Cathode



The Diode


- Allows current to flow in only one direction.
 - Two electrodes: *anode* and *cathode*
 - AC current is changed to varying pulses of DC – called *rectification*
 - Diodes used to change AC power to DC power are called *rectifiers*

- Schematic symbols

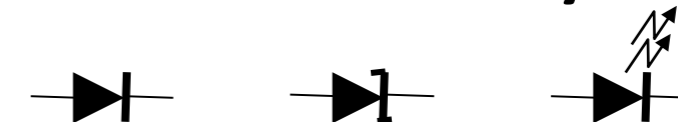

- Designator

- (D or CR)

Anode  Cathode




The Transistor



© Mister RF (via Wikimedia Commons)



© Mister RF (via Wikimedia Commons)

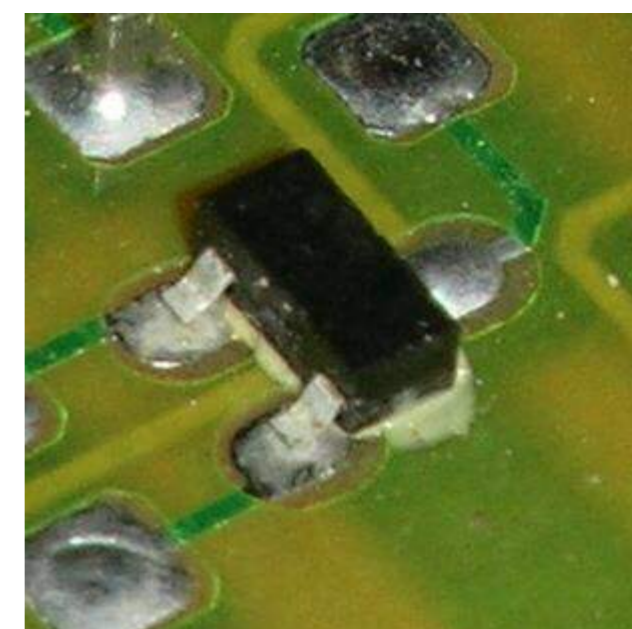

© Hutschi (via Wikimedia Commons)




The Transistor

- The function of a transistor is to control large signals with small ones.



The Transistor

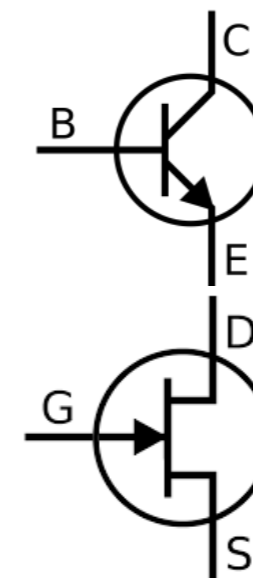- The function of a transistor is to control large signals with small ones.
- An “electronically controlled current valve”
- Schematic symbol
- Designator (Q)




Bipolar Junction
Transistor (BJT)

Field-Effect Transistor
(FET)



The Transistor

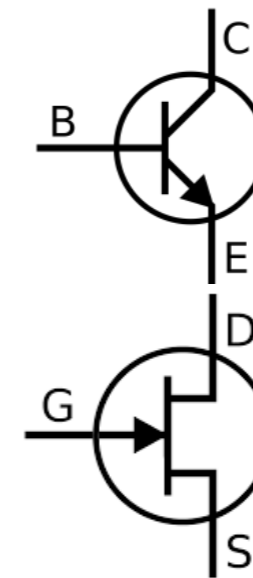- The function of a transistor is to control large signals with small ones.
- Schematic symbol
- Designator (Q)
- An “electronically controlled current valve”
- When used as an amplifier a transistor produces *gain*




Bipolar Junction
Transistor (BJT)


Field-Effect Transistor
(FET)

The Transistor

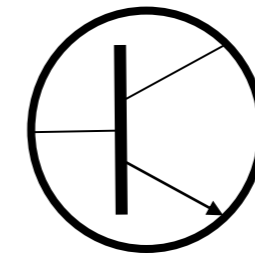- The function of a transistor is to control large signals with small ones.
 - An “electronically controlled current valve”
 - When used as an amplifier a transistor produces *gain*
 - Transistors can also be used as a switch
- Schematic symbol
- Designator (Q)



Bipolar Junction Transistor (BJT)

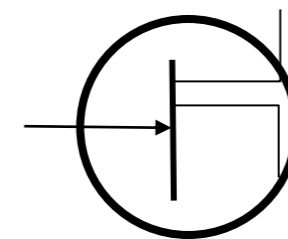

Field-Effect Transistor (FET)




The Transistor

- The Bipolar Junction Transistor (BJT) has three layers of N or P material connected to electrodes:



The Transistor

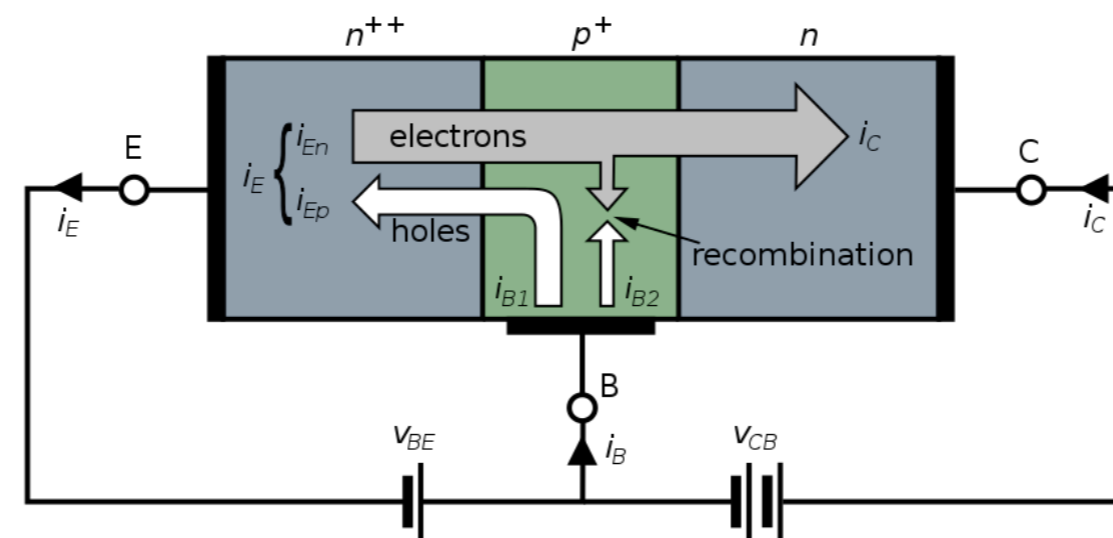- The Bipolar Junction Transistor (BJT) has three layers of N or P material connected to electrodes:




- Depending on the arrangement of layers, a BJT is either an NPN or PNP transistor.



The Transistor

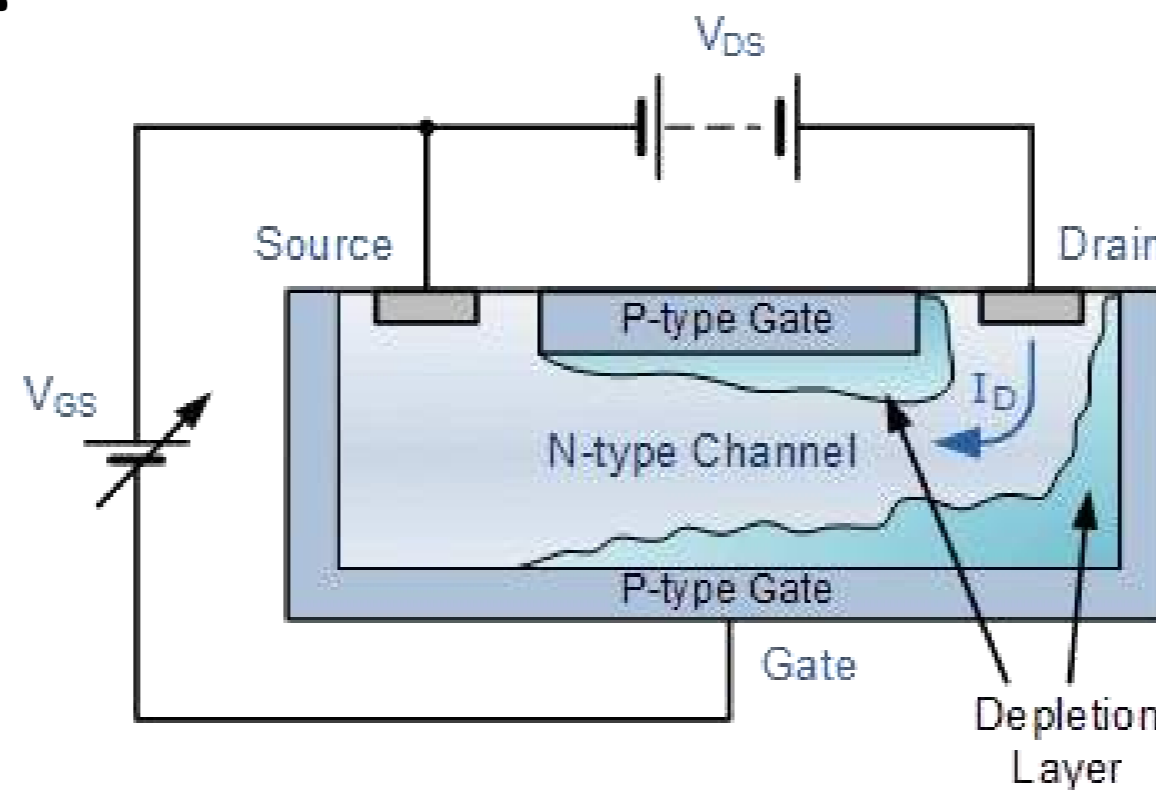
- The Field-Effect Transistor (FET) has a conducting path or channel of N and P material connected to the drain and source electrodes.





The Transistor

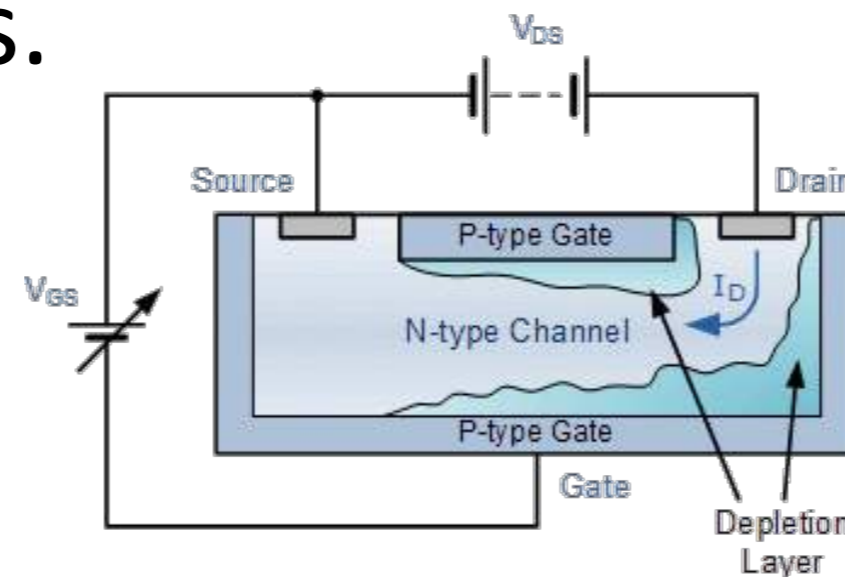
- The Field-Effect Transistor (FET) has a conducting path or channel of N and P material connected to the drain and source electrodes.




- Voltage applied to the gate electrode controls current through the channel.



The Integrated Circuit

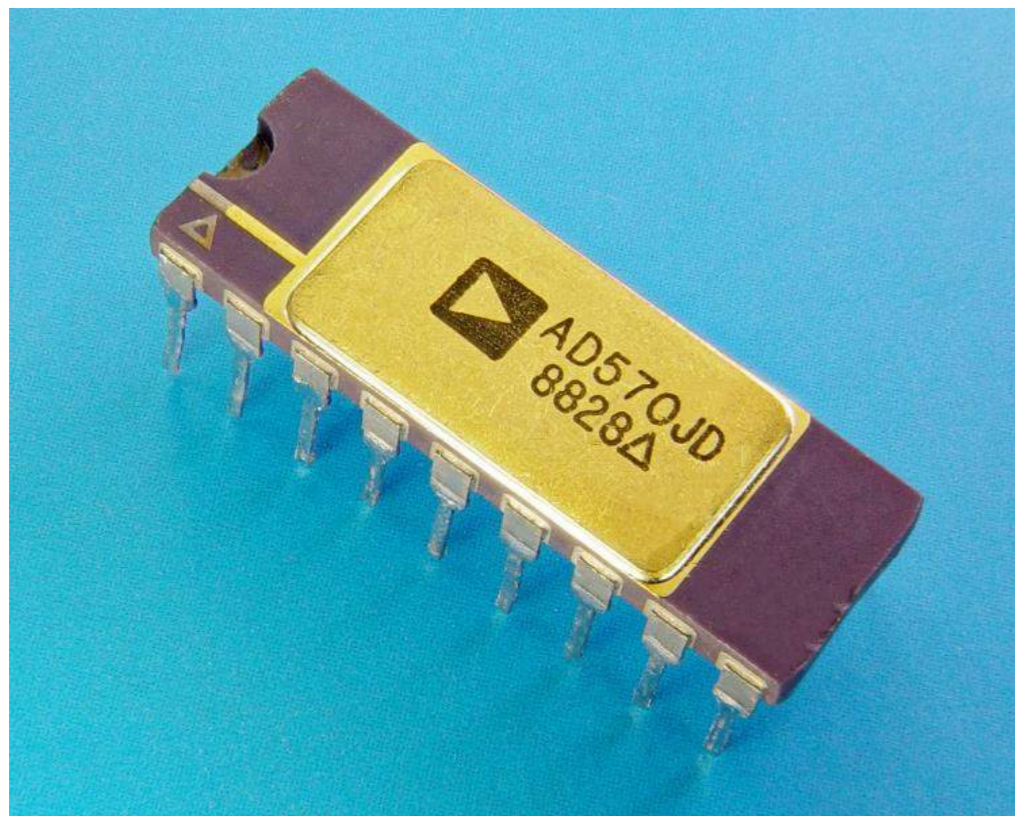

© Mister RF (via Wikimedia Commons)

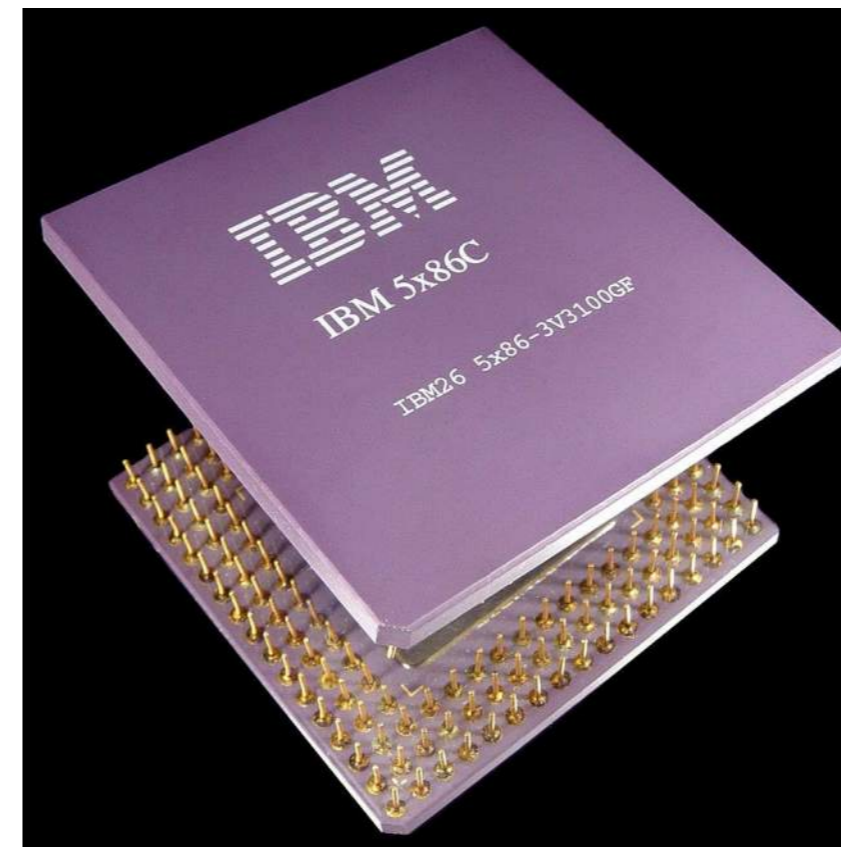


© Mister RF (via Wikimedia Commons)



The Integrated Circuit

- The integrated circuit is a collection of components contained in one device that accomplishes a specific task.

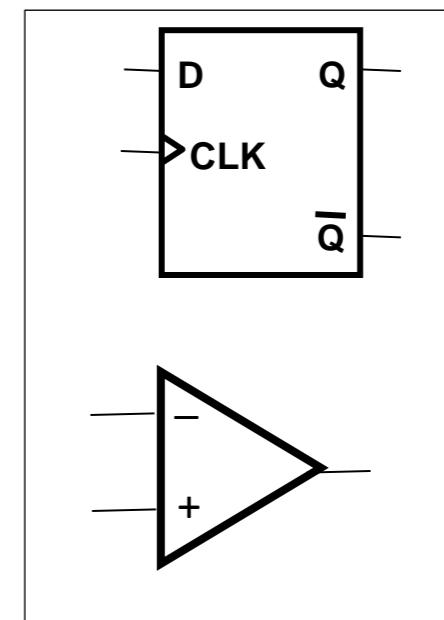- Schematic symbol
- Designator (IC or U)





Protective Components




© Mcapdevila (via Wikimedia Commons)



Protective Components

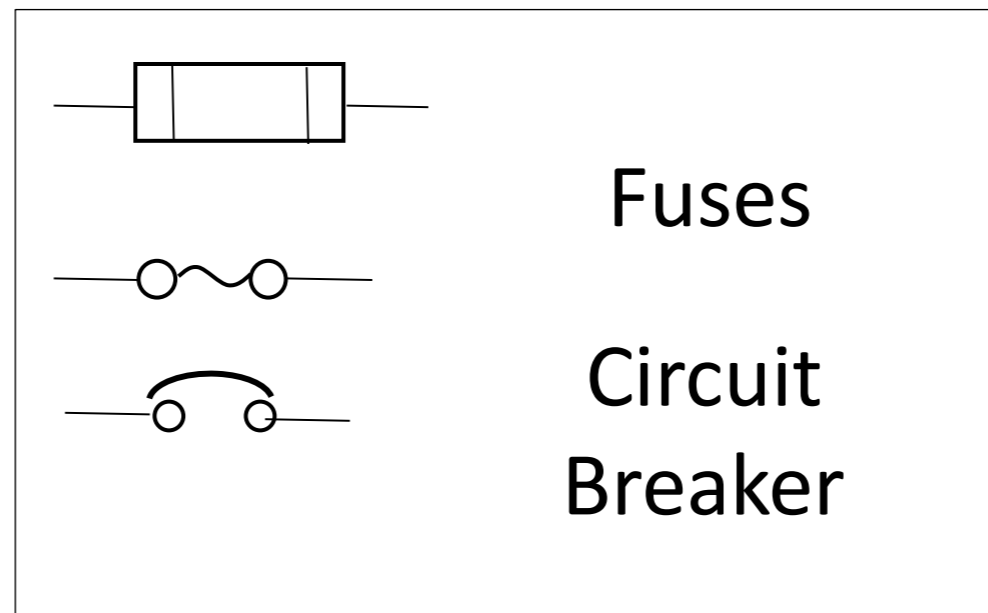- Fuses and circuit breakers are designed to remove power in case of a circuit overload.
- Schematic symbol
- Designator (F or CB)





Protective Components

- Fuses and circuit breakers are designed to remove power in case of a circuit overload.
 - Fuses blow – one time protection



Protective Components

- Fuses and circuit breakers are designed to remove power in case of a circuit overload.
 - Fuses blow – one time protection
 - Circuit breakers trip – can be reset and reused




Protective Components

- Fuses and circuit breakers are designed to remove power in case of a circuit overload.
 - Fuses blow – one time protection
 - Circuit breakers trip – can be reset and reused
 - Always use proper rating



Switches

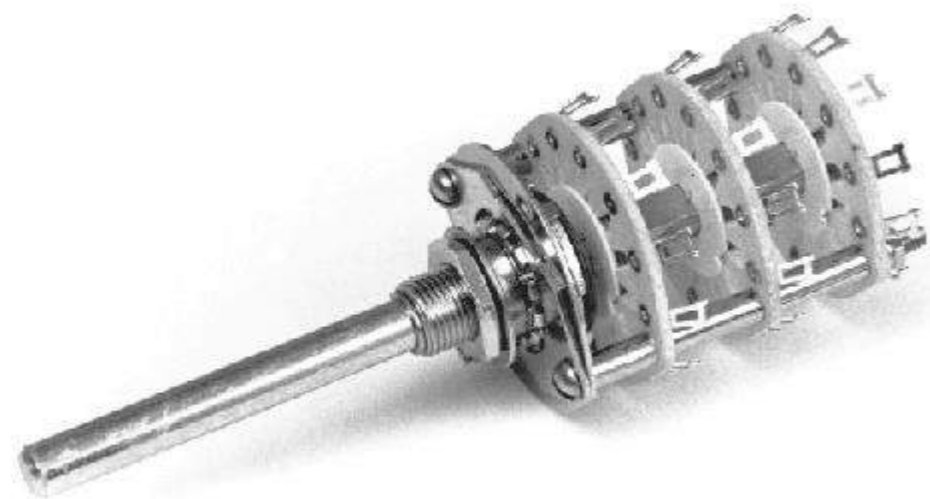

© Raeky (via Wikimedia Commons)




© Achalshanth (via Wikimedia Commons)



Switches

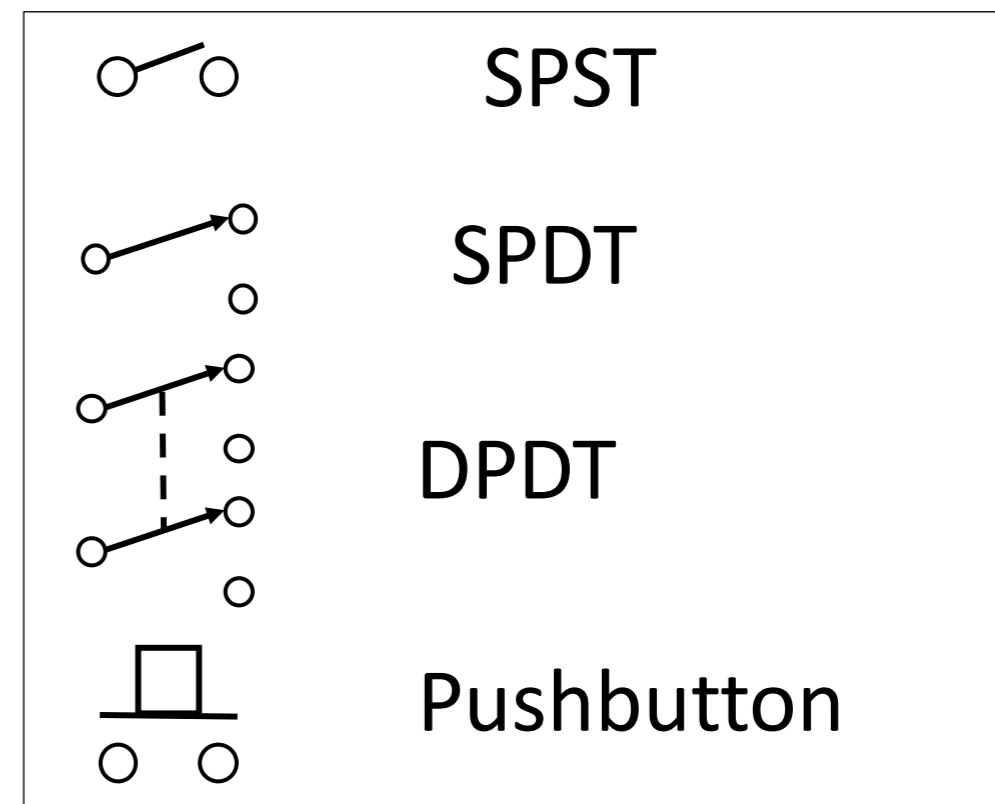
- Switches are used to interrupt or allow current to flow.
- Designator (S or SW)
- Schematic Symbol:





Switches

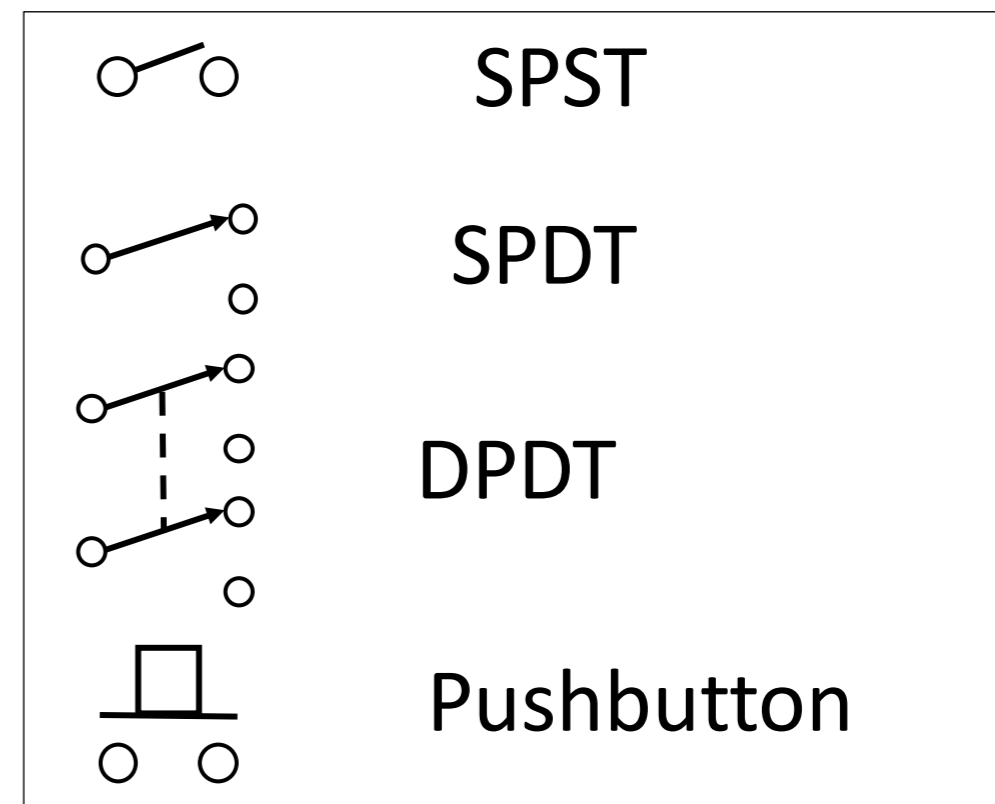
- Switches are used to interrupt or allow current to flow.
- Each circuit controlled by the switch is a *pole*






Switches

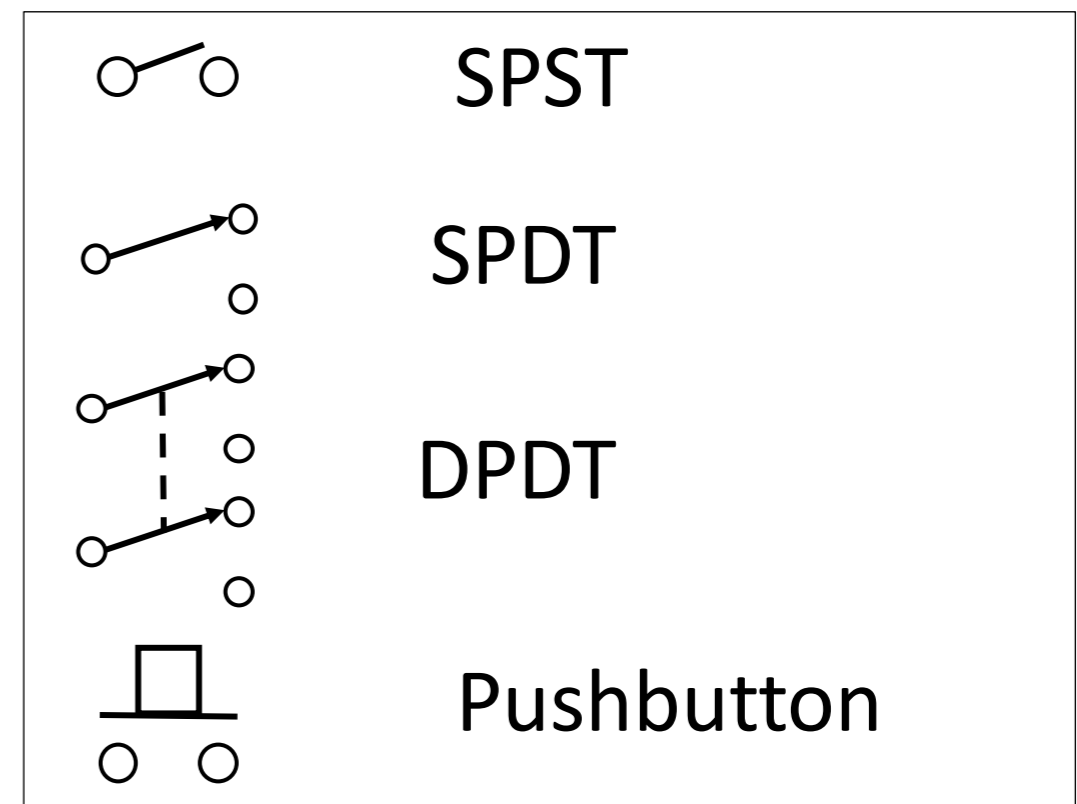- Switches are used to interrupt or allow current to flow.
- Each circuit controlled by the switch is a *pole*
- Each position is called a *throw*





Relays

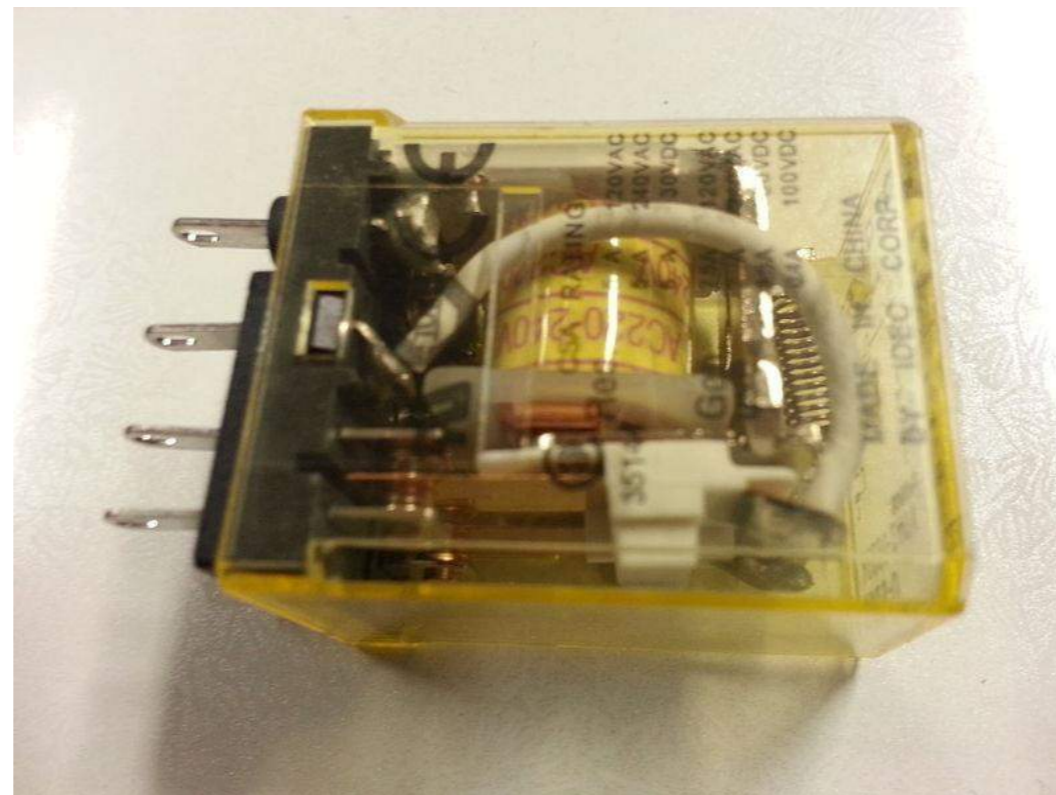


© Balurbala (via Wikimedia Commons)



Relays

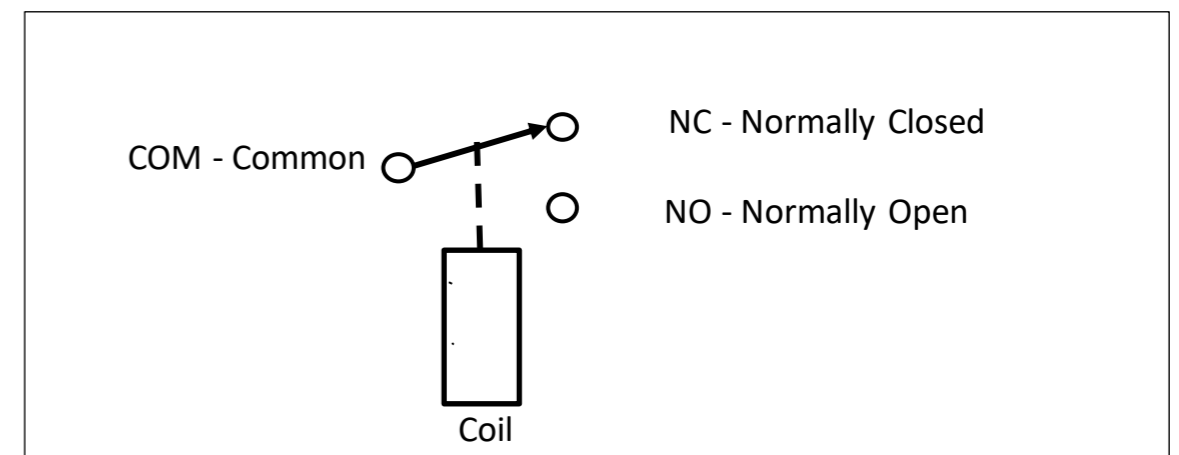
- Relays are switches activated by current in a coil (electromagnet)
- Designator (K or RLY)
- Schematic Symbol





Relays

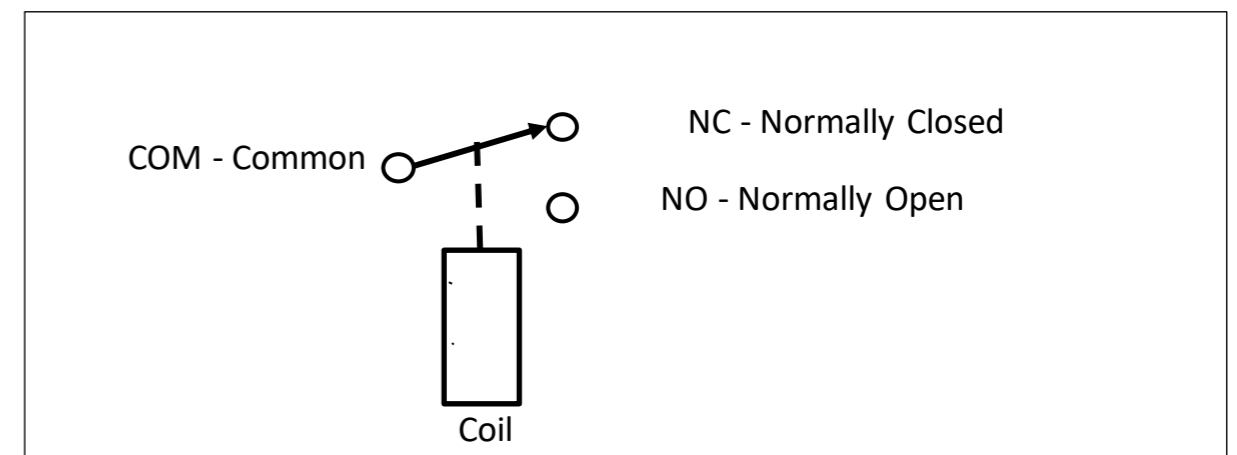
- Relays are switches activated by current in a coil (electromagnet)
- Relays use the same pole/throw names as switches





Relays

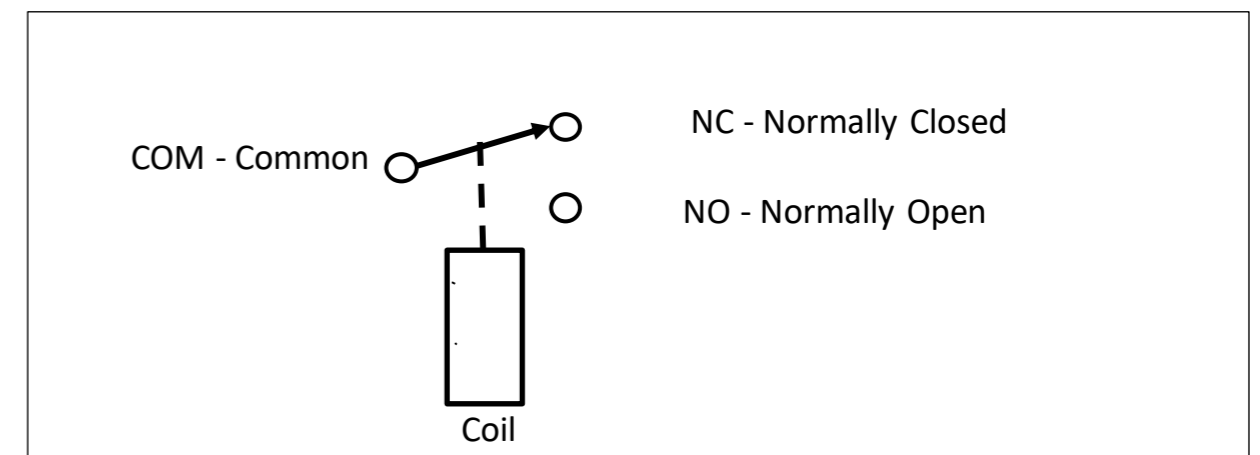
- Relays are switches activated by current in a coil (electromagnet)
- Relays use the same pole/throw names as switches
- The moving switch is called the *armature*





Relays

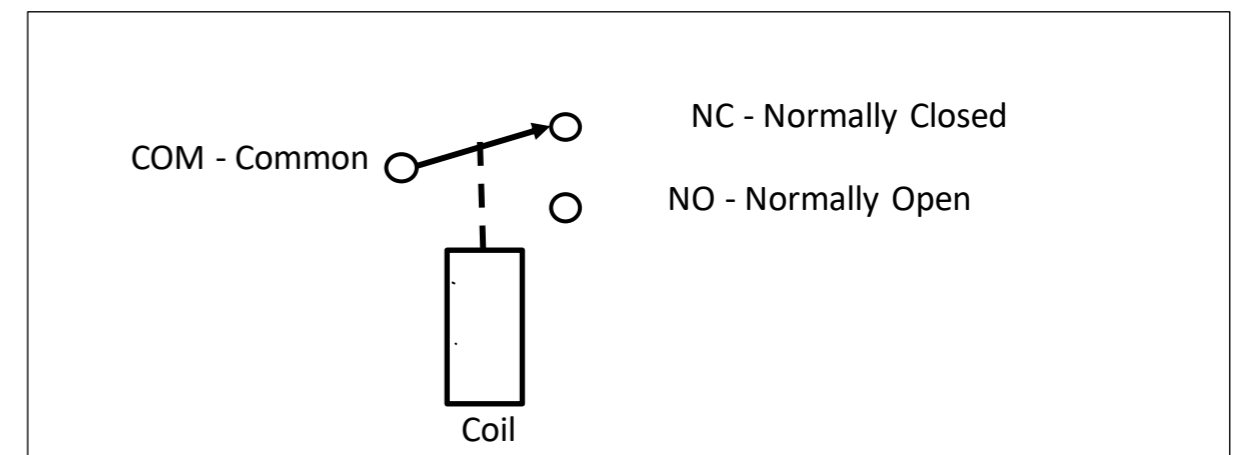- Relays are switches activated by current in a coil (electromagnet)
- Relays use the same pole/throw names as switches
- The moving switch is called the *armature*
- *Contacts* are named by when they are connected



Ham Radio License Course

Discovering the Excitement of Ham Radio



ARRL The national association for
AMATEUR RADIO®

Are there any questions?