


Yet Another Code Practice Oscillator

5/5/2021

Jon - KI6RT


While most HF rigs can be configured to act as a code practice oscillator for new hams an IC 7300, FT 991, or other comparable transceiver may not be readily available. While CPO (code practice oscillators) circuits are everywhere this CPO design (leveraged from implementations created by others and placed into the public domain) attempts to:

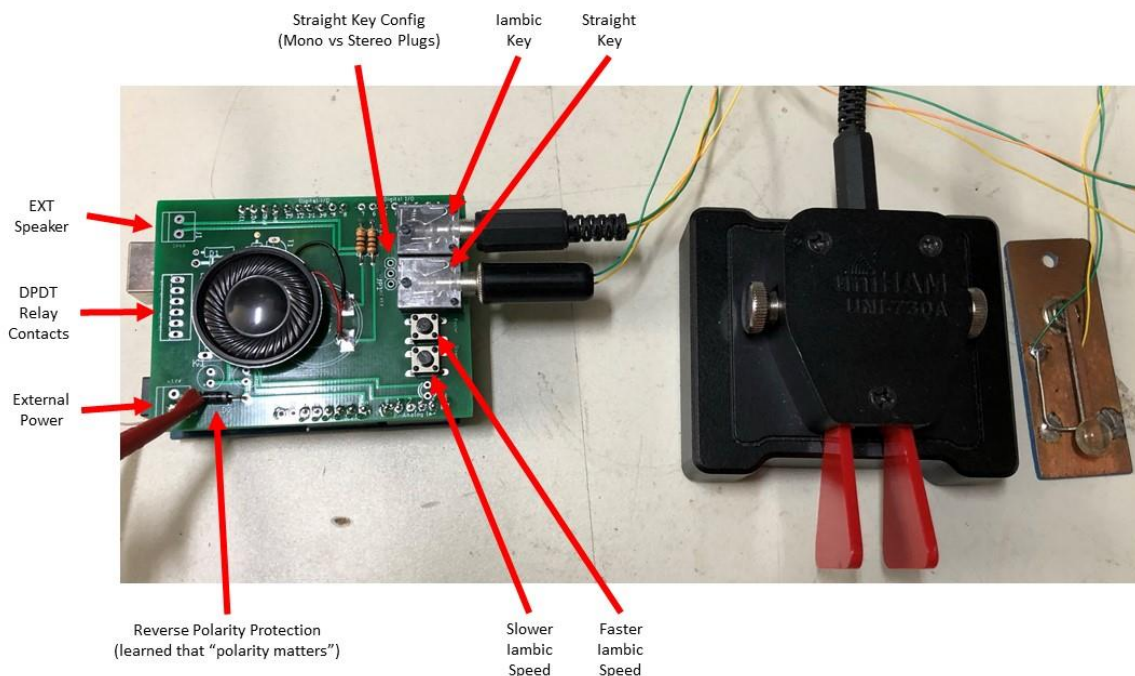1. Build on low cost Arduino Uno (now available for as little as \$3-\$5/board) as a shield
2. Power flexibility (5V to 30V DC) – I am using a 9V Battery
3. Supports straight and lambic keyers driving a low cost speaker
4. May be used to key other transmitters/transceivers and or TR switches using the optional circuitry provided via a DPDT relay
5. Enough remaining memory and spare DIO pins to add your own features (e.g. button to auto send CW messages like “CW CW CW QRP de KI6RT K”)



Overview

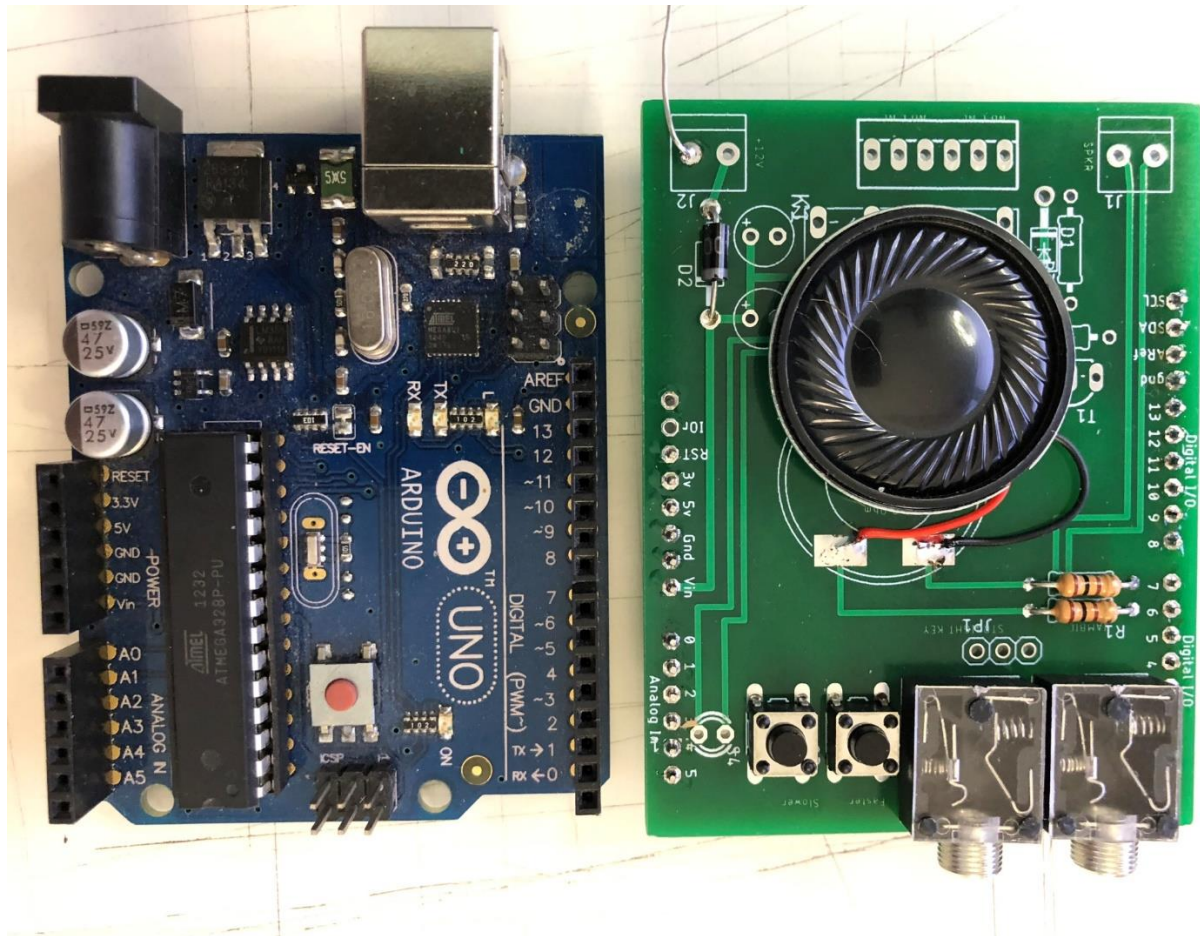The CPO is designed as an Arduino Uno shield using standard 2.54 spacing headers. DPDT relay used to key a transmitter is not populated due to potential interference with the Arduino USB connector.




Notes

1. Miniature speaker is glued on using silicon calking or double stick tape
2. Jumper JP1 is not populated but is provided in case a mono phone jack is used
3. J1 is provided to solder an optional external speaker


Bill Of Materials

ITEM	REF DESIG	DESCRIPTION	MANUFACTURER	ORDER INFO
optional	C1, C2	47uF 25V electrolytic capacitor	generic	
1	R1, R2	100 ohm ¼ watt resistor	generic	Tadya Electronics A-2051
optional	R3	4.7K ¼ watt resistor	generic	
optional	R4	1K ¼ watt resistor	generic	
2	D1, D2	1N4001A silicon diode	generic	Tadya Electronics A-162
optional	T1	2N2222 NPN transistor	generic	
optional	LED1	5mm LED, color of users choice	generic	
3	S2, S3	Tactile momentary switch	C&K PTS645SK43JSMTR92 LFS	Mouser 611-SM43JSMTR92LFS
4	X1, X2	3.5 mm headphone jack	Switchcraft 35RAPC2BH3	Mouser 502-35RAPC2BH3
user supplied	SPK1	8 ohm miniature speaker	Visaton K23 – 8 ohm	Mouser 243-K23-8OHM
optional	K1	12V DPDT Relay	generic	
user supplied	na	40 pin 2.54mm header strip	generic	Tadya Electronics A-197
user supplied	Na	Arduino Uno (any generation or clone will work)	generic	Sparkfun \$22.95 Amazon \$20.16 eBay \$3.99

Schematic

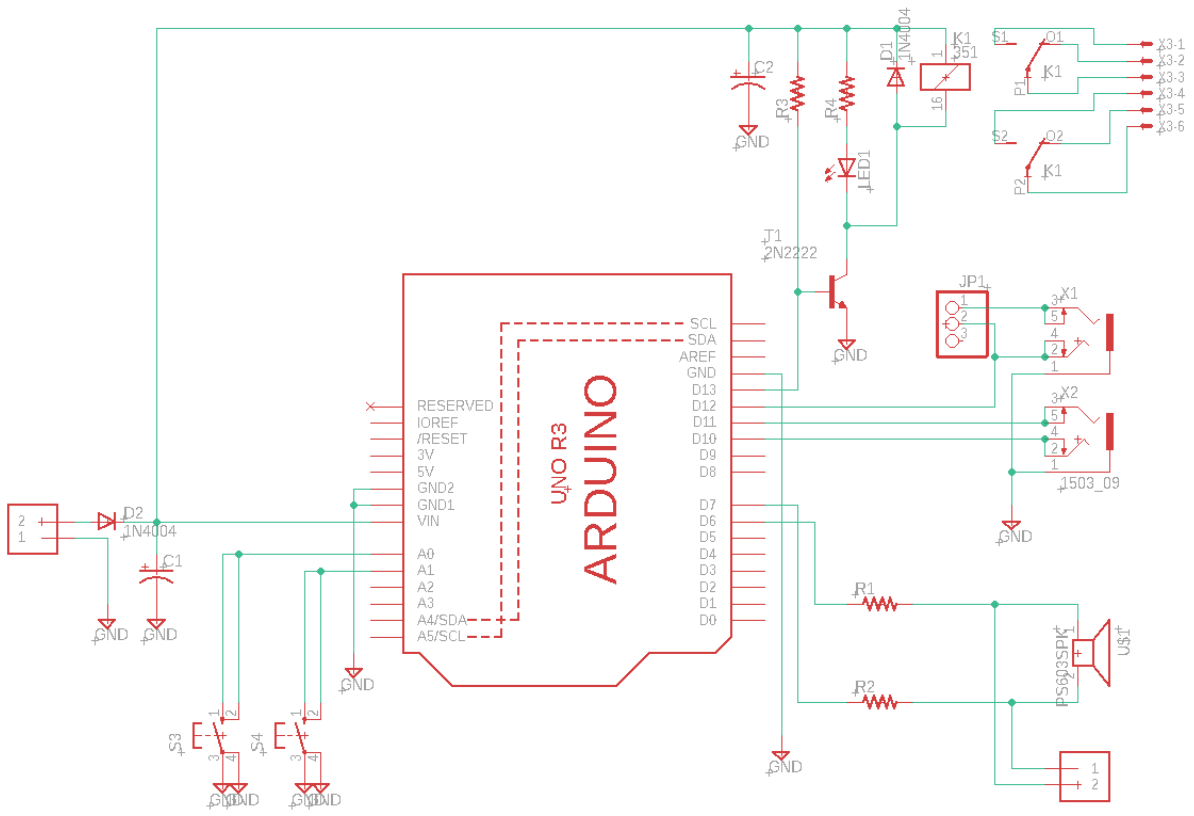

PCB Layout

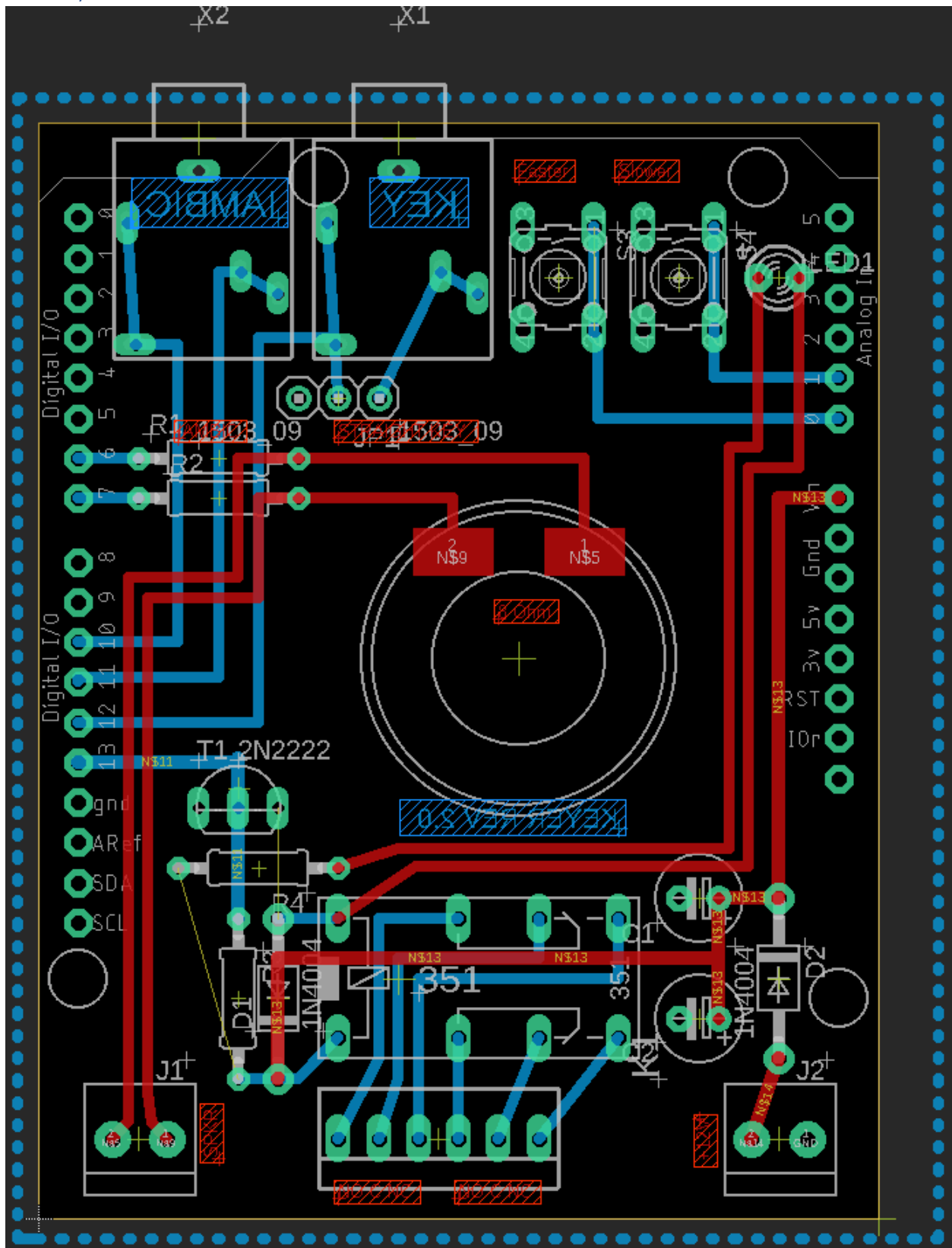

Build Instructions

1. Trim & solder header strips
2. Install X1 & X2 (depending on supplier may need to trim leads to insert into PCB)
3. Install S2 & S3
4. Install R1 & R2
5. Install SPK1 and glue to PCB
6. Install D2 polarity protection diode
7. Program the Arduino Uno (email me for the latest source that I will upload to groups.io once fully debugged)

Operation

1. Plug shield onto programmed Arduino, connect key and power.
2. In lmbic mode use the momentary contact switch to increase/decrease CW rate.